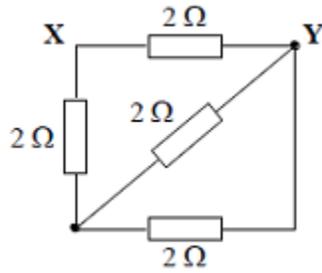


- 1** The diagram shows a network of four $2\ \Omega$ resistors.




The effective resistance, in Ω , between **X** and **Y** is

- A** 0.5
- B** 1.2
- C** 1.7
- D** 2.0

(Total 1 mark)

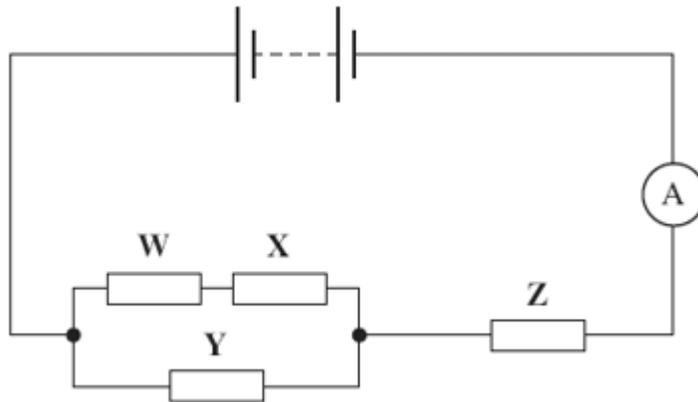- 2** The circuit shown in the figure below shows an arrangement of resistors, **W**, **X**, **Y**, **Z**, connected to a battery of negligible internal resistance.



The emf of the battery is 10V and the reading on the ammeter is 2.0 A.

- (a) (i) Calculate the total resistance of the circuit.

answer = Ω

(1)

- (ii) The resistors **W**, **X**, **Y**, and **Z** all have the same resistance. Show that your answer to part (a) (i) is consistent with the resistance of each resistor being 3.0Ω .

answer = Ω

(3)

- (b) (i) Calculate the current through resistor **Y**.

answer = A

(2)

- (ii) Calculate the pd across resistor **W**.


answer = V

(2)

(Total 8 marks)

3

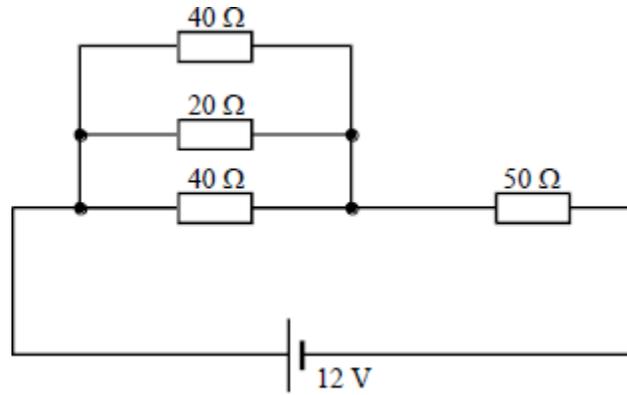A battery of e.m.f. 12 V and negligible internal resistance is connected to a resistor network as shown in the circuit diagram.



(a) Calculate the total resistance of the circuit.

.....

.....

.....

.....

.....

(3)

(b) Calculate the current through the 50 Ω resistor.

.....


.....

(1)

(Total 4 marks)

4

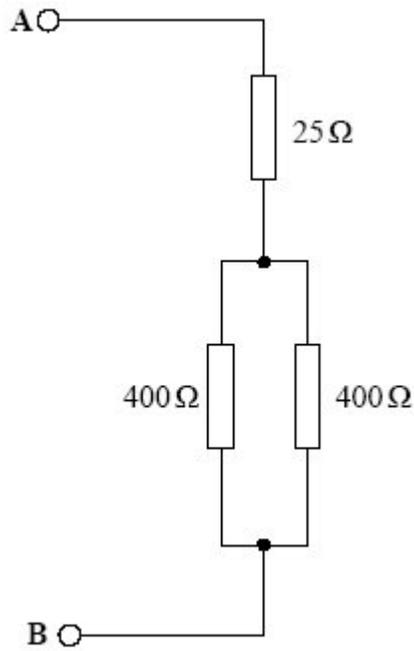The diagram below shows an arrangement of resistors.



- (a) Calculate the total resistance between terminals **A** and **B**.

answer = Ω

(2)

- (b) A potential difference is applied between the two terminals, **A** and **B**, and the power dissipated in each of the $400\ \Omega$ resistors is $1.0\ \text{W}$.

- (i) Calculate the potential difference across the $400\ \Omega$ resistors.

answer = V

(ii) Calculate the current through the 25 Ω resistor.

answer = A

(iii) Calculate the potential difference applied to terminals **A** and **B**.

answer = V

(6)
(Total 8 marks)


5

(a) Define the electrical resistance of a component.

.....
.....
.....
.....

(2)

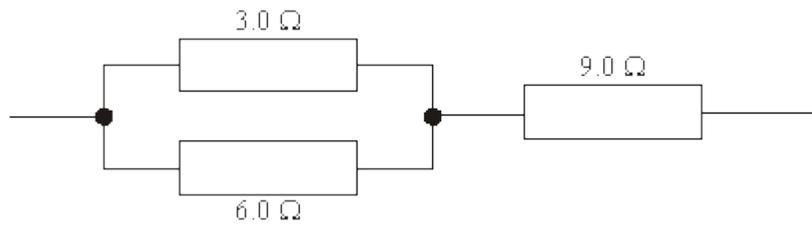(b) Calculate the total resistance of the arrangement of resistors in the figure below.



total resistance

(3)

(c) (i) Calculate the current in the 3.0Ω resistor in the figure above when the current in the 9.0Ω resistor is 2.4 A .

current in the 3.0Ω resistor

(ii) Calculate the total power dissipated by the arrangement of resistors in the figure above when the current in the 9.0Ω resistor is 2.4 A .


total power

(4)

(Total 9 marks)

6

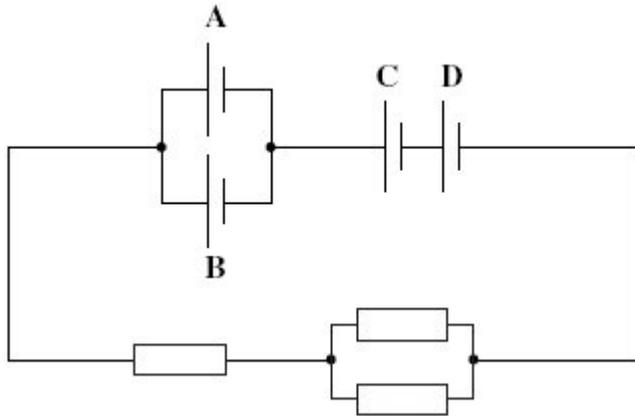The circuit in the diagram below contains four identical new cells, **A**, **B**, **C** and **D**, each of emf 1.5V and negligible internal resistance.



(a) The resistance of each resistor is 4.0Ω .

(i) Calculate the total resistance of the circuit.

answer = Ω

(1)

(ii) Calculate the total emf of the combination of cells.

answer = V

(1)

(iii) Calculate the current passing through cell **A**.

answer = A

(2)

- (iv) Calculate the charge passing through cell **A** in five minutes, stating an appropriate unit.

answer =

(2)

- (b) Each of the cells can provide the same amount of electrical energy before going flat. State and explain which two cells in this circuit you would expect to go flat first.

.....

.....

.....

.....

.....


.....

(3)

(Total 9 marks)

7

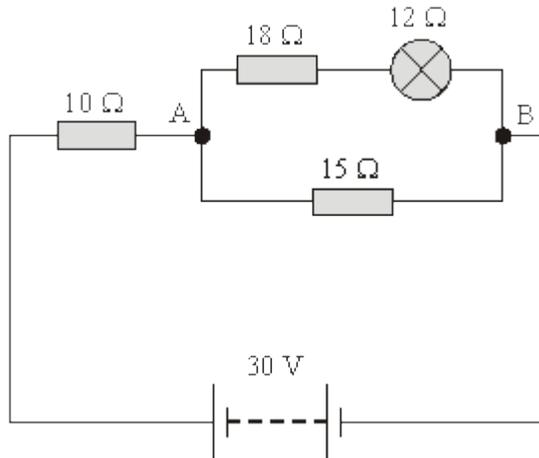In the circuit shown in the figure below, the battery, of negligible internal resistance, has an emf of 30 V. The pd across the lamp is 6.0 V and its resistance is 12 Ω.



(a) Show that the total resistance of the circuit is 20 Ω.

.....

.....

.....

.....

(3)

(b) Calculate

(i) the current supplied by the battery,

.....

.....

(ii) the pd between the points A and B,

.....

.....

(iii) the current in the lamp.

.....

.....

(4)

(c) (i) What is the power of the lamp, in W?

.....

(ii) What percentage of the power supplied by the battery is dissipated in the lamp?

.....

(3)
 (Total 10 marks)

8

In the circuit shown in **Figure 1**, the battery, of emf 6.0V, has negligible internal resistance.

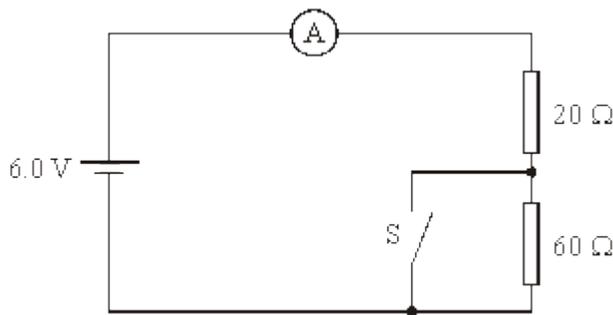


Figure 1

(a) Calculate the current through the ammeter when the switch S is

(i) open,

.....

(ii) closed.

.....

(3)

- (b) The switch S is now replaced with a voltmeter of infinite resistance. Determine the reading on the voltmeter.

.....

(2)
(Total 5 marks)

9

- (a) A student is given three resistors of resistance 3.0Ω , 4.0Ω and 6.0Ω respectively.

- (i) Draw the arrangement, using all three resistors, which will give the largest resistance.

- (ii) Calculate the resistance of the arrangement you have drawn.

.....

- (iii) Draw the arrangement, using all three resistors, which will give the smallest resistance.

- (iv) Calculate the resistance of the arrangement you have drawn.

.....

(5)

- (b) The three resistors are now connected to a battery of emf 12 V and negligible internal resistance, as shown in **Figure 1**.

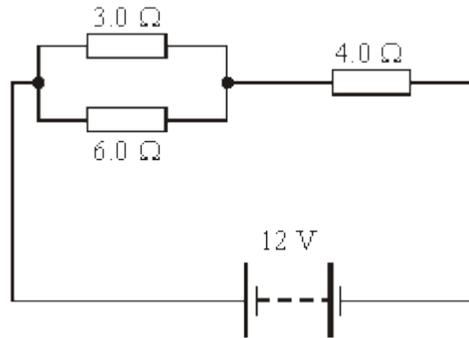


Figure 1

- (i) Calculate the total resistance in the circuit.

.....

- (ii) Calculate the voltage across the 6.0 Ω resistor.

.....

(4)
 (Total 9 marks)

10


- (a) X and Y are two lamps. X is rated at 12 V, 24 W and Y at 6.0 V, 18 W. Calculate the current through each lamp when it operates at its rated voltage.

X:

Y:

(2)

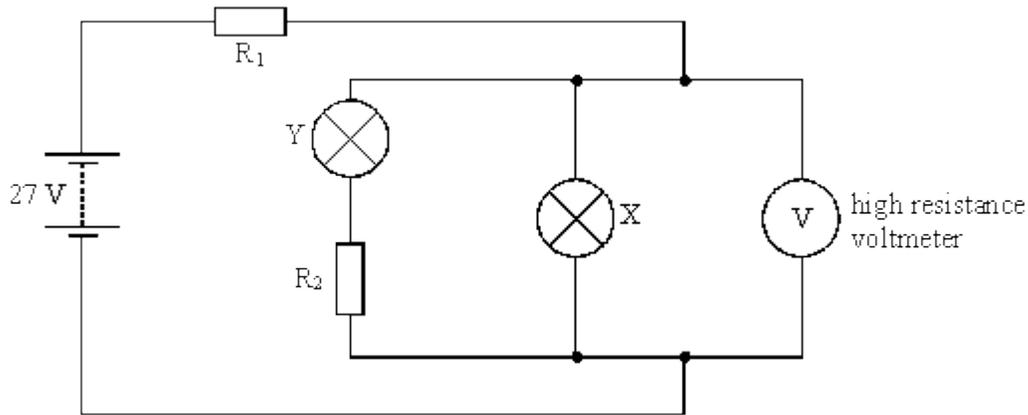- (b) The two lamps are connected in the circuit shown. The battery has an emf of 27 V and negligible internal resistance. The resistors R_1 and R_2 are chosen so that the lamps are operating at their rated voltage.



- (i) What is the reading on the voltmeter?

.....

- (ii) Calculate the resistance of R_2 .

.....

- (iii) Calculate the current through R_1 .

.....

- (iv) Calculate the voltage across R_1 .

.....

- (v) Calculate the resistance of R_1 .

.....

(7)
 (Total 9 marks)

11

In each of the following circuits the battery has negligible internal resistance and the bulbs are identical.

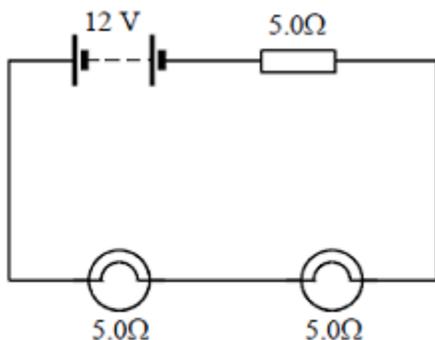


Figure 1

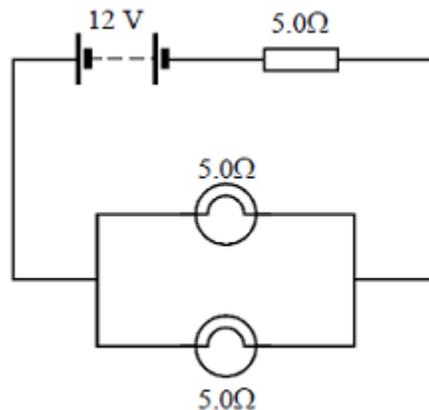


Figure 2

(a) For the circuit shown in **Figure 1** calculate

(i) the current flowing through each bulb,

.....

(ii) the power dissipated in each bulb.

.....

(2)

(b) In the circuit shown in **Figure 2** calculate the current flowing through each bulb.

.....

(3)

(c) Explain how the brightness of the bulbs in **Figure 1** compares with the brightness of the bulbs in **Figure 2**.

.....

(2)

(Total 7 marks)

12

Four resistors, each having resistance of $50\ \Omega$, are connected to form a square. A resistance meter measured the resistance between different corners of the square. Determine the resistance the meter records when connected between the following corners.

- (a) Between A and C, as in **Figure 1**.

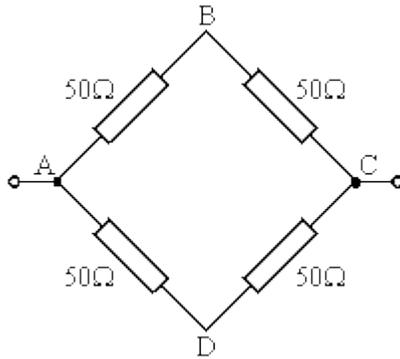


Figure 1

.....

.....

.....

.....

(2)

(b) Between A and B, as in **Figure 2**.

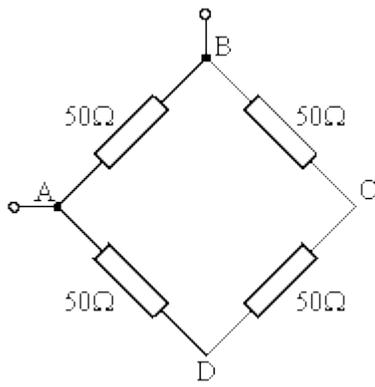


Figure 2

.....

.....


.....

.....

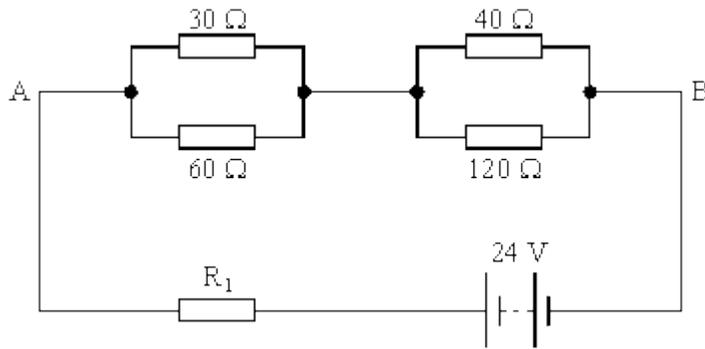(3)
(Total 5 marks)

13

A battery of emf 24 V and negligible internal resistance is connected to a resistor network as shown in the circuit diagram in the diagram below.



- (a) Show that the resistance of the single equivalent resistor that could replace the four resistors between the points A and B is 50 Ω.

.....

.....

.....

.....

.....

.....

.....

(4)

- (b) If R_1 is 50 Ω, calculate

- (i) the current in R_1 ,

.....

.....

- (ii) the current in the 60 Ω resistor.

.....


.....

.....

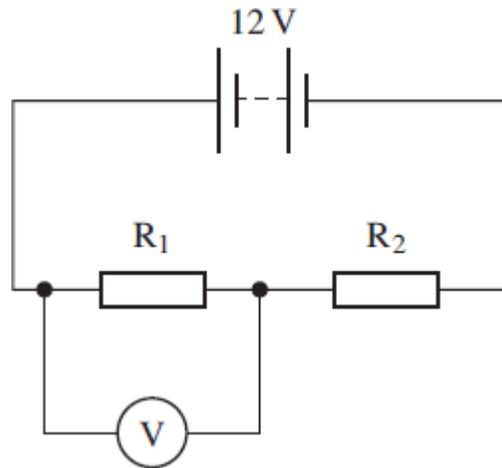(4)
(Total 8 marks)

14

The figure below shows two resistors, R_1 and R_2 , connected in series with a battery of emf 12 V and negligible internal resistance.



(a) The reading on the voltmeter is 8.0 V and the resistance of R_2 is 60 Ω .

(i) Calculate the current in the circuit.

answer = A

(2)

(ii) Calculate the resistance of R_1 .

answer = Ω

(1)

(iii) Calculate the charge passing through the battery in 2.0 minutes. Give an appropriate unit for your answer.

answer = unit =

(2)

- (b) In the circuit shown in the figure above R_2 is replaced with a thermistor. State and explain what will happen to the reading on the voltmeter as the temperature of the thermistor increases.

.....

.....

.....

.....

.....

.....

(3)
(Total 8 marks)

15

- (a) In the circuit in **Figure 1**, the battery, of emf 15 V and the negligible internal resistance, is connected in series with two lamps and a resistor. The three components each have a resistance of 12Ω .

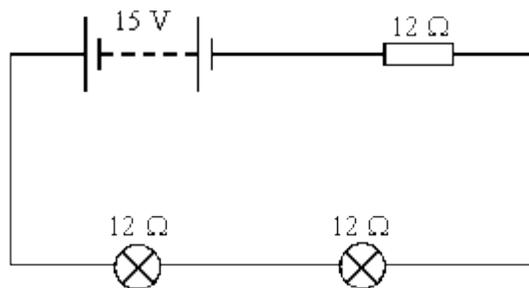


Figure 1

- (i) What is the voltage across each lamp?

.....

- (ii) Calculate the current through the lamps.

.....

.....

(3)

(b) The two lamps are now disconnected and reconnected in parallel as shown in **Figure 2**.

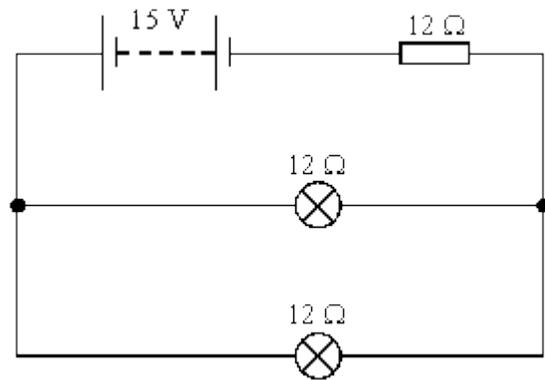


Figure 2

(i) Show that the current supplied by the battery is 0.83 A.

.....

.....

.....

.....

(ii) Hence show that the current in each lamp is the same as the current in the lamps in the circuit in **Figure 1**.

.....

.....

.....

.....

(3)

(c) How does the brightness of the lamps in the circuit in **Figure 1** compare with the brightness of the lamps in the circuit in **Figure 2**?

Explain your answer.

.....

.....

.....

(2)

(Total 8 marks)

16

(a) **Figure 1** shows two possible arrangements of connecting three resistors, each resistor having a resistance of $40\ \Omega$.

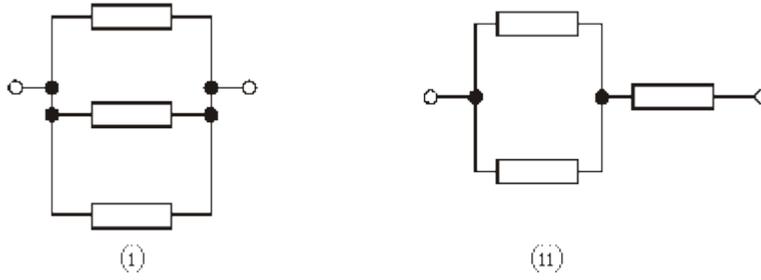


Figure 1

Calculate the equivalent resistance in each case.

(i)

.....

.....

(ii)

.....

.....

(3)

- (b) The designer of a heating element for the rear window of a car decides to connect six separate heating elements together as shown in **Figure 2**. Each element has a resistance of 6.0Ω and the unit is connected to a 12 V dc supply having zero internal resistance.

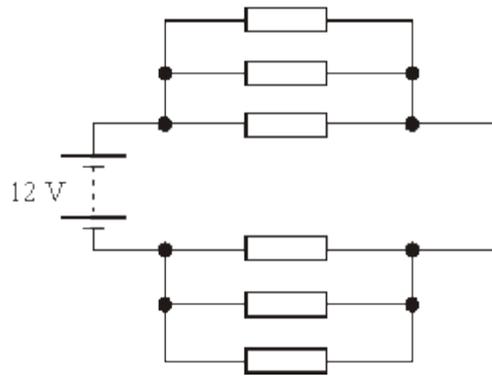


Figure 2

- (i) Calculate the current in each single element.

.....

.....

.....

.....

.....

- (ii) With the aid of a similar calculation give a reason why the heater would not be as effective if all six were connected in series.

.....


.....

.....

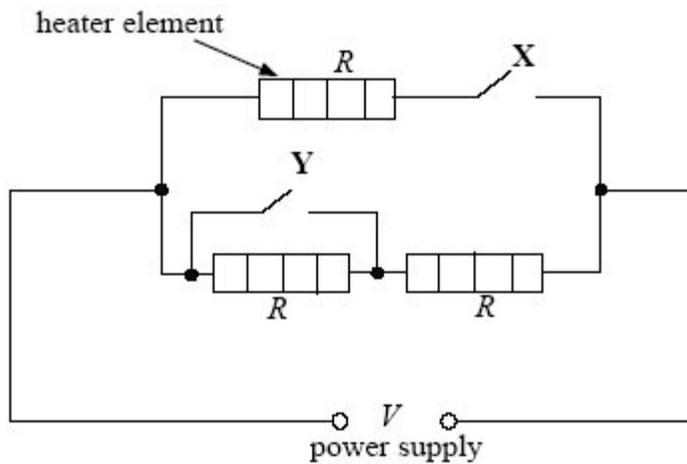(5)
(Total 8 marks)

17

The diagram below shows the circuit for a small convector heater. Heater elements can be switched in and out of the circuit using switches **X** and **Y**. Each element has a resistance R and the power supply has an emf V .



- (a) The table shows the possible combinations of open and closed switches. When a switch is closed, charge can flow through it.

Complete the table. Assume that the internal resistance of the power supply is negligible. The first row of the table has been done for you.

switch combination	total resistance in circuit
X open, Y closed	R
X closed, Y open	
X open, Y open	
X closed, Y closed	

(3)

- (b) State and explain which switch combination will dissipate least energy.

.....

.....

.....

(2)

- (c) Explain in terms of electron flow how thermal energy is produced in one of the heater elements when charge flows through it.

.....

(2)

- (d) The power supply for the heater is replaced with one that has a higher internal resistance. Explain how this change will affect the thermal energy output of the heater for a given switch combination. State which switch combination will be affected most by the change.

.....

(3)

- (e) The resistance of each heater element is 68Ω . Each one is made from 7.2 m of nichrome wire wound on a rod.

- (i) Calculate the radius of the nichrome wire.

resistivity of nichrome = $1.1 \times 10^{-6} \Omega \text{ m}$

radius m

(2)


- (ii) Suggest **two** properties that the rod must have to make it suitable in this application.

.....

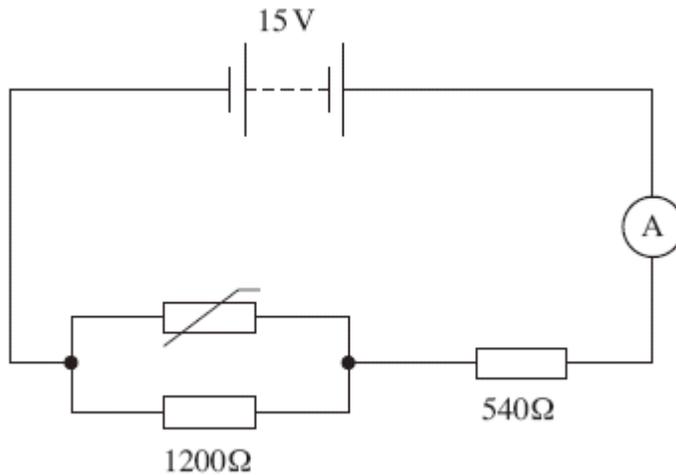(2)

(Total 14 marks)

- 18** The circuit shown below shows a thermistor connected in a circuit with two resistors, an ammeter and a battery of emf 15V and negligible internal resistance.



- (a) When the thermistor is at a certain temperature the current through the ammeter is 10.0 mA.
- (i) Calculate the pd across the 540 Ω resistor.

answer = V

(1)

- (ii) Calculate the pd across the 1200 Ω resistor.

answer = V

(1)

(iii) Calculate the resistance of the parallel combination of the resistor and the thermistor.

answer = Ω

(2)

(iv) Calculate the resistance of the thermistor.

answer = Ω

(2)

(b) The temperature of the thermistor is increased so that its resistance decreases. State and explain what happens to the pd across the 1200 Ω resistor.

.....

.....

.....


.....

(3)

(Total 9 marks)

19

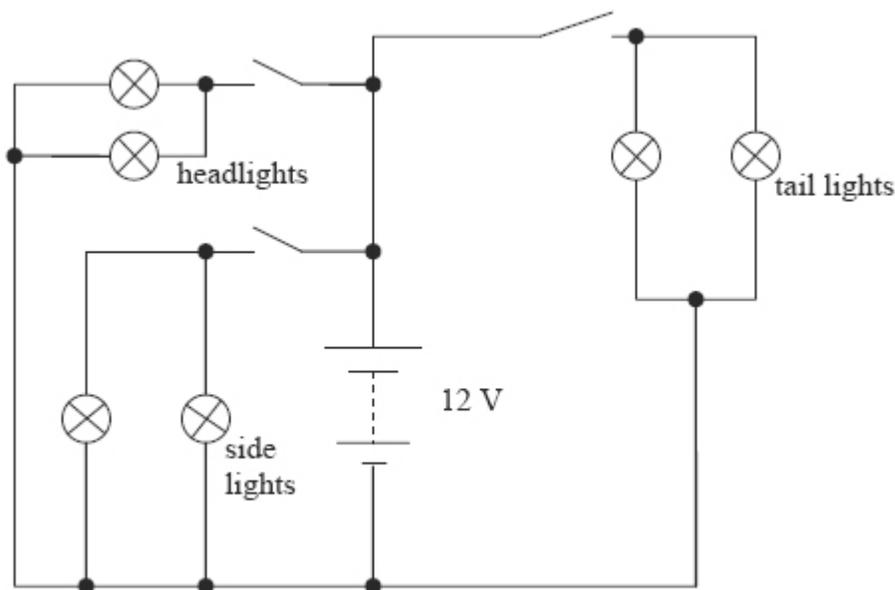The following figure shows part of the circuit diagram for a car lighting circuit.



The table shows the power rating of the various lamps used in the circuit.

Lamp	Power/W
Tail light	8.0
Sidelight	5.0
Headlight	60

(a) Explain why all the lamps are connected in parallel.

.....

.....

.....

(2)

(b) The emf of the battery used in the circuit is 12 V and it has negligible internal resistance. Calculate the current through the battery when the headlights and tail lights are both on.

current A

(3)

(c) (i) State which lamp filament has the least resistance.

.....

(ii) Explain why this resistance is smaller when the lamp is first switched on.

.....

(3)

(d) The side and tail lamps are accidentally left on for 12 hours when the car is parked.

(i) Calculate the energy dissipated in the lamps during this time.

energy J

(ii) The battery used by the car is capable of delivering a current of 1.5 A for 24 hours. The car's starter motor needs a current of 100 A which lasts for at least one second in order to start the engine. State and explain whether the car is likely to start after the 12 hours.

.....

.....

.....

.....

(5)

(Total 13 marks)

20

(a) A set of decorative lights consists of a string of lamps. Each lamp is rated at 5.0 V, 0.40 W and is connected in series to a 230 V supply.

Calculate

(i) the number of lamps in the set, so that each lamp operates at the correct rating,

.....

(ii) the current in the circuit,

.....

(iii) the resistance of each lamp,

.....

(iv) the total electrical energy transferred by the set of lights in 2 hours.

.....

(5)

(b) When assembled at the factory, one set of lights inadvertently contains 10 lamps too many. All are connected in series. Assume that the resistance of each lamp is the same as that calculated in part (a) (iii).

(i) Calculate the current in this set of lights when connected to a 230 V supply.

.....

(ii) How would the brightness of each lamp in this set compare with the brightness of each lamp in the correct set?


.....

(3)

(Total 8 marks)

21

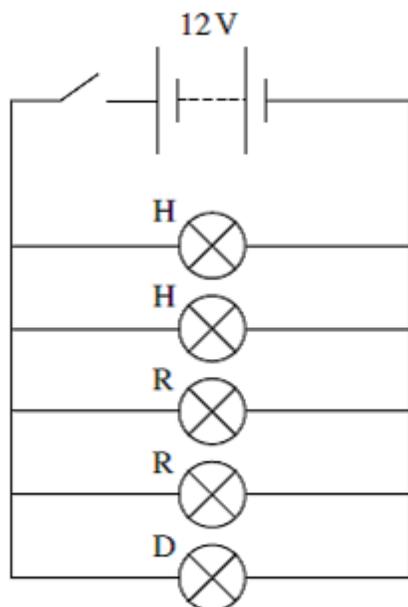The Figure below shows a simplified circuit for the main lights on a car. The battery has an emf of 12 V and no internal resistance.



The table below gives data about the lamps being used in the circuit. The resistances given are correct when the lamp is operating at its normal operating voltage.

LAMP	OPERATING VOLTAGE V	RESISTANCE Ω
H, headlight lamp	12	3.8
R, rear lamp	12	5.6
D, dashboard lamp	12	72

(a) (i) Calculate the power of a single headlight lamp when operating at 12 V.

.....

.....

.....

.....

power W

(2)

(ii) Calculate the resistance of the combination of lamps when operating at 12 V.

.....

resistance Ω

(3)

(iii) Calculate the total power of the combination of lamps when operating at 12 V.

.....

power W

(2)

(b) The battery is replaced with one of a lower emf. State and explain how the resistance of the lamps would have to change in order to achieve the same brightness.


.....

(2)

(Total 9 marks)

22

A battery of negligible internal resistance is connected to lamp P in parallel with lamp Q as shown in **Figure 1**. The emf of the battery is 12 V.

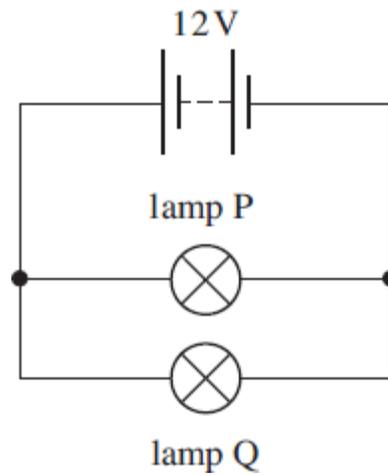Figure 1

(a) Lamp P is rated at 12 V 36 W and lamp Q is rated at 12 V 6 W.

(i) Calculate the current in the battery.

answer = A

(2)

(ii) Calculate the resistance of P.

answer = Ω

(1)

(iii) Calculate the resistance of Q.

answer = Ω

(1)

- (b) State and explain the effect on the brightness of the lamps in the circuit shown in **Figure 1** if the battery has a significant internal resistance.

.....

.....

.....

.....


.....

.....

(3)

- (c) The lamps are now reconnected to the 12 V battery in series as shown in **Figure 2**.

Figure 2

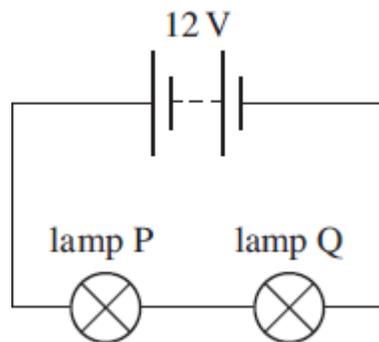

- (i) Explain why the lamps will not be at their normal brightness in this circuit.

.....

.....

.....

.....

.....

.....

(2)

- (ii) State and explain which of the lamps will be brighter assuming that the resistance of the lamps does not change significantly with temperature.

.....

.....

.....


.....

(3)
(Total 12 marks)

23

- (a) The cell in **Figure 1** has an emf of 3.0 V and negligible internal resistance.

Figure 1

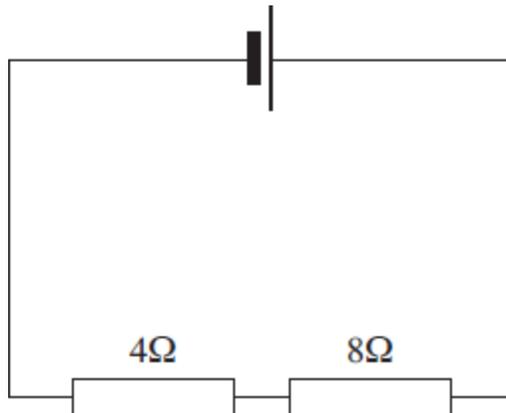


Calculate the potential difference across the 8Ω resistor.

potential difference V

(2)

(b) **Figure 2** shows the same circuit with a voltmeter connected across the $8\ \Omega$ resistor.

Figure 2

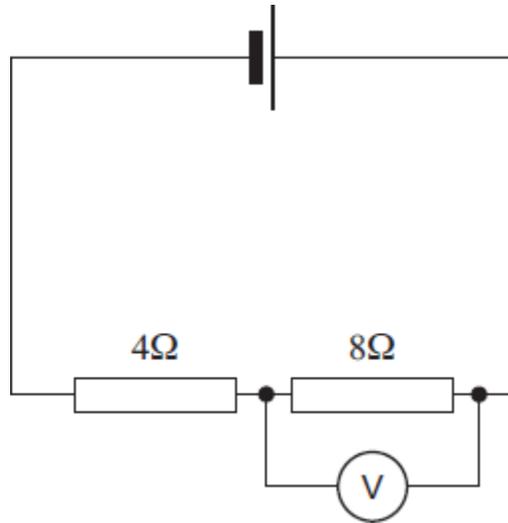


The voltmeter reads 1.8 V. Calculate the resistance of the voltmeter.

resistance Ω

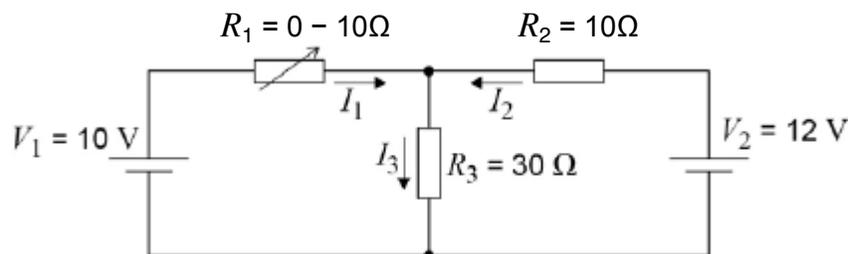(3)
(Total 5 marks)

24

The cells in the circuit shown in the figure below have zero internal resistance. Currents are in the directions shown by the arrows.



R_1 is a variable resistor with a resistance that varies between 0 and $10\ \Omega$.

(a) Write down the relationship between currents I_1 , I_2 and I_3 .

.....

(1)

(b) R_1 is adjusted until it has a value of 0Ω .

State the potential difference across R_3 .

potential difference = V

(1)

(c) Determine the current I_2 .

current = J

(2)

(d) State and explain what happens to the potential difference across R_2 as the resistance of R_1 is gradually increased from zero.

.....

.....

.....

.....


.....

(3)

(Total 7 marks)

25

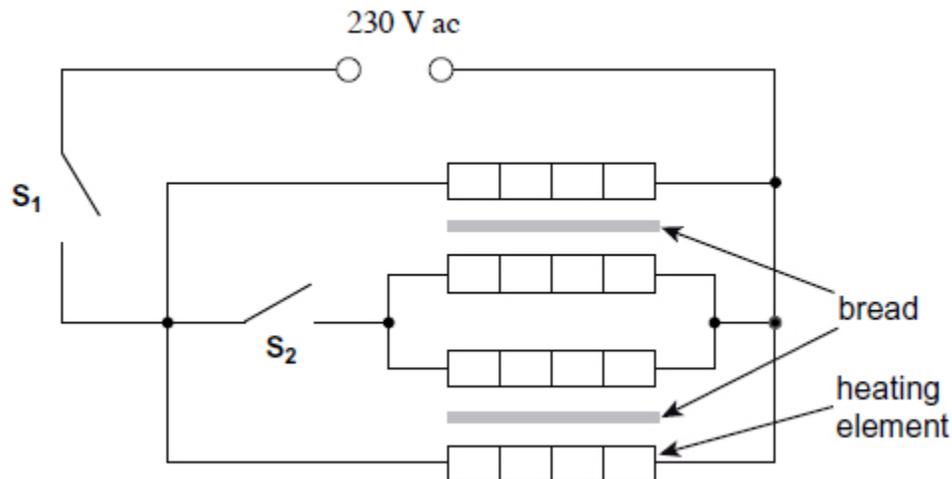The diagram shows the circuit diagram for a two-slice electric toaster that is operated at a mains voltage of 230 V.



The toaster has four identical heating elements and has two settings: normal and low. On the normal setting both sides of the bread are toasted. On the low setting, only one side of the bread is toasted. The setting is controlled by switches S_1 and S_2 .

The table shows the position of each switch and the power for each setting.

Setting	S_1	S_2	Power / W
Low	closed	open	400
Normal	closed	closed	800

(a) Calculate the current in S_2 when the normal setting is selected.

current A

(2)

(b) (i) Show that the resistance of **one** heating element is approximately 260Ω when the toaster is operating at its working temperature.

(2)

(ii) Calculate the total resistance when the normal setting is selected.

resistance Ω

(2)

(iii) Each heating element is made of nichrome wire of diameter 0.15 mm .
The nichrome wire is wrapped around an insulating board.

Determine the length of nichrome wire needed to provide a resistance of 260Ω .

resistivity of nichrome at the working temperature = $1.1 \times 10^{-6} \Omega \text{ m}$

length of wire m

(3)

(c) Explain why the resistivity of the nichrome wire changes with temperature.

.....

.....

.....

.....

.....

(3)

(d) The nichrome wire has an equilibrium temperature of 174°C when the toaster is operating.

Calculate the peak wavelength of the electromagnetic radiation emitted by the wire.

Give your answer to an appropriate number of significant figures.

peak wavelength m

(3)

(Total 15 marks)

Mark schemes

- 1** B [1]
- 2** (a) (i) (use of $R = V/I$)
 $R = 10/2.0 = 5.0 \Omega$ ✓ 1
- (ii) $\frac{1}{R} = \frac{1}{3} + \frac{1}{3+3} = \frac{3}{6}$ ✓
 $R = 2 (\Omega)$ ✓
 $R_{\text{total}} = 2 + 3$ ✓ (= 5 Ω) 3
- (b) (i) voltage across Y = $10.0 - 2.0 \times 3.0 = 4.0 \text{ V}$ ✓
current in Y = $4.0/3.0 = 1.3 \text{ A}$ ✓ 2
- (ii) current through W = 0.67 A ✓
voltage = $0.67 \times 3 = 2.0 \text{ V}$ ✓
(or $4.0/2 = 2.0 \text{ V}$ ✓) 2
- [8]
- 3** (a) (three parallel resistors) give $\frac{1}{40} + \frac{1}{20} + \frac{1}{40} = \frac{1}{R}$ (1)
 $R = 10 (\Omega)$ (1)
10 Ω and 50 Ω in series gives 60 Ω (1)
(allow e.c.f. from value of R) (3)
- (b) ($V = IR$ gives) $12 = I \times 60$ and $I = 0.2 \text{ A}$ (1)
(allow e.c.f. from (a)) (1)
- [4]

4(a) (use of $1/R_{\text{total}} = 1/R_1 + 1/R_2$)

$$1/R_{\text{total}} = 1/400 + 1/400 = 2/400$$

$$R_{\text{total}} = 200 \Omega \text{ (1) (working does not need to be shown)}$$

$$\text{hence total resistance} = 25 + 200 = 225\Omega \text{ (1)}$$

2

(b) (i) (use of $P = V^2/R$)

$$1 = V^2/400 \text{ (1)}$$

$$V^2 = 400 \text{ (working does not need to be shown)}$$

$$V = 20V \text{ (1)}$$

(ii) (use of $I = V/R$)

$$I = 20/400 = 0.05A \text{ (1) (working does not need to be shown)}$$

$$\text{hence current} = 2 \times 0.05 = 0.10A \text{ (1)}$$

(iii) (use of $V = IR$)

$$\text{pd across } 25\Omega \text{ resistor} = 25 \times 0.10 = 2.5V \text{ (1)}$$

(working does not need to be shown)

$$\text{hence maximum applied pd} = 20 + 2.5 = 22.5V \text{ (1)}$$

6

[8]**5**(a) $R = V/I$

M1

with all **three** variables defined
accept voltage

A1

2

(b) use of $1/R = 1/R_1 + 1/R_2$

C1

effective resistance of parallel resistors = 2

C1

3

total resistance = 11 Ω

A1

(c) (i) ratio 2/3 seen/ $V = 4.8$ V used

/clear attempt to find pd across parallel resistors

C1

current = 1.6 A

c.a.o.

A1

4

(ii) use of $P = I^2R$ ($= 2.4^2 \times 11$)

C1

total power = 63.4 W

allow e.c.f. from (b)

A1

[9]

6

(a) (i) 6.0 (Ω) (1)

1

(ii) 4.5 (V) (1)

1

(iii) (use of $I = V/R$)

$I = 4.5/6.0 = 0.75$ (A) (1)

current through cell A = $0.75/2 = 0.375$ (A) (1)

2

(iv) charge = $0.375 \times 300 = 112$ (1) C (1)

2

- (b) cells C and D will go flat first or A and B last longer **(1)**

current/charge passing through cells C and D (per second) is double/more than that passing through A or B **(1)**

energy given to charge passing through cells **per second** is double or more than in cells C and D **(1)** or in terms of power

3

[9]

7

- (a) (for lamp and resistor) $18(\Omega) + 12(\Omega) = 30(\Omega)$ **(1)**

(in parallel) $\frac{1}{30} + \frac{1}{15} = \frac{3}{30}$ **(1)** (gives $R = 10(\Omega)$)

(allow C.E. for wrong value in first step)

total resistance = $\frac{30}{3} + 10$ **(1)**
(= 20 Ω)

3

- (b) (i) (use of $V = IR$ gives) $I = \left(\frac{30}{20}\right) = 1.5$ A **(1)**

(ii) $\text{pd}_{AB} = 30 - (10 \times 1.5)$ **(1)**
 $= 15$ V **(1)**

[or alternative method]

(allow C.E. for value of I from (i))

(iii) $I_{\text{lamp}} = \frac{6}{12} = 0.5$ A **(1)**

[or alternative method] (allow C.E. for value of pd_{AB} from (ii))

4

- (c) (i) (lamp power) ($= I^2 R$) $= 0.5^2 \times 12 = 3.0$ (W) **(1)**
(allow C.E. for value of I_{lamp} from (b) (iii))

- (ii) power from battery = $30 \times 1.5 = 45$ (W) **(1)**
(allow C.E. for value of I from (b) (i))

$$\% = \frac{3 \times 100}{45} = 6.7(\%) \text{ (1)}$$

(allow C.E. for power in lamp and/or battery in (i))

3

[10]

8

- (a) (i) (total) resistance = $(20 + 60)$ (Ω) **(1)**

$$(V = IR \text{ gives}) \quad I = \frac{6.0}{80} = 0.075 \text{ A (1)}$$

- (ii) with S closed, (effective) resistance = 20 (Ω) **(1)**

$$I = \frac{6.0}{20} = 0.3 \text{ A (1)}$$

max 3

- (b) use of same current as in part (i) **(1)**
 voltmeter reading = $0.075 \times 60 = 4.5$ V **(1)**

[or use potentiometer equation $6 \times \frac{60}{80} = 4.5$ V]
(allow C.E. for value of I from (a)(i))

2

[5]

9

- (a) (i) three resistors in series **(1)**
 (ii) $R = 3.0 + 4.0 + 6.0 = 13$ Ω **(1)**
 (iii) three resistors in parallel **(1)**

$$(iv) \quad \frac{1}{R} = \frac{1}{3} + \frac{1}{4} + \frac{1}{6} = \frac{9}{12} \text{ (1)}$$

$$R = 1.3 \Omega \text{ (1)}$$

5

- (b) (i) two resistors in parallel give $\frac{1}{R'} = \frac{1}{3} + \frac{1}{6}$ and $R' = 2.0 \text{ } (\Omega)$ **(1)**
 total resistance = $(2 + 4) = 6.0 \text{ } \Omega$ **(1)**

4

- (ii) divide the emf in the ratio of 2 : 4 **(1)**
 to give 4.0 V **(1)**
 [or any suitable method]

[9]

10

- (a) (i) for X: ($P = VI$ gives) $24 = 12I$ and $I = 2 \text{ A}$ **(1)**
 for Y $18 = 6I$ and $I = 3 \text{ A}$ **(1)**

2

- (b) (i) 12 V **(1)**

- (ii) voltage across R_2 ($= 12 - 6$) = 6 (V) **(1)**
 $I = 3 \text{ (A)}$ **(1)**

($V = IR$ gives) $6 = 3R_2$ and $R_2 = 2\Omega$ **(1)**

(allow C.E. for I and V from (a) and (b)(i))

[or $V = I(R_y + R_2)$ **(1)** $12 = 3(2 + R_2)$ **(1)** $R_2 = 2\Omega$ **(1)**]

- (iii) current = 2 (A) + 3 (A) = 5 A **(1)**
 (allow C.E. for values of the currents)

- (iv) $27 \text{ (V)} - 12 \text{ (V)} = 15 \text{ V}$ across R_1 **(1)**

- (v) for R_1 , $15 = 5 R_1$ and $R_1 = 3\Omega$ **(1)**
 (allow C.E. for values of I and V from (iii) and (iv))

7

[9]

11

- (a) (i) $I = \frac{12}{15} = 0.80 \text{ A}$ **(1)**

- (ii) $P = (0.80)^2 \times 5 = 3.2 \text{ W}$ **(1)** (allow e.c.f. from (a)(i))

(2)

(b) $I_{\text{tot}} = \frac{12}{7.5} \text{ (1)} = 1.60 \text{ (A) (1)}$

$$I = \frac{1.6}{2} = 0.80 \text{ (A) (1) (allow e.c.f. from } I_{\text{tot}})$$

(3)

- (c) same brightness (1)
because same current (1)
[or an answer consistent with their current values]

(2)

[7]

12

- (a) between A and C: (each) series resistance = 100Ω (1)

(parallel resistors give) $\frac{1}{100} + \frac{1}{100} = \frac{1}{50} \Rightarrow$ gives $R_{AC} = 50\Omega$ (1)

2

(allow C.E. for incorrect series resistance)

- (b) between A and B: series resistance = 150Ω (1)

parallel = $\frac{1}{50} + \frac{1}{150}$ (1)

(allow C.E. for series resistance)

$R_{AB} = 37.5\Omega$ (1) (38Ω)

3

[5]

13

- (a) first pair in parallel $\frac{1}{R'} = \frac{1}{30} + \frac{1}{60}$ (1)

$= \frac{3}{60} =$ gives $R = 20 (\Omega)$ (1)

second pair in parallel $\frac{1}{R''} = \frac{1}{40} + \frac{1}{120}$ gives $R'' = 30(\Omega)$ (1)

resistance between A and B = $20 + 30$ (1) (= 50Ω)

(allow C.E. for values of R and R'')

4

- (b) (i) total resistance = $50 + 50 = 100 \Omega$ (1)
 ($V = IR$ gives) $24 = I \times 100$ and $I = 0.24 \text{ A}$ (1)
- (ii) current in $60 \Omega = \frac{1}{3} I$ (1)
 = 0.080 (A) (1)
 [or alternative method]
 (allow C.E. for value of I from (b)(i))

4

[8]

14

- (a) (i) (use of $V = IR$)
 $I = (12-8) / 60 \checkmark = 0.067$ Or $0.066(\text{A}) \checkmark$

2

- (ii) (use of $V = IR$)
 $R = 8/0.067 = 120 (\Omega) \checkmark$

1

- (iii) (use of $Q = It$)
 $Q = 0.067 \times 120 = 8.0 \checkmark \text{ C} \checkmark$

2

- (b) reading will increase \checkmark
 resistance (of thermistor) decreases (as temperature increases) \checkmark
 current in circuit increase (so pd across R_1 increases) OR correct potential divider argument \checkmark

3

[8]

15

- (a) (i) 5 V (1)
 (ii) $R_T = 36 (\Omega)$
 (use of $V = IR$ gives) $15 = I \times 36$ and $I = 0.42 \text{ A}$ (1)

3

- (b) (i) equivalent resistance of the two lamps $\frac{1}{R} = \frac{1}{12} + \frac{1}{12} = \frac{1}{6}$ (1)
 $R_T = 6 + 12 = 18 (\Omega)$ and $15 = I \times 18$ (1) (to give $I = 0.83 \text{ A}$)
- (ii) current divides equally between lamps (to give $I = 0.42 \text{ A}$)
 (or equivalent statement) (1)

3

- (c) same brightness **(1)**
(because) same current **(1)**

2

[8]

16

(a) (i) $\frac{1}{R} = \frac{1}{40} + \frac{1}{40} + \frac{1}{40}$ **(1)**

$$R = \frac{40}{3} = 13.3 \Omega \text{ (1) (13.3)}$$

- (ii) two resistors in parallel give 20 (Ω) **(1)**
 $R = 20 + 40 = 60$ (Ω) **(1)**

max 3

- (b) (i) three resistors in parallel give $\frac{1}{6} + \frac{1}{6} + \frac{1}{6}$ (= 2 (Ω))
and total resistance = 4 (Ω) **(1)**

$$\text{total current} = \frac{12}{4} = 3 \text{ (A) (1)}$$

(allow C.E. for value of total resistance)

current in each element 1.0 A **(1)**

(allow C.E. for value of total current)

[or 6 V across each set
resistance of each set = 2 Ω , gives current through
each set = 3 (A)
current in each element = 1.0 A]
[or 6 V across each set/resistor,
resistance of one resistor = 6 Ω ,
gives current in each element = 1.0 A]

- (ii) six resistors in series gives $R = 36$ (Ω) and $I = \frac{12}{36} = 0.3$ (A) **(1)**

heating effect (I^2R) much reduced [or less power] **(1)**

5

[8]

17

(a)

	total resistance in circuit
X open, Y closed	R (given)
X closed, Y open	$2/3 R$
X open, Y open	$2R$
X closed, Y closed	$R/2$

(b) energy dissipation is V^2/R

or approach using both $I = V/R$ and $P = VI$

B1

highest resistance gives least energy

or X open, Y open or their highest tabulated resistance

B1

2

(c) electrons collide with ions

M1

transferring energy to them/giving them or increasing their vibrational/kinetic energy

A1

2

(d) voltage across load **lower** or load voltage = $\frac{R}{(R+r)}V$

B1

or load current reduced or load current = $\frac{V}{R+r}$

thermal energy output will decrease (in any stated circuit)

or identifies lowest resistance in table as being most affected

M1

since $P = \frac{V^2}{R}$ or since power = $I^2 R$

A1

3

(e) (i) resistance = $\frac{\rho L}{A^2}$ or substitution *or* $A = 1.16 \times 10^{-7} \text{ (m}^2\text{)}$

C1

$1.93 \times 10^{-4} \text{ (m)}$ 0.193mm

A1

(ii) **two** properties from

high resistance/resistivity (low electrical conductivity)

B1

high melting point

B1

low thermal capacity/specific heat capacity

B1

4

[14]

18

(a) (i) voltage = $0.01 \times 540 = 5.4 \text{ V (1)}$

1

(ii) voltage = $15 - 5.4 = 9.6 \text{ V (1)}$

1

(iii) (use of resistance = voltage/current)

$$\text{resistance} = 9.6/0.01 \text{ (1)} = 960 \Omega \text{ (1)}$$

$$\text{or } R_T = 15/0.01 = 1500 \Omega \text{ (1)}$$

$$R = 150 - 590 = 960 \Omega \text{ (1)}$$

or potential divider ratio (1)(1)

2

(iv) (use of $1/R = 1/R_1 + 1/R_2$)

$$1/960 = 1/200 + 1/R_2 \text{ (1)}$$

$$1/R_2 = 1/960 - 1/200$$

$$R_2 = 4800 \Omega \text{ (1)}$$

2

(b) (voltage of supply constant)

(circuit resistance decreases)

(supply) current increases or potential divider argument (1)

hence pd across 540 Ω resistor increases (1)

hence pd across 1200 Ω decreases (1)

or resistance in parallel combination decreases (1)

pd across parallel resistors decreases (1)

pd across 1200 Ω decreases (1)

3

[9]

19

(a) so that each lamp is connected directly across the battery (1)

if one lamp blows others are still on (1)

2

(b) use of $power = VI$ (1)

$$\text{current through each headlight} = 60/12 = 5.0 \text{ A}$$

$$\text{or current through each tail light} = 8/12 = 0.67 \text{ A (1)}$$

$$\text{total current} = 2 \times 5.0 + 2 \times 0.6667 = 11(.3) \text{ A (1)}$$

3

(c) the lamp with the highest power rating has the least resistance **(1)**

the resistance is greater because the temperature of the filament is lower **(1)**

and resistance increases with temperature **(1)**

3

(d) (i) (use of energy = power × time)

energy dissipated = $(8.5) \times 2 \times 12 \times 3600$
(any power × time) **(1)**

energy dissipated = $1.1(2) \times 10^6$ J **(1)**

2

(ii) stored energy in battery =

$12 \times 1.2 \times 24 \times 3600 = 1.24 \times 10^6$ **(1)**

energy to start = $12 \times 100 \times 1 = 1200$ J **(1)**

energy left = $(1.24 - 1.12) \times 10^6 = 120\,000$ J
so hence car will start **(1)**

(conclusion assuming all working correct)

3

[13]

20

(a) (i) no of bulbs = $\left(\frac{230}{5}\right) = 46$ **(1)**

(ii) (use of $P = VI$ gives) $I = \left(\frac{0.4}{5}\right) = 0.080$ A **(1)**

(iii) resistance of each bulb = $\frac{230}{0.080 \times 46} = 63 \Omega$ (62.5 Ω)

(allow C.E. for number of bulbs and value of I)

[or $R \left(\frac{V}{I}\right) = \frac{5}{0.08} = 62.5 \Omega$

or $\left(P = \frac{V^2}{R} \text{ gives}\right) R = \frac{25}{0.40} = 62.5 \Omega$

5

(iv) energy consumed by the set = $0.4 \times 46 \times (2 \times 60 \times 60)$ **(1)**
 = 132 kJ **(1)**
 (allow C.E. for number of bulbs from (i))

(b) (i) no of bulbs = 56, gives total resistance = 62.5×56 (Ω) (= 3500) **(1)**

$$I = \frac{230}{3500} = 0.066 \text{ A (1) (0.0657 A)}$$

(use of 63 Ω gives 0.065 A)

(allow C.E. for no. of bulbs in (a) (i) and R in (a) (iii))

(ii) bulbs would shine less bright **(1)**

3

[8]

21

(a) (i) $P = V^2/R$ with substitution: 144/any resistance

C1

37.9 (W)

A1

2

(ii) use of $1/R$ formula with substitution of some data
 even if not all five resistors

C1

correct calculation of $1/R$ (giving 0.897)

C1

1.11 (Ω)

A1

3

(iii) 144/their aii

C1

129 to 131 (W) **ecf**

A1

2

(b) lower resistance needed

B1

(to achieve) higher current (for I^2R to be the same)/
correct use of V^2/R

B1

2

[9]

22

(a) (i) (use of $P=VI$)

$$I = 36/12 + 6/12 \checkmark = 3.5 \text{ (A)} \checkmark$$

2

(ii) (use of $V=IR$)

$$R = 12/3 = 4 \text{ (}\Omega\text{)} \checkmark$$

1

(iii) $R = 12/0.50 = 24 \checkmark \text{ (}\Omega\text{)}$

1

(b) terminal pd/voltage across lamp is now less OR current is less \checkmark

due to lost volts across internal resistance OR due to higher resistance \checkmark

lamps less bright \checkmark

3

(c) (i) current through lamps is reduced as resistance is increased **or**
pd across lamps is reduced as voltage is shared \checkmark

hence power is less OR lamps dimmer \checkmark

2

(ii) lamp Q is brighter \checkmark

lamp Q has the higher resistance hence pd/voltage across is greater \checkmark

current is the same for both \checkmark

hence power of Q greater \checkmark

3

[12]

23

(a) potential divider formula used or current found to be 0.25 A

C1

A1

allow 1 s.f.

2.0 V

1.0 V (with working) gains 1 mark

2

(b) main current = $1.2 \text{ V} / 4 \Omega = 0.3 \text{ (A)}$

C1

$R_{\text{total}} = 1.8 \text{ V} / 0.3 \text{ A} = 6 \Omega$ or $I_b = 0.225 \text{ (A)}$

C1

$R_v = 24 \Omega$

A1

3

[5]

24

(a) $I_3 = I_1 + I_2 \checkmark$

1

(b) 10 V \checkmark

1

(c) $I_2 = (12 - 10) / 10 \checkmark$

Allow ce for 10 V

1

= 0.2 A \checkmark

The first mark is for the pd

The second is for the final answer

1

(d) pd across R_2 increases

As R_1 increases, pd across R_1 increases as $\text{pd} = I_1 R_1 \checkmark$

First mark is for identifying that pd across R_1 increases (from zero).

1

pd across $R_3 = 10 \text{ V} - \text{pd across } R_1$

Therefore pd across R_3 decreases \checkmark

Second mark is for identifying that pd across R_3 must decrease

1

pd across $R_2 = 12 - \text{pd across } R_3$

Therefore pd across R_2 increases ✓

Third mark is for identifying that this means pd across R_2 must increase

1

[7]

25

Correct substitution into $P=VI$

1.74 (A)

2

(b) (i) Correct substitution into $R=V/I$ or V^2/P or P/I^2
264 (Ω)

Allow correct use of parallel resistor equation

2

(ii) Use of $1/R_T = 1/R_1 + 1/R_2$ or $R = V^2/P$
65 (66.1) (Ω)

2

(iii) $A = \pi(1.5 \times 10^{-4})^2/4$ or $\pi(7.5 \times 10^{-5})^2$ or 1.767×10^{-8} (m^2)
Substitution into $l=RA/\rho$ with their area
4.2 (4.18) (m)

2 marks for 17 (m), using of d instead of r

3

(c) Resistivity / resistance increases with increasing temperature
(Lattice) ions vibrate with greater amplitude
Rate of movement of charge carriers / electrons (along wire)
reduced (for given pd)

ORA

Condone atoms for ions.

Accept "vibrate more".

*Accept more frequent collisions occur between electrons and ions
owtte*

3

(d) $2.9 \times 10^{-3}/447$ or $2.9 \times 10^{-3}/174$ seen

6.5 (6.49) $\times 10^{-6}$ (m)

Correct answer given to 2 sig fig

Condone use of 174 for T for C1 and B1 marks

Allow 3 sig fig answer if 2.90×10^{-3} used

3

[15]

Examiner reports

2

This question proved to be very discriminating with only the high performing candidates able to score high marks. The calculations involved in part (a) proved to be straightforward and the majority of candidates realised that this was 5.0Ω . Part (a)(ii) caused more problems and there were many answers in which the calculation of the resistance of the parallel component was spoilt by poor setting out – equating $\frac{1}{2}$ to 2Ω was a common occurrence.

Part (b) required candidates to calculate currents in the parallel branches of the circuit. Many tried to do this by ratio and got the currents the wrong way round, ie quoting a value of 0.67 A instead of the correct 1.3 A . A more successful approach, used by more able candidates, involved the calculation the pd across the series resistor and hence the deduction of the pd across Y. Once this was known the current in Y could be correctly calculated. This approach also enabled candidates to give the correct pd across W because they realised it was half the value of the pd they had already calculated for Y.

3

Part (a) was, in general, very well done with the mathematical manipulation of three resistors in parallel posing a problem to only a handful of candidates. There were many attempts however where the candidates did not seem sure of the expression and had the four resistors in parallel, or, more frequently, considered the 50Ω to be in series with $1 / R_t$, where R_t was the sum of the three parallel resistors.

In contrast to part (a), part (b) gave very poor results with some 50% of the candidates failing to gain the allocated mark. The common error was giving the current as $I = 12 / 50$ i.e. ignoring the equivalent resistance of the three parallel resistors. This showed a very poor understanding of the dc circuit.

4

Part (a) was answered well, with many candidates obtaining full marks.

Part (b) caused more problems and the use of the power formula that involves potential difference and resistance was quite rare. In part (b) (ii) there was some confusion over potential difference and candidates frequently used their answer from part (b) (i). Part (b) (iii) was answered much better, with candidates frequently benefiting from consequential error.

5

(a) Fewer than half of the candidates were able to fully define electrical resistance.

(b) This was answered correctly by most. Those who did go wrong usually demonstrated a weakness in mathematics rather than in physics.

- (c) This part was generally not answered well.
- (i) Only the more able candidates were able to correctly answer this part.
 - (ii) Even with errors carried forward from part (i), only a few more candidates gained full marks for this question.

6 The majority of candidates seemed to approach this question with confidence and set out their working well. Many did not appreciate the effect of connecting the two identical cells in parallel and it was quite common to see them using the combination of parallel resistors formula to combine the emfs of the two cells. This was something that was not confined to the less able candidates but was seen across the full ability range. This was not a heavy penalty as subsequent answers received full credit whatever value candidates had deduced for the total emf.

Part (a) (iv) assessed the unit for charge and the majority of candidates had no problems with this.

The deduction required for part (b) proved quite discriminating and only the very best candidates obtained all three marks. The first mark for identifying cells C and D proved quite straightforward but the explanation less so. Many candidates appreciated that the greater current in the cells in series was significant but were unable to take this to the next step and link this with the rate of energy dissipation.

7 This question proved to be very accessible and full marks were gained frequently. It is worth, however, pointing out a few recurring errors. In part (a), because the answer was given, it was expected that candidates would show full working. Very often the final expression would contain $10Q$, being added in series to the product of the parallel

arrangement, the parallel resistance still being in the mathematical form $\frac{1}{R_1} + \frac{1}{R_2}$ etc.

Because it was so easy to deduce that the parallel section was equivalent to 10Ω , examiners did expect to see the value being worked out from the basic expression, otherwise a mark would be deducted.

In part (b) the first two calculations were usually correct, but the third part often produced wrong answers, 1.25 A appearing quite frequently. Part (c) produced many correct answers, with candidates being quite familiar with calculations for power and being able to calculate the percentage.

8 The majority of candidates found this question straightforward and gained the maximum number of marks. Others, however, were not sure of the effect on the circuit of having the switch open or closed. A considerable number of candidates reversed the calculations for parts (a) (i) and (ii). Several candidates, in the situation when the switch was closed, i.e. effectively shorting out the 60Ω , resorted to adding up the two resistances using the expression for parallel resistors.

In part (b) the majority of candidates realized that a voltmeter of infinite resistance had the same effect on the circuit as an open switch and proceeded accordingly.

9 This is the first time in these series of examinations that candidates have been required to draw their own arrangement of resistors. The majority of candidates gave the correct answers in part (a), although some did try an arrangement of resistors similar to that in part (b). There were a few incorrect calculations in part (a) (ii) even though the three resistors were in series. The usual error in part (iv) was calculating correctly the value of VR but then forgetting to invert to obtain R .

In part (b) the calculation for the total resistance was usually correct although there was some concern amongst the examiners to see the expression $R_T = \frac{1}{3} + \frac{1}{6} + 4$ occurring quite frequently.

Invariably this resulted in the wrong answer, because candidates would not invert the value for the parallel resistors. The occurrence of this 'system' of calculating resistance was brought to the attention of teachers in the last report, but it seems to be more common than before. Part (ii) was not answered well, with candidates just writing numbers down without any reasoning and in the end confusing themselves. Candidates who just gave an answer of 4 V with no working shown were not credited, because it was possible to obtain that answer by incorrect physics. Candidates should be trained to give some explanation of what they are attempting in such calculations. It was also sad to see candidates obtaining the (correct) answer of 4.0 V across the parallel resistors, but then shooting themselves in the foot by assuming that the voltage across the 6.0Ω was different to that across the 3.0Ω .

10 This question involved the analysis of a relatively difficult circuit, which included two lamps and two resistors. The question however, was so structured that the majority of candidates were able to work through and gain full marks. Others, unfortunately, although making a reasonable attempt, failed to gain many marks. In part (a), the majority of candidates calculated the correct value of the currents passing through each lamp.

In part (b), obtaining the correct answers to parts (i) and (ii) depended to a large extent on realising that the reading on the voltmeter equalled the voltage across lamp X. Many candidates missed this point, but were still able to gain some marks. In part (ii) the error that was committed regularly was determining the resistance of lamp Y instead of the resistance of resistor R_2 . But at least, more candidates realised that the same current passed through lamp Y and R_2 . Answers to parts (iii) and (iv) used the answer to part (a) as a starting point, but many candidates failed to realise that the current through R_1 was the sum of the current through the two lamps. Considerable guesswork took over at this stage and although most of it was wrong, candidates could still get a mark for part (v) by using the answers obtained to parts (iii) and (iv).

12 In this example of calculating equivalent resistance, the same resistor network was used twice, the equivalent resistance being calculated between different terminals. The majority of candidates had no difficulty with the calculations, but it was worrying to find many answers where the candidates had attempted a solution, not by calculation, but with phrases such as “electricity takes the path of least resistance and therefore the effective resistance (in part (b)) is 50Ω .”

It was surprising to find that a significant number of candidates obtained the correct result in part (b) but failed on part (a), since part (b) was deemed to be the most difficult of the two. Considerable arithmetical difficulty was encountered by many candidates with the reciprocal of the resistance when calculating the resistance of parallel resistors.

13 Part (a) was the calculation of the equivalent resistance of a network of resistors consisting of resistors connected in series and in parallel. The majority of candidates gained full marks on this section and were not troubled by the calculation. However, it is worth pointing out that since the final answer of 50Ω was given in the question, then in order to gain full marks it was necessary to show that the two equivalent series resistors were being added together.

Part (b) did not prove to be as easy; the problem in (i) was that many candidates gave the total resistance as 50Ω rather than 100Ω . No consequential error for calculating the current was allowed and frequently no marks were awarded for this section. It was possible in part (b)(ii) to gain the two marks even if the answer to (i) was incorrect, but very few candidates managed to gain these marks. The usual error was giving the current in the circuit as $24/20$, i.e. ignoring the second batch of parallel resistors. Again, many candidates, having calculated the total current correctly, assumed that $2/3$ would pass through the 60Ω resistor, not realising that the greater the resistor, the lower the current for a given voltage.

14 The majority of students were able to analyse the circuit correctly although surprisingly a significant minority had problems with (a)(i) because they did not appreciate that the pd across R_2 was 4.0 V. This did not affect their subsequent responses however, as the answer they gave was carried forward to subsequent calculations. The qualitative aspect of the question presented students with a greater challenge. Many incorrectly stated that the voltmeter reading would decrease as the thermistor resistance falls seemingly forgetting that the voltmeter was connected across R_1 .

15 The question involved straightforward calculations on voltage, resistance and current. In part (a)(i) it was hoped that candidates would have spotted the correct voltage across each lamp by inspection. Surprisingly, even those who managed to get the wrong answer in part (i) nevertheless ignored their answer and proceeded from first principles to obtain the correct answer to part (ii).

Part (b) involved the same circuit components as in part (a) but connected differently. The majority of candidates showed that the current from the battery was the value given in the question. Using this value they then proceeded to argue or calculate the current in each lamp. Those candidates who merely halved the current value obtained in part (i) without any reasoning did not gain the mark.

Although the question told the candidates that the current through each lamp was the same in both circuits it was disappointing to find in part (c) how many candidates tried to argue that the brightness of the bulbs in the 2nd circuit would be different to that in the first, the main thrust of their argument being that the voltage across each bulb was different and therefore that the brightness would be different.

16 Candidates are by now well used to questions on resistors in series and in parallel and part (a) contained no hidden terrors. Invariably, correct answers were gained for both circuits. Examiners are concerned however at the trend of using an unusual nomenclature for a combination of resistors in series and in parallel, e.g. the combination of resistors in the second circuit would be given by candidates in some

centres as $R_T = \frac{1}{40} + \frac{1}{40} + 40$. The fact that they subsequently gave the correct

answer of 60Ω showed that the candidates had worked out the parallel section first and then added the series section. Such a system is not to be encouraged since it serves to confuse and if a wrong answer is given, it does not help the examiner to find out where the error occurred and then perhaps award a consequential error mark. The other point concerning this section, was that answers to part (i) were given in many instances as $13\frac{1}{3} \Omega$ or 13.3Ω (i.e. recurring). These were treated as significant figure errors. Answers given as fractions are not accepted.

Part (b) was more difficult and many candidates failed to understand the physics of the circuit. Comparatively few candidates gained full marks. An error which cropped up continually in part (i) was correctly calculating the resistance of three resistors in parallel (2Ω) but then using 12 V to calculate the current, not realising that the effect of the other three resistors halved the pd. There were also many candidates who calculated the correct current from the supply, but split this equally between the six resistors and not three. In part (ii), although most candidates calculated the current as 0.33 A and thus correctly concluded that the current was less than that in the part (i), they failed to capitalise on this and merely said that 'therefore the heater was less effective'. In order to gain the final mark it was necessary to mention the heat/power generated by the current.

17

Many were unable to identify which resistors were in the circuit for different switch settings and then calculate the total resistance in part (a). The $2R$ value was most easily identified but only about 20% of the candidates obtained credit for the other switch settings. Some could correctly write down the equations for calculating resistors in parallel but then got no further.

Part (b) was not done well. Few appreciated that they need to use V^2/R and not I^2R because potential difference was the common factor for each setting and not current.

Part (c) exposed many misconceptions about charge flow through conducting material. Many thought thermal energy to be produced by electrons bumping into each other or that they excite atoms which then release the energy as heat. Some thought the nuclei of atoms in the conducting material to be involved.

In part (d) a good proportion of the candidates appreciated that the thermal energy output would be decreased and, although there were some very good answers, many went on to give a partial explanation of why this would happen in terms of the reduced pd across the load or a reduced load current.

There were many correct answers to part (e) (i), but it was disappointing that a quarter of the candidates were unable to make any progress with the calculation.

A majority could give at least one sensible property in part (e) (ii), but many candidates had clearly confused the rod with the resistance wire so gave properties that were 'opposite' to those needed or irrelevant properties. Some gave contradictory properties such as 'it must have a low resistivity and be a good conductor'.

18

This question proved to be very discriminating with only the more able candidates able to score high marks. The calculations involved in part (a) proved too challenging for many candidates. Part (a) (i) and (ii) generated the most correct responses, but the remainder of the analysis was only accessible to the more able candidates.

Part (b) required analysis without calculation and the majority of explanations seen were confused and not self consistent. Many candidates stated that more current goes through the thermistor and therefore the pd across it falls, resulting in the pd across the parallel $1200\ \Omega$ resistor increasing. Another common misunderstanding was the effect that the decreasing thermistor resistance had on the current through the battery. Many thought that the current remained constant and, although this still led them to deduce that the pd fell, their arguments frequently contained contradictions.

20

All candidates were able to gain a reasonable number of marks for this question, and many were awarded full marks. The answer to part (a) (i) was usually correct, but there were some problems with part (a) (ii). The most common error was obtaining the correct value of the current in the circuit, as required, but then dividing this value by the number of lamps. The resistance of each lamp, in part (iii), was usually calculated correctly, although some candidates made heavy weather of the calculation when using the expression VIR for power. Several recurring errors in part (iv) resulted in this part not being answered as well as the others. These errors would be calculating the energy used by one lamp instead of by the set, or omitting the factor of 2 (hours) when calculating the number of seconds, or omitting the conversion from minutes into seconds.

Incorrect answers in part (a) were allowed to be carried forward into part (b), which resulted in part (b) performing quite well. The usual error in part (i) was carrying out the calculations for 10 lamps, instead of 56. Answers to part (ii) were usually correct, candidates realising that the greater the current, the greater the brightness.

21

Almost all of the candidates correctly calculated the power of a headlight lamp. A very few extracted an incorrect value of resistance from the table. In part (a)(ii), candidates made the usual errors of using the resistors in series formula instead of resistors in parallel. Others omitted to invert their answer once they had calculated the sum of the reciprocals of the five resistors. In part (a)(iii), some candidates revisited their part (a)(i) type calculations to find the powers of all of the lamps, rather than using the overall resistance value that they had just calculated.

In part (b), most candidates realised that, in this circumstance, lamps of lower resistance ought to be used. Candidates' justifications were not always convincing. The best answers referred to the equation relating power to voltage and resistance. Some argued that lower resistances should be used so that the current would increase, this was acceptable. What was not acceptable was the argument that it was necessary to restore the current to its previous value.

22

The quantitative parts of this question were well answered but as is often case, students found the qualitative aspect the much more challenging. The calculations of current and resistance caused few problems and the majority of students were able to explain the effect of an appreciable internal resistance. Part (c) caused far more problems and a significant proportion could not convincingly explain why the lamps were not at normal brightness when connected in series. They seemed not to appreciate that the voltage of the 12 V battery was divided between the lamps or that the circuit resistance is higher when the lamps are in series. They also found it very difficult to explain which lamp was brighter – many incorrectly assuming that it was lamp P as it had a higher power rating.

23

The majority of candidates correctly calculated the voltage in (a). Many used the same current as in (a) to do the calculation in (b); dividing the difference in the voltage across the resistor [between (a) and (b) = 0.2 V] by the current in (a) to give 0.8Ω was a very common incorrect answer. Only a few candidates were able to perform the complete calculation to obtain a resistance of 24Ω .

25

- (a) Most students obtained the total current but failed to appreciate the need to halve this value.
- (b) A variety of routes were possible for part (i) but clear evidence of the method was expected to be seen. The 'parallel resistor' equation was often invoked but rarely written explicitly. Parts (ii) and (iii) were answered well.
- (c) This was poorly answered. Explanations often lacked the required precision. Many students clearly thought that nichrome is a semi-conductor.
- (d) Most students recognised the need to use Wien's Law and to convert the temperature to kelvin.