

Marking Scheme

#1

Question			Marking details	Marks available				Maths	Prac
				AO1	AO2	AO3	Total		
1	(a)	(i)	Resistance of LDR / circuit increases [as light intensity decreases] (1) [Hence] current decreases (1)	2			2		2
		(ii)	Either: $\text{Current in LDR} = \frac{4.0}{2.4 \times 10^3} = [1.67 \times 10^{-3} \text{ A}] \text{ (1)}$ $R = \frac{5.0(1)}{1.67 \times 10^{-3}}$ $R = 3.0 \text{ k}\Omega \text{ (1)}$ Alternative: $4.0 = \frac{2.4 \times 10^3 \times 9.0}{(2.4 \times 10^3 + R)} \text{ (1) [substitution into potential divider equation]}$ Correct algebra (1) $R = 3.0 \text{ k}\Omega \text{ (1)}$ Alternative: $\frac{4}{5} = \frac{2.4}{R}$ $R = 3.0 \text{ k}\Omega \text{ (1)}$	1	1	1	3	2	3
	(b)		Light from lamp will decrease [LDR resistance and hence] V across lamp low so lamp not activated (1) Hence reason for on/off, e.g. lamp off \rightarrow LDR in dark \rightarrow V_{out} high \rightarrow lamp on		2		2		2
			Question 1 total	3	4	0	7	2	7

#2

Question			Marking details	Marks available				Maths	Prac
				AO1	AO2	AO3	Total		
2	(a)		There are 6 J of energy/work done (converted from electrical to other forms) (1) Per coulomb of charge between X and Y (1)	2			2		
	(b)	(i)	Attempt to use equation to determine resistors in parallel (1) Resistance of parallel combination = $3.7[2] \Omega$ (1) Total circuit resistance = 9.3Ω ecf on parallel (1) Current = $\frac{V}{R} = 0.64 \text{ A}$ [accept 0.65 A] answer to 2 d.p. (1)	1	1	1	4	3	
		(ii)	Apply ecf from part (b) (i) PD across parallel = 0.65×3.7 ecf OR pd across $5.6 \Omega = 0.65 \times 5.6 = 3.6 \text{ V}$ (1) Answer = 2.4 V (1)		2		2	1	
		(iii)	Substitute values into $P = I^2 R$ [$P = 0.65^2 \times 3.7$] (1) $P = 1.54 \text{ W}$ – ecf (1)	1	1		2	2	
			Question 2 total	4	6	0	10	6	0

#3

Question	Marking details	Marks available					
		AO1	AO2	AO3	Total	Maths	Prac
6 (a)	capacitance = $\frac{\text{charge (on either plate)}}{\text{pd (between the plates)}}$ Accept charge per unit pd / voltage [between plates] (1) Accept $C = \frac{Q}{V}$ if Q and V defined	1			1		
(b) (i)	$Q = -75 \text{ nC}$, $R = +75 \text{ nC}$, $S = -75 \text{ nC}$ All numerical values stated as 75 [nC] (1) Correct signs and unit, i.e. nC (1) One of: (1) <ul style="list-style-type: none"> Capacitors in series carry equal charges when joined to common pd Conservation of charge applies for series circuit [hence if +75 μC moves from A to plate P, the same moves from Q \rightarrow R etc] Opposite charge to P (accept R), since connected to negative potential [Accept: battery transfers electrons from P to Q] 	3			3		
(ii)	Total capacitance = 7.5 nF (1) $V = \frac{75 \times 10^{-9}}{7.5 \times 10^{-9}}$ (ecf on total C) $V = 10 \text{ V}$ (1) Alternative: Application and substitution into $\frac{Q}{C_1} + \frac{Q}{C_2}$ i.e. $\frac{75 \times 10^{-9}}{30 \times 10^{-9}} + \frac{75 \times 10^{-9}}{10 \times 10^{-9}}$ (1) $V = 10 \text{ V}$ (1)		2		2	2	
(iii)	Either: Q same on both capacitors (1) $\frac{1}{2} \frac{Q^2}{C}$ is bigger on smaller capacitor (1) (Award 2 marks for correct numerical analysis) Or: $V \propto \frac{1}{C}$ so V bigger across smaller capacitor (1) $\frac{1}{2} CV^2$ bigger across smaller capacitor (V^2 factor) (1) (Award 2 marks for correct numerical analysis) Or Q same on both capacitors and $V \propto \frac{1}{C}$ so V bigger across smaller capacitor (1) $\frac{1}{2} QV$ is bigger on smaller capacitor (1) (Award 2 marks for correct numerical analysis)			2	2		
(c)	New $C = 0.47 \text{ pF}$ (1) New $d = 3.0 \times 10^{-3} \text{ m}$ (1) $\Delta d = 5.2 \times 10^{-3} - 3.0 \times 10^{-3} = 2.2 \times 10^{-3} \text{ m}$ (1) (ecf from new d) Application of $F = k\Delta d$ ecf $k = 91 \text{ N m}^{-1}$ so spring of $k = 90 \text{ N m}^{-1}$ suitable [conclusion consistent with value of F](1) Alternative 'Trial and Error' : Application of $x = \frac{F}{k}$ for each spring constant, showing that for: $k = 120 \text{ N m}^{-1}$, $x = 1.67 \times 10^{-3} \text{ m}$ $k = 150 \text{ N m}^{-1}$, $x = 1.33 \times 10^{-3} \text{ m}$ $k = 90 \text{ N m}^{-1}$, $x = 2.22 \times 10^{-3} \text{ m}$ (All required for 1) New $C = 0.47 \text{ pF}$ (1) Application of $C = \frac{\epsilon_0 A}{d}$ for each value of x above to show that, for $x = 2.22 \times 10^{-3} \text{ m}$, $C = 0.475 \times 10^{-12} \text{ F}$, so $k = 90 \text{ N m}^{-1}$ suitable. (1)			4	4	3	
Question 6 total		4	2	6	12	5	0

#4

Question	Marking details	Marks available				Maths	Prac
		AO1	AO2	AO3	Total		
(a)	<u>Electrical energy</u> (or work) <u>transferred</u> [to other forms] <u>per unit</u> [<u>accept coulomb</u>] of <u>charge</u> [passing between the two points]	1			1		
(b)	<p>Either: I in circuit = $\frac{2.4}{160}$ (1) [= 15.0 mA]</p> <p>$R_{\text{Thermistor}} = \frac{(12.0 - 2.4)(1)}{15.0 \times 10^{-3}}$ [ecf on I]</p> <p>= 640 $[\Omega]$ (1)</p> <p>Or: $R_T = \frac{9.6(1)}{2.4} \times 160$ (1) or $2.4 = \frac{12 \times 160}{160 + R_T}$ (2)</p> <p>= 640 $[\Omega]$ (1)</p>	1	1		3	3	
(c)	(i) [Resistance of thermistor decreases as temp increases] pd across thermistor decreases (1) So pd across fixed resistor increases because: Either - ratio of pds across potential divider changes Or - total pd must = 12.0 V (or equivalent) (1) Alternative: [Resistance of thermistor decreases as temp increases] so circuit current increases (1) So pd across fixed resistor increases because $V = IR$ and R is constant or $V \propto I$ (1)		2		2		
	(ii) At 30 °C, $R_{\text{thermistor}} = 480 \Omega$ from graph (1) $V_{\text{cooling system}} = \frac{160}{(480 + 160)} \times 12.0$ (1) [ecf on $R_{\text{Thermistor}}$] = 3.0 [V] (1) Alternative: $2.8 = \frac{160}{(R_{\text{Thermistor}} + 160)} \times 12.0$ (1) $R_{\text{Thermistor}} = 526 [\Omega]$ (1) Corresponds to 25 °C from graph (1) Alternative: $I_R = \frac{2.8}{160} = 0.0175$ [A] (1) $R_T = \frac{9.2}{0.0175} = 526 [\Omega]$ (1) Corresponds to 25 °C from graph (1) Alternative: $I_R = \frac{2.8}{160} = 0.0175$ [A] (1) At 30 °C, $R_{\text{thermistor}} = 480 \Omega$ from graph (1) $I_T = \frac{9.2}{480} = 0.0192$ [A] (1) Alternative: At 30 °C, $R_{\text{thermistor}} = 480 \Omega$ from graph (1) $I = \frac{V}{R} = \frac{12}{(480 + 160)} = 0.01875$ [A] (1) $V = IR = 0.01875 \times 160 = 3$ [V] (1) Final mark for all methods - Valid conclusion consistent with answer: i.e. Claim incorrect - system activated at $\theta < 30^\circ\text{C}$ (1)				4	4	3
(d)	More effective at 0 °C – 10 °C (no mark) Because: Steeper gradient / larger change in resistance (1) Greater sensitivity in this range / greater [fractional] change in R per °C change in temperature or over the same temperature range) (1)			2	2		2
	Question total	2	4	6	12	6	2

#5

Question	Marking details		Marks available						
			AO1	AO2	AO3	Total	Maths	Prac	
1	(a)	<p>I - Energy (per coulomb or unit charge) used in external resistor/circuit [1] E - Energy (per coulomb/unit charge) transferred by source [or from chemical energy or from other forms] or used in whole circuit [1] Ir - energy (per coulomb/unit charge) wasted/lost in source or due to internal resistance [1] Use of 'per coulomb' or 'unit charge' at least once [1]</p>	4			4			
	(b)	(i)	<p>Circuit current = $\frac{1050 \times 10^{-3}}{2.5} = 0.42$ [A] [1] Total internal resistance = $\frac{0.5}{0.42} = 1.2$ [Ω] ecf on I [1] $r_{\text{cell}} = 0.6$ [Ω] [1]</p>		3		3	2	
		(ii)	<p>Substitution into $I^2 r t$ i.e. $(0.42)^2 \times 0.6 \times 60$ (ecf on I, r) [1] Alternative: Substitution into $\frac{I^2 t}{r}$ i.e. $\frac{(0.25)^2 \times 60}{0.6}$ (ecf on I, r) Alternative: Substitution into It^2 i.e. $0.42 \times 0.25 \times 60$ (ecf on I, I) Energy dissipated = 6.3 [J] [N.B. Alternative \rightarrow 6.4 J] [1]</p>	1					
	(c)		<p>Either: Total resistance of coils in parallel = 2.975 [Ω] [1] and total circuit resistance = 4.175 [Ω] ecf [1] New current in circuit = $\frac{3}{4.175} = 0.72$ [A] [1] For the 4th mark: Rate of energy dissipation in each cell = $(0.72)^2 \times 0.6 = 0.31$ [W] so Kiera correct (or ratio calculated to be approx. 3) Or Energy dissipated in each cell in one minute = $(0.72)^2 \times 0.6 \times 60 = 18.6$ [J] so Kiera correct (or ratio calculated to be approx. 3) [1] Alternative: Total resistance of coils in parallel = 2.975 [Ω] [1] and total circuit resistance = 4.175 [Ω] ecf [1] New current = 0.72 [A] and pd drop across internal resistance = $0.72 \times 1.2 = 0.86$ [V] [1] Rate of energy dissipation in each cell For the 4th mark: = $\frac{(0.43)^2}{0.6} = 0.31$ [W] so Kiera correct (or ratio calculated to be approx. 3) Or Energy dissipated in each cell in one minute = $\frac{(0.43)^2 \times 60}{0.6} = 18.6$ [J] so Kiera correct (or ratio calculated to be approx. 3) [1]</p>			4	4		
			Question 1 total	5	4	4	13	3	0

#6

Question		Marking details	Marks available				Maths	Prac
			AO1	AO2	AO3	Total		
	(a)	Label axis with units and suitable scale (1) Plot all points correctly $\pm \frac{1}{2}$ small square division (1) Draw a smooth curve with maximum between 2.3 and 2.6 Ω no straight lines present (no requirement to extend back to the origin) (1)	1	1		3	3	3
	(b)	(i) 6.0 [J] of [chemical] energy transferred/converted/work done to electrical [potential] energy (1) Per unit charge [or coulomb] [flowing through the cell/battery] (1)	2			2		2
		(ii) Using $P = I^2 R$ (1) Data point from graph when $R = 4.5 \Omega$, $P = 3.64 \text{ W}$ (1) Need 2 dp and within $\pm \frac{1}{2}$ small square Calculation of current correctly i.e. = 0.90 [A] (1)	1	1		3	3	3
		(iii) Using $E = V + Ir$ (1) Substituting correct values $6 = 0.90 \times 4.5 + 0.90r$ ecf (1) Internal resistance = 2.2 [Ω] (1)	1	1		3	3	3
	(c)	Power is <u>higher/greater/larger</u> (1) Total resistance of circuit is less for <u>all values of R</u> (1) Accept peak of graph shifts to left			2	2		2
		Question total	5	6	2	13	9	13

#7

Question	Marking details			Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
2	(a)	(i)	Rate of charge flow Accept $I = \frac{\Delta Q}{\Delta t}$ only if ΔQ and Δt defined [accept Q and t]	1			1		
		(ii)	J C ⁻¹ and C s ⁻¹ as units of V and I respectively clearly shown (1) Correct division seen i.e. $\frac{JC^{-1}}{Cs^{-1}}$ seen (1) Or from alternative correct expression, e.g. $R = \frac{V^2}{P}$ Or equivalent in terms of quantities.	1	1		2	1	
	(b)	(i)	I through $R_p = 1.2 A$ and I through $R_T = 0.8 A$ (1) $\frac{V_p}{V_T} = \frac{1.2R_p}{0.8R_T}$ (=1.5) seen (1) Or Parallel combination calculated as $\frac{2}{3}R$ (1) Potential divider: $\frac{R}{R + \frac{2}{3}R} \times 9 = 1.5$ (1)		2		2	1	
		(ii)	$2.5V_T = 9.0$ or $\frac{5V_p}{3} = 9.0$ (1) $V_T = 3.6 V$ or $V_p = 5.4 V$ (1) Award 2 marks for either V_p or V_T calculated correctly. $R_T = \frac{3.6}{0.8} = 4.5 \Omega$ or $R_p = \frac{5.4}{1.2} = 4.5 \Omega$ or $\frac{1.8}{0.4} = 4.5 \Omega$ (1) Alternative: Total circuit $R = \frac{9.0}{1.2} = 7.5 \Omega$ (1) Parallel and series combination shown to be = $\frac{5R}{3}$ (1) $\frac{5R}{3} = 7.5$ and $R = 4.5 \Omega$ (1) Alternative: Understanding that $V_p + V_T = 9$ (1) $1.2R_p + 0.8R_T = 9$ (1) (award 2 marks for this only) $R_p = R_T = R$ and $R = \frac{9}{2} = 4.5 \Omega$ clearly shown (1) Accept reverse argument.		3		3	3	
	(c)		P (circuit) = 10.8 W (1) (either $\frac{81}{7.5}$ or $(1.2)^2 \times 7.5$ or 1.2×9) P in $R_0 = (0.4)^2 \times 4.5 = 0.72 W$ (1) $\frac{10.8}{0.72} = 15$ seen (1) Alternative: $P_s = P_0$ since $I_s = I_0$ $P_T = 4 \times P_0$ since $I_T = 2 \times I_0$ $P_p = 9 \times P_0$ since $I_p = 3 \times I_0$ Hence total circuit power = $P_0 + P_0 + 4P_0 + 9P_0$ = $15P_0$ Award (1) for correct individual power analysis Award (1) for correct reason linked to currents Award (1) for showing correct total P		3		3	2	
	(d)		Circuit resistance increases, leading to total current decreasing. Power dissipated in circuit decreases (1) V across R_0 has increased (from 1.8 V to 3.0 V), so P_0 increases / I through R_0 has increased (from 0.4 A to 0.67 A) so P_0 increases (1) Hence ratio decreases (1) [only award from correct explanation] Accept numerical explanation: e.g. Circuit resistance is now 13.5 Ω and circuit current = 0.67 A (1) circuit power shown to be 6 W and P_0 shown to be 2 W (1) Hence ratio decreases or is now 3 (1) Alternative: With T removed, I through all remaining resistors is the same or V across each is the same (1) Use of VI or I^2R or V^2/R or power / energy dissipated in all three resistors equal (1) So total $P = 3 \times P_0$ or which is less than $15P_0$ (1)		3		3		
			Question 2 total	2	12	0	14	7	0

#8

Question	Marking details	Marks available					
		AO1	AO2	AO3	Total	Maths	Prac
5 (a) (i)	All resistors connected in parallel (1) Using $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ [or equiv] (1) $R_{\text{total}} = 1.44 [\Omega]$ (1)	1	1		3	2	3
(b) (i)	(A4/emf) is the energy generated in the cell (1) per coulomb (1) Loss of energy in circuit in the load resistor (E4) (1) $E - V$ is the energy is lost in internal resistance (1) Energy is conserved (1) Re-arrange gives $r = \frac{E - V}{I}$ (1)	1	1		6	1	
(ii)	Substituting values in $\frac{A7 - E7}{D7}$ (1) $r = 0.15 [\Omega]$ (1)	1	1		2	2	
(iii)	Using $P = I^2 R$ (1) $P = 0.45 [\text{W}]$ (1) 0.50 W – has to be greater than the power dissipated (need reason) (1)	1	1		3	1	
Question 5 total		5	9	0	14	6	3

#9

Question	Marking details	Marks available																	
		AO1	AO2	AO3	Total	Maths	Prac												
(a) (i)	For Left Hand Combination: $\frac{1}{R_{\text{parallel}}} = \frac{1}{2R} + \frac{1}{R} + \frac{1}{2R}$ (RHS seen in any correct form e.g. $\frac{4}{2R}$) (1) $= \frac{R}{2}$ (1) Total $R = \frac{R}{2} + R$ or $\frac{3R}{2}$ seen (1) Alternative solutions possible e.g. Sum of top and bottom branch = R (1) Then parallel branch = $\frac{R}{2}$ (1) Total $R = \frac{R}{2} + R$ (1)		3		3	3													
(ii)	Right hand resistor circled (1) Greatest current / greatest voltage (1)		2		2														
(b)	Correct substitution into $l = \frac{RA}{\rho}$ i.e. $\frac{2.0 \times 10^8 \times 250 \times 10^{-9} \times 0.25 \times 10^{-3}}{1.20 \times 10^{-6}}$ (1) $l = 0.10 [\text{m}]$ (1) (ecf on slip in powers of 10)	1	1		2	2													
(c) (i)	n - free electron density. Accept- number of free electrons per unit volume or per m^3 (or equivalent)	1			1														
(ii)	<table border="1"> <thead> <tr> <th>Ratio</th> <th>Value</th> <th>Explanation</th> </tr> </thead> <tbody> <tr> <td>$\frac{n_x}{n_y}$</td> <td>1</td> <td>Wires made of the same material</td> </tr> <tr> <td>$\frac{I_x}{I_y}$</td> <td>1</td> <td>Wires in series</td> </tr> <tr> <td>$\frac{v_x}{v_y}$</td> <td>0.25</td> <td>Correct explanation based on $A_x v_x = A_y v_y$ e.g. $(\frac{d}{2})^2 v_y$</td> </tr> </tbody> </table> <p>Award 1 mark for each correct row</p>	Ratio	Value	Explanation	$\frac{n_x}{n_y}$	1	Wires made of the same material	$\frac{I_x}{I_y}$	1	Wires in series	$\frac{v_x}{v_y}$	0.25	Correct explanation based on $A_x v_x = A_y v_y$ e.g. $(\frac{d}{2})^2 v_y$	1	1	1	3		
Ratio	Value	Explanation																	
$\frac{n_x}{n_y}$	1	Wires made of the same material																	
$\frac{I_x}{I_y}$	1	Wires in series																	
$\frac{v_x}{v_y}$	0.25	Correct explanation based on $A_x v_x = A_y v_y$ e.g. $(\frac{d}{2})^2 v_y$																	
(iii)	$R = \frac{\rho l}{A}$ substituted into $P = I^2 R$ i.e. $P = \frac{I^2 \rho l}{A}$ (1) $P_x = \frac{I^2 \rho_x l_x}{A_x}$ and $P_z = \frac{I^2 \rho_z l_z}{A_z}$ (or equivalent) - can award 1 st mark from one of these expressions $A_x = 4A_z$ and $l_x = \frac{l_z}{2}$ and $\rho_x = 2\rho_z$ to show: (1) $\frac{P_x}{P_z} = 4$ (1)		3		3	3													
Question total		4	10	0	14	8	0												