

Mark schemes

1	A	[1]
2	B	[1]
3	B	[1]
4	D	[1]
5	B	[1]
6	A	[1]
7	D	[2]
8	C	[1]
9	C	[1]
10	D	[1]

11 D [1]

12 A [1]

13 A [1]

14 C [1]

15 D [1]

16 D [1]

17 B [1]

18 B [1]

19 (a) $d = \frac{8.9 \times 10^{-12} \times 2.3 \times 250 \times 10^{-4}}{370 \times 10^{-12}} \checkmark$

$1.4 \times 10^{-3} \text{ m (1.4 (1.38) mm)} \checkmark$

Data substitution – condone incorrect powers of 10 for C and A ✓

2

(b) New capacitance = 161 pF ✓

New $V = 0.13 \text{ nC} / 161 \text{ pF} = 81 \text{ V} \checkmark$

2

(c) Energy stored = $\frac{1}{2} \times 161 \times 10^{-12} \times 81^2 \checkmark$

0.53 μJ \checkmark

2

(d) Energy increases because:

In the polar dielectric molecules align in the field with positive charged end toward the negative plate (or WTTE). \checkmark

Work is done on the capacitor separating the positively charged surface of the dielectric from the negatively charged plate (or vice versa). \checkmark

2

[8]

20

(a) (i) energy stored by capacitor (= $\frac{1}{2} CV^2$)

$$= \frac{1}{2} \times 70 \times 1.2^2 \checkmark (= 50.4) = 50 \text{ (J)} \checkmark$$

to **2 sf** only \checkmark

3

(ii) energy stored by cell (= $I V t$) = $55 \times 10^{-3} \times 1.2 \times 10 \times 3600 \checkmark$

$$= 2380 \text{ J}$$

$$\frac{\text{energy stored by cell}}{\text{energy stored by capacitor}} = \frac{2380}{50} = 48 \text{ (ie about 50)} \checkmark$$

2

(b) capacitor would be impossibly large (to fit in phone) \checkmark

capacitor would need recharging very frequently

[or capacitor could only power the phone for a short time] \checkmark

capacitor voltage [or current supplied or charge] would fall continuously while in use \checkmark

max 2

[7]

21

(a) ratio of charge to potential

C1

4.2 μC per volt etc

A1

2

- (b) (i) method: time for voltage to half/tangent at origin/use of decay equation/ $1/e$ value

B1

appropriate reading from graph ($T_{1/2} = 440$ or $450 \mu\text{s}$)

B1

substitution into correct equation

B1

R correct for method ($151/152/155 \Omega$)

B1

4

- (ii) **B** smaller than **A** **M0**

B discharges faster/**A** discharges slower

B1

reference to decay equation/calculation for **B**

B1

2

- (c) $E = \frac{1}{2} CV^2$ or $\frac{1}{2} QV$ seen

C1

both 4.0 (V) and 0.9 (V)/ 16.8 (μC) and 3.8 (μC) seen

C1

31.9 (μJ)

A1

3

[11]

22

- (a) (i) tangent drawn at
- $t = 0$

M1

coordinates correct and manipulated correctly
 0.015 to 0.020 (A) 15 mA – 20 mA
 or $V = 4000$ V as in (ii) then $I = 18$ mA

A1

2

- (ii)
- $V = 220 \times$
- their (i) condoning powers of 10

C1

about 4000 V (3300 – 4400 V)

A1

or use of $V = Q/C$; $V = 100$ mC/25 μ F

C1

4000 V

A1

2

- (iii) more charge leads to increased potential difference across the capacitor

M1

$$\text{pd} = V_R + V_C$$

or if V_C increases then V_R decreases

M1

(if V_R falls) so I falls

A1

3

- (b) (i) use of energy =
- $\frac{1}{2} Q^2/C$
- or use of
- $C = Q/V$
- and
- $\frac{1}{2} QV$

C1

0.083(7) or 0.084 C

condone 0.083 C

A1

2

- (ii) power = 14 kW

B1

(c) time constant = 5.5 s

M1

sensible attempt to find the charge after 8.3 s – by calculation or reading from graph

M1

about 78 mC and needs to be 85 mC/has not reached 85 mC so designer's suggestion is not valid

A1

3

[13]

23

(a) $E \propto V^2$ (or $E = \frac{1}{2}CV^2$) (1)

pd after 25 s = 6 V (1)

2

(b) (i) use of $Q = Q_0 e^{-t/RC}$ or $V = V_0 e^{-t/RC}$ (1)

(e.g. $6 = 12e^{-25/RC}$) gives $e^{-\frac{25}{RC}} = \frac{12}{6}$ and $\frac{25}{RC} = \ln 2$ (1)

($RC = 36(.1)$ s)

[alternatives for (i):

$V = 12 e^{-25/36}$ gives $V = 6.0$ V (1) (5.99 V)

or time for pd to halve is $0.69RC$

$\therefore RC = \frac{25}{0.69}$ (1) = 36(.2) s]

(ii) $R = \frac{36.1}{680 \times 10^{-6}}$ (1) = $5.3(0) \times 10^4 \Omega$ (1)

4

[6]

24


- (a) (i) straight line through origin **(1)**
- (ii) $\frac{1}{\text{capacitance}}$ **(1)**
- (iii) energy (stored by capacitor) **(1)** (or work done (in charging capacitor))

3

- (b) (i) $RC = 5.6 \times 10^3 \times 6.8 \times 10^{-3}$ **(1)** (= 38.1 s)
 $V (= V_0 e^{-t/RC}) = 12 e^{-26/38.1}$ **(1)**
 $= 6.1 \text{ V}$ **(1)** (6.06 V)
 [or equivalent using $Q = Q_0 e^{-t/RC}$ and $Q = CV$]

- (ii) $(RC)' = 2.8 \times 10^3 \times 6.8 \times 10^{-3}$ **(1)** (= 19.0 s)
 $V (= 6.06 e^{-14/19}) = 2.9(0) \text{ V}$ **(1)**
 (use of $V = 6.1 \text{ V}$ gives $V = 2.9(2) \text{ V}$)

(iii)

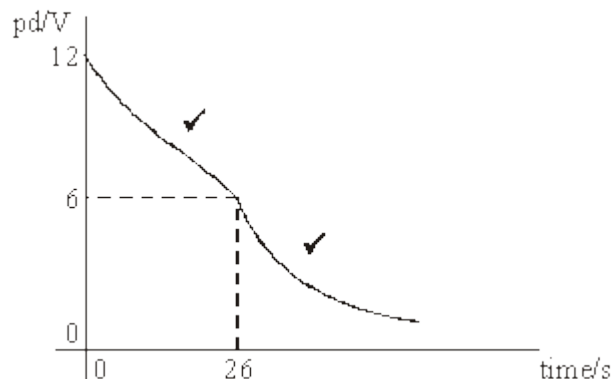

7

[10]**25**

- (a) $Q (= CV = 330 \times 9.0) = 2970 \text{ } (\mu\text{C})$ **(1)**
 $E (= \frac{1}{2}QV) = \frac{1}{2} \times 2.97 \times 10^{-3} \times 9.0 = 1.34 \times 10^{-2} \text{ J}$ **(1)**
 [or $E (= \frac{1}{2}CV^2) = \frac{1}{2} \times 330 \times 10^{-6} \times 9.0^2$ **(1)** = $1.34 \times 10^{-2} \text{ J}$ **(1)**]

2

- (b) time constant (= RC) = $470 \times 10^3 \times 330 \times 10^{-6} = 155 \text{ s}$ **(1)**

1

$$(c) \quad Q (= Q_0 e^{-t/RC}) = 2970 \times e^{-60/155}$$

$$= 2020 \text{ } (\mu\text{C})$$

(allow C.E. for time constant from (b))

$$V = \left(\frac{Q}{C} \right) = \frac{2020}{330} = 6.11 \text{ V } \quad (1)$$

(allow C.E. for Q)

$$[\text{or } V = V_0 e^{-t/RC} \quad (1) = 9.0 e^{-60/155} \quad (1) \quad = 6.11 \text{ V } \quad (1)]$$

3

[6]

26

$$(a) \quad Q = CV \quad (1)$$

$$= 4.7 \times 10^{-6} \times 6.0 = 28 \times 10^{-6} \text{ C or } 28 \mu\text{C} \quad (1)$$

2

$$(b) \quad E = \frac{1}{2} CV^2 \quad (1)$$

$$= \frac{1}{2} \times 4.7 \times 10^{-6} \times 2.0^2 \quad (1)$$

$$= 9.4 \times 10^{-6} \text{ J } \quad (1)$$

$$[\text{or } E = \frac{1}{2} QV \quad (1)]$$

$$= \frac{1}{2} \times 9.4 \times 10^{-6} \times 2.0 \quad (1)$$

$$= 9.4 \times 10^{-6} \text{ J } \quad (1)]$$

3

$$(c) \quad \text{time constant is time taken for } V \text{ to fall to } \frac{V_0}{e} \quad (1)$$

$$\therefore V \text{ must fall to } 2.2 \text{ V } \quad (1)$$

$$\text{time constant} = 32 \text{ ms } \quad (1)$$

$$[\text{or draw tangent at } t = 0 \quad (1)]$$

$$\text{intercept of tangent on } t \text{ axis is time constant } \quad (1)$$

$$\text{accept value } 30 - 35 \text{ ms } \quad (1)]$$

$$[\text{or } V = V_0 \exp(-t/RC) \text{ or } Q = Q_0 \exp(-t/RC) \quad (1)]$$

$$\text{correct substitution } \quad (1)$$

$$\text{time constant} = 32 \text{ ms } \quad (1)]$$

3

(d) time constant = RC (1)


$$R = \frac{32 \times 10^{-3}}{4.7 \times 10^{-3}} = 6800 \Omega \text{ (1)}$$

(allow C.E. for value of time constant from (c))

2
[10]

27

(a)

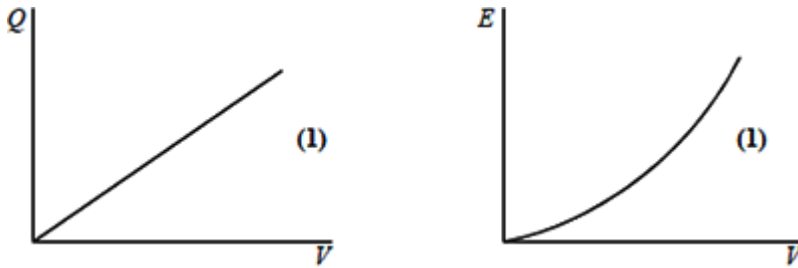

capacitance [or charge per volt or Q/V] (1)

(3)

(b) (i) $Q = CV (= 0.68 \times 6.0) = 4.1 \text{ C}$ (1)

(ii) $E \left(= \frac{1}{2} QV = \frac{1}{2} \times 4.1 \times 6.0 \right) = 12 \text{ J}$ (1)

(2)

[5]

28

(a) (i) remains constant since connected to constant p.d. (1)

(ii) decreases because $C \propto \frac{1}{d}$ (1)

(iii) decreases because $Q = CV$ and C has decreased (1)

(iv) decreases because $E = \frac{1}{2} CV^2$ and C has decreased (1)

4

(b) (i) $C \left(= \frac{\epsilon_0 A}{d} \right) = \frac{8.85 \times 10^{-12} \times 8.0 \times 10^6}{0.75 \times 10^{-3}} \text{ (1) } (= 9.44 \times 10^{-8} \text{ F})$

$E (= \frac{1}{2} CV^2) = \frac{1}{2} \times 9.44 \times 10^{-8} \times (200 \times 10^3)^2 \text{ (1)}$
 $= 1890 \text{ J (1)}$

(ii) $I \left(= \frac{Q}{t} \right) = \frac{9.44 \times 10^{-8} \times 200 \times 10^3}{120 \times 10^{-6}} \text{ use of } Q = CV \text{ (1) use of } I = \frac{Q}{t} \text{ (1)}$
 $= 157 \text{ A (1)}$

6
[10]

29

(a) $1/C = 1/500 + 1/1000 \text{ or } C = \frac{500 \times 1000}{500 + 1000}$

C1

330 (333) μF

A1

2

(b) (i) $Q = VC \text{ or } Q = 0.25 \times 9$

C1

2.3 or 2.25 C (c.a.o. unit essential)

A1

(ii) $\text{energy} = \frac{1}{2} CV^2 \text{ or } 0.5 \times 0.25 \times 9^2 \text{ or } \frac{1}{2} QV \text{ used}$

C1

10(.1) J (allow e.c.f. for Q)

A1

(iii) $V = V_0 e^{-t/RC}$

C1

7

$0.1 = 9 e^{-t/(8.5 \times 0.25)}$

C1

9.6 (9.56) s

(c) (i) $Q = mc\Delta\theta$ or mass = volume \times density

C1

correct substitution $10.1 = (2.2 \times 10^{-7} \times 8900 \times 400 \times \Delta\theta)$

C1

12 (12.3) K or $^{\circ}\text{C}$ ecf for energy from (b) (ii)

A1

5

(ii) some energy raises temperature of the thermometer

B1

energy/heat lost to (raise temperature of) surroundings

B1

[14]**30**

(a) 1 coulomb of charge is stored for a p.d. of 1 V between the plates
(or equivalent statement) Condone 1 coulomb per volt

B1

1

(b) (i) Correct substitution in $C = \frac{\epsilon_0 \epsilon_r A}{d}$ (ignore powers of 10)

C1

Plate area = $4.65 \times 10^{-3} \text{ m}^2$ or $C = \frac{\epsilon_0 \epsilon_r \pi r^2}{d}$ with correct data

A1

Radius = (their area /3.14)^{1/2}; 0.038(4 or 5) m if correct

B1

3

- (ii) $E = \frac{1}{2} CV^2$ or correct numerical substitution or
 $E = \frac{1}{2} QV$ & $Q = VC$

C1

$$4.1(4) \times 10^{-10} \text{ J}$$

A1

2

- (c) Time constant = RC or Time to halve = $0.69 RC$
 or $V = V_0 e^{-t/RC}$

C1

Time to fall to $1/e$ (0. 19 ms) or time to halve (0. 13 ms)
 or $V_0 = 6 \text{ V}$ and correct coordinates of point on line
 (0.6 ms max)

C1

$$8.1 - 8.6 \text{ M}\Omega$$

A1

3

[9]