

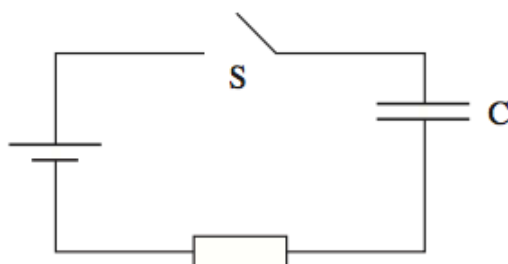


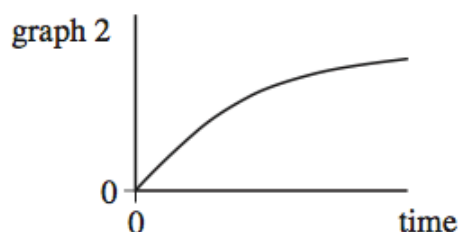1)

In the circuit shown the capacitor C charges when switch S is closed.



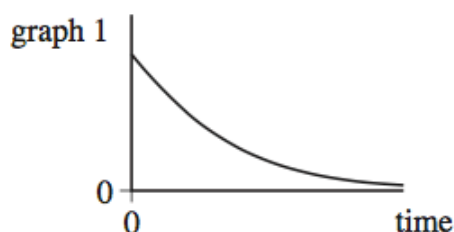Which line, **A** to **D**, in the table gives a correct pair of graphs showing how the charge on the capacitor and the current in the circuit change with time after S is closed?



	charge	current
A	graph 1	graph 1
B	graph 1	graph 2
C	graph 2	graph 2
D	graph 2	graph 1

2)

A capacitor of capacitance C stores an amount of energy E when the pd across it is V . Which line, **A** to **D**, in the table gives the correct stored energy and pd when the charge is increased by 50%?

	energy	pd
A	$1.5 E$	$1.5 V$
B	$1.5 E$	$2.25 V$
C	$2.25 E$	$1.5 V$
D	$2.25 E$	$2.25 V$


3)

A capacitor of capacitance C discharges through a resistor of resistance R . Which one of the following statements is **not** true?

- A The time constant will decrease if C is increased.
- B The time constant will increase if R is increased.
- C After charging to the same voltage, the initial discharge current will increase if R is decreased.
- D After charging to the same voltage, the initial discharge current will be unaffected if C is increased.

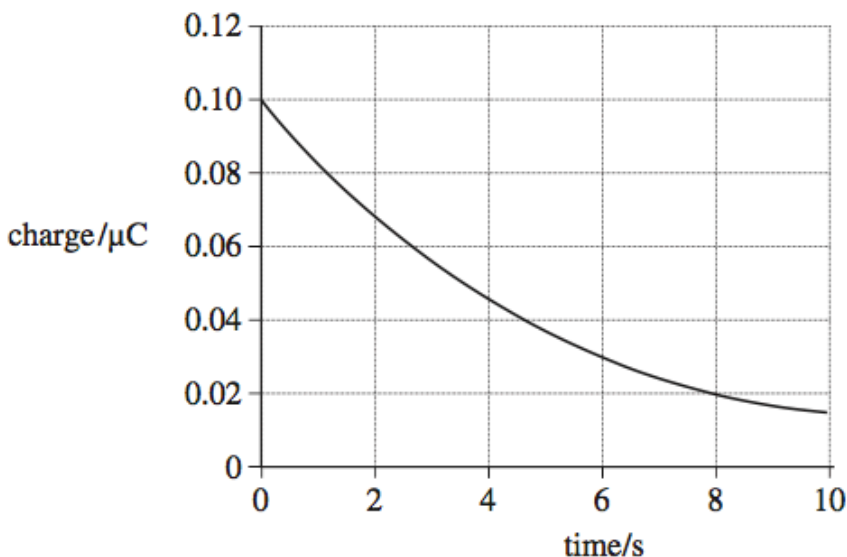4)

The graph shows how the charge on a capacitor varies with time as it is discharged through a resistor.



What is the time constant for the circuit?

- A 3.0 s
- B 4.0 s
- C 5.0 s
- D 8.0 s

5)

A $1\ \mu\text{F}$ capacitor is charged using a **constant** current of $10\ \mu\text{A}$ for 20 s. What is the energy finally stored by the capacitor?

- A $2 \times 10^{-3}\ \text{J}$
- B $2 \times 10^{-2}\ \text{J}$
- C $4 \times 10^{-2}\ \text{J}$
- D $4 \times 10^{-1}\ \text{J}$

6)

An uncharged 4.7 nF capacitor is connected to a 1.5 V supply and becomes fully charged.

How many electrons are transferred to the negative plate of the capacitor during this charging process?

- A 2.2×10^{10}
- B 3.3×10^{10}
- C 4.4×10^{10}
- D 8.8×10^{10}


7)

When fully charged the 2.0 mF capacitor used as a backup for a memory unit has a potential difference of 5.0 V across it. The capacitor is required to supply a constant current of $1.0 \mu\text{A}$ and can be used until the potential difference across it falls by 10% . For how long can the capacitor be used before it must be recharged?

- A 10 s
- B 100 s
- C 200 s
- D 1000 s

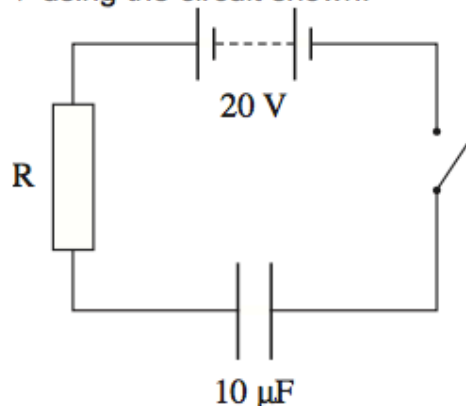8)

A capacitor of capacitance $10 \mu\text{F}$ is charged through a resistor R to a potential difference (pd) of 20 V using the circuit shown.



When the capacitor is fully charged which one of the following statements is **incorrect**?

- A The energy stored by the capacitor is 2 mJ .
- B The total energy taken from the battery during the charging process is 2 mJ .
- C The pd across the capacitor is 20 V .
- D The pd across the resistor is 0 V .

9)


Initially a charged capacitor stores $1600 \mu\text{J}$ of energy. When the pd across it decreases by 2.0 V , the energy stored by it becomes $400 \mu\text{J}$.

What is the capacitance of this capacitor?

- A $100 \mu\text{F}$
- B $200 \mu\text{F}$
- C $400 \mu\text{F}$
- D $600 \mu\text{F}$

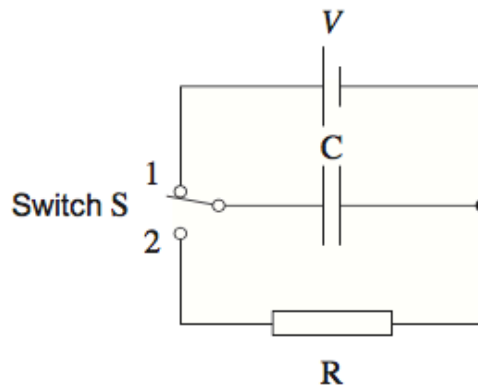10)

Switch S in the circuit is held in position 1, so that the capacitor C becomes fully charged to a pd V and stores energy E .



The switch is then moved quickly to position 2, allowing C to discharge through the fixed resistor R . It takes 36 ms for the pd across C to fall to $\frac{V}{2}$. What period of time must elapse, after the switch has moved to position 2, before the energy stored by C has fallen to $\frac{E}{16}$?

- A 51 ms
- B 72 ms
- C 432 ms
- D 576 ms

11)

A nuclear fusion device is required to deliver at least 1 MJ of energy using capacitors. If the largest workable potential difference is 10 kV, what is the minimum capacitance of the capacitors that should be used?

- A 0.01 F
- B 0.02 F
- C 2 F
- D 100 F

12)

The voltage across a capacitor falls from 10 V to 5 V in 48 ms as it discharges through a resistor.

What is the time constant of the circuit?

- A 24 ms
- B 33 ms
- C 69 ms
- D 96 ms

13)


A 1000 μF capacitor and a 10 μF capacitor are charged so that they store the same energy. The pd across the 1000 μF capacitor is V_1 and the pd across the other capacitor is V_2 .

What is the value of the ratio $\left(\frac{V_1}{V_2}\right)^2$?

- A $\frac{1}{1000}$
- B $\frac{1}{100}$
- C $\frac{1}{10}$
- D 10

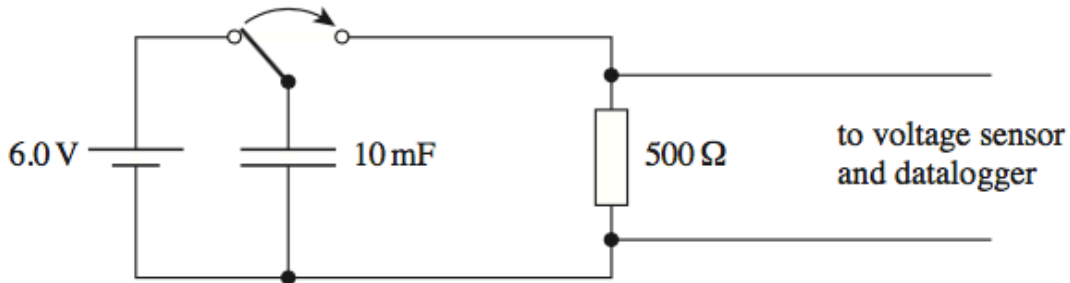14)

A voltage sensor and a datalogger are used to record the discharge of a 10 mF capacitor in series with a 500 Ω resistor from an initial pd of 6.0 V. The datalogger is capable of recording 1000 readings in 10 s. Which line, **A** to **D**, in the table gives the pd and the number of readings made after a time equal to the time constant of the discharge circuit?



	potential difference/V	number of readings
A	2.2	50
B	3.8	50
C	3.8	500
D	2.2	500

15)

When a 220 μF capacitor is discharged through a resistor R, the capacitor pd decreases from 6.0 V to 1.5 V in 92 s.

What is the resistance of R?

- A** 210 kΩ
- B** 300 kΩ
- C** 420 kΩ
- D** 440 kΩ

16)

A 400 μF capacitor is charged so that the voltage across its plates rises at a constant rate from 0 V to 4.0 V in 20 s. What current is being used to charge the capacitor?

- A** 5 μA
- B** 20 μA
- C** 40 μA
- D** 80 μA


17)

When a capacitor discharges through a resistor it loses 50% of its charge in 10s. What is the time constant of the capacitor-resistor circuit?


- A 0.5 s
- B 5 s
- C 14 s
- D 17 s

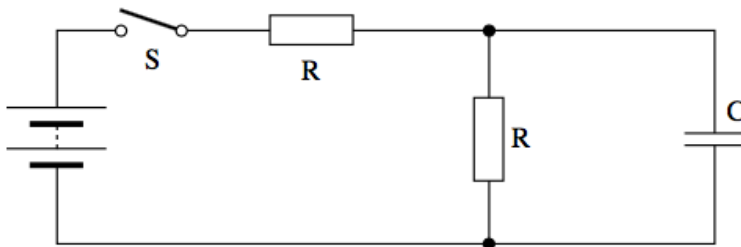18)


When switch S in the circuit is closed, the capacitor C is charged by the battery to a pd V_0 . The switch is then opened until the capacitor pd decreases to $0.5 V_0$, at which time S is closed again. The capacitor then charges back to V_0 .



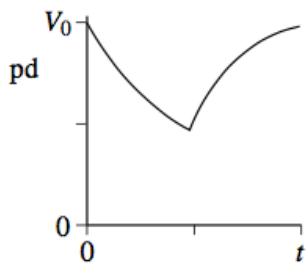
Which graph best shows how the pd across the capacitor varies with time, t , after S is opened?




A

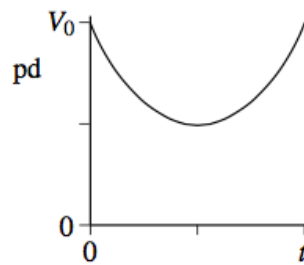

B

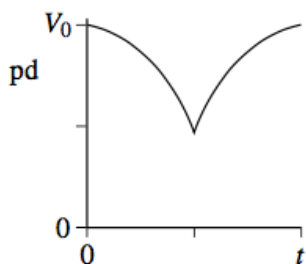

C

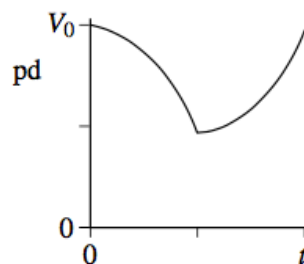

D