

1)

(a)		(use of $1/R_{\text{total}} = 1/R_1 + 1/R_2$) $1/R_{\text{total}} = 1/400 + 1/400 = 2/400$ $R_{\text{total}} = 200 \Omega$ ✓ (working does not need to be shown) hence total resistance = $25 + 200 = 225 \Omega$ ✓	2
(b)	(i)	(use of $P = V^2/R$) $1 = V^2/400$ ✓ $V^2 = 400$ (working does not need to be shown) $V = 20 \text{ V}$ ✓	6
	(ii)	(use of $I = V/R$) $I = 20/400 = 0.05 \text{ A}$ ✓ (working does not need to be shown) hence current = $2 \times 0.05 = 0.10 \text{ A}$ ✓	
	(iii)	(use of $V = IR$) pd across 25Ω resistor = $25 \times 0.10 = 2.5 \text{ V}$ ✓ (working does not need to be shown) hence maximum applied pd = $20 + 2.5 = 22.5 \text{ V}$ ✓	
Total			8

2)

(a)	(i)	$6.0 (\Omega)$ ✓	1
(a)	(ii)	$4.5 (\text{V})$ ✓	1
(a)	(iii)	(use of $I = V/R$) $I = 4.5/6.0 = 0.75 (\text{A})$ ✓ current through cell A = $0.75/2 = 0.375 (\text{A})$ ✓	2
(a)	(iv)	charge = $0.375 \times 300 = 112$ ✓ C ✓	2
(b)		cells C and D will go flat first or A and B last longer ✓ current/charge passing through cells C and D (per second) is double/more than that passing through A or B ✓ energy given to charge passing through cells per second is double or more than in cells C and D ✓ or in terms of power	3
Total			9

3)

a		(use of $P = VI$) $I = 36/12 = 3.0 \text{ A} \checkmark$ $I = 2.0/4.5 = 0.44 \text{ A} \checkmark$	2
b	i	pd = $24 - 12 = 12 \text{ V} \checkmark$	1
b	ii	current = $3.0 + 0.44 = 3.44 \text{ A} \checkmark$	1
b	iii	$R_1 = 12/3.44 = 3.5 \Omega \checkmark$	1
b	iv	pd = $12 - 4.5 = 7.5 \text{ V} \checkmark$	1
b	v	$R_2 = 7.5/0.44 = 17 \Omega \checkmark$	1
c	i	(circuit) resistance increases \checkmark current is lower (reducing voltmeter reading) \checkmark or correct potential divider argument	2
c	ii	pd across Y or current through Y increases \checkmark hence power/rate of energy dissipation greater or temperature of lamp increases \checkmark	2
Total			11

4)

a	i	(use of $R = V/I$) $R = 10/2.0 = 5.0 \Omega \checkmark$	1
a	ii	$\frac{1}{R} = \frac{1}{3} + \frac{1}{3+3} = \frac{3}{6} \checkmark$ $R = 2(\Omega) \checkmark$ $R_{\text{total}} = 2 + 3 \checkmark (= 5 \Omega)$	3
b	i	voltage across Y = $10.0 - 2.0 \times 3.0 = 4.0 \text{ V} \checkmark$ current in Y = $4.0/3.0 = 1.3 \text{ A} \checkmark$	2
b	ii	current through W = $0.67 \text{ A} \checkmark$ voltage = $0.67 \times 3 = 2.0 \text{ V} \checkmark$ (or $4.0/2 \checkmark = 2.0 \text{ V} \checkmark$)	2
Total			8

5)

a	i	(use of $P=VI$) $I = 36/12 + 6/12 \checkmark = 3.5 \text{ (A)} \checkmark$	2
a	ii	(use of $V=IR$) $R = 12/3 = 4 \text{ (}\Omega\text{)} \checkmark$	1
a	iii	$R = 12/0.50 = 24 \checkmark \text{ (}\Omega\text{)}$	1
b		terminal pd/voltage across lamp is now less OR current is less \checkmark due to lost volts across internal resistance OR due to higher resistance \checkmark lamps less bright \checkmark	3
c	i	current through lamps is reduced as resistance is increased or pd across lamps is reduced as voltage is shared \checkmark hence power is less OR lamps dimmer \checkmark	2
c	ii	lamp Q is brighter \checkmark lamp Q has the <u>higher resistance</u> hence <u>pd/voltage</u> across is greater \checkmark current is the same for both \checkmark hence power of Q greater \checkmark	max 3

6)

a	i	(use of $V = IR$) $I = (12-8) / 60 \checkmark = 0.067 \text{ Or } 0.066 \text{ (A)} \checkmark$	2
a	ii	(use of $V = IR$) $R = 8/0.067 = 120 \text{ (}\Omega\text{)} \checkmark$	1
a	iii	(use of $Q = It$) $Q = 0.067 \times 120 = 8.0 \checkmark \text{ C} \checkmark$	2
b		reading will increase \checkmark resistance (of thermistor) decreases (as temperature increases) \checkmark current in circuit increase (so pd across R_1 increases) OR correct potential divider argument \checkmark	3

7)

(i)	(use of $V=Ir$) $V = 4.2 \times 1.5 \checkmark = 6.3$ (V)	1	
(ii)	$pd = 12 - 6.3 = 5.7$ V ✓	1	NO CE from (i)
(iii)	(use of $I = V/R$) $I = 5.7/2.0 = 2.8(5)$ A ✓	1	CE from (ii) (a(ii)/2.0) accept 2.8 or 2.9
(iv)	$I = 4.2 - 2.85 = 1.3(5)$ A ✓	1	CE from (iii) (4.2 –(a)(iii)) accept 1.3 or 1.4
(v)	$R = 5.7/1.35 = 4.2$ Ω ✓	1	CE from (iv) (a(ii)/(a)(iv)) Accept range 4.4 to 4.1
(vi)	$\frac{1}{R_{parallel}} = \frac{1}{4.2} + \frac{1}{2.0} = 0.737$ ✓ $R_{parallel} = 1.35$ Ω $R_{total} = 1.35 + 1.5 \checkmark = 2.85$ Ω OR $R = 12/4.2 \checkmark$ $R = 2.85$ Ω ✓	2	CE from (a)(v) second mark for adding internal resistance

(b)	(i)	resistor	Rate of energy dissipation (W)	3	CE from answers in (a) but not for first value 2.0: $a(iii)^2 \times 2$ R: $a(iv)^2 \times a(v)$
		1.5 Ω internal resistance	$4.2^2 \times 1.5 = 26.5$ ✓		
		2.0 Ω	$2.85^2 \times 2.0 = 16.2$ (15.68 – 16.82) ✓		
		R	$1.35^2 \times 4.2 = 7.7$ (7.1 – 8.2) ✓		
(b)	(ii)	energy provided by cell per second = $12 \times 4.2 = 50.4$ (W) ✓ energy dissipated in resistors per second = $26.5 + 16.2 + 7.7 = 50.4$ ✓ (hence energy input per second equals energy output)		2	if not equal can score second mark if an appropriate comment

8)

(a)	(i)	(use of $I = V/R$) $I = 6.0/(50\ 000+35\ 000+5000) \checkmark = 6.7 \times 10^{-5}$ A ✓	2	first mark for adding resistance values 90 k Ω accept 7×10^{-5} or dotted 6×10^{-5} but not 7.0×10^{-5} and not 6.6×10^{-5}
(a)	(ii)	$V = 6.7 \times 10^{-5} \times 5000 \checkmark = 0.33$ (0.33 – 0.35) V ✓ OR $V = 5/90 \times 6 \checkmark = 0.33$ (V) ✓	2	CE from (i) BALD answer full credit 0.3 OK and dotted 0.3
(b)		resistance of LDR decreases ✓ reading increase because greater <u>proportion/share</u> of the voltage across R OR higher current ✓	2	need first mark before can qualify for second
(c)		$I = 0.75/5000 = 1.5 \times 10^{-4}$ (A) ✓ (pd across LDR = 0.75 (V)) pd across variable resistor = $6.0 - 0.75 - 0.75 = 4.5$ (V) ✓ $R = 4.5/1.5 \times 10^{-4} = 30\ 000$ Ω ✓ OR $I = 0.75/5000 = 1.5 \times 10^{-4}$ (A) ✓ $R_{total} = 6.0/1.5 \times 10^{-4} = 40\ 000$ Ω ✓ $R = 40\ 000 - 5000 - 5000 = 30\ 000$ Ω ✓	3	

9)

(a)	(i)	voltage = $0.01 \times 540 = 5.4 \text{ V}$ ✓	1
(a)	(ii)	voltage = $15 - 5.4 = 9.6 \text{ V}$ ✓	1
(a)	(iii)	(use of resistance = voltage/current) resistance = $9.6/0.01$ ✓ = 960Ω ✓ or $R_T = 15/0.01 = 1500 \Omega$ ✓ $R = 150 - 590 = 960 \Omega$ ✓ or potential divider ratio ✓✓	2
(a)	(iv)	(use of $1/R = 1/R_1 + 1/R_2$) $1/960 = 1/200 + 1/R_2$ ✓ $1/R_2 = 1/960 - 1/1200$ $R_2 = 4800 \Omega$ ✓	2
(b)		(voltage of supply constant) (circuit resistance decreases) (supply) current increases or potential divider argument ✓ hence pd across 540Ω resistor increases ✓ hence pd across 1200Ω decreases ✓ or resistance in parallel combination decreases ✓ pd across parallel resistors decreases ✓ pd across 1200Ω decreases ✓	3
Total			9

10)

a	(i)	$1/R_{\text{total}} = 1/(40)$ ✓ + $1/(10+5)$ ✓ = 0.09167 $R_{\text{total}} = 10.9 \text{ k}\Omega$ ✓	3									
a	(ii)	$I = 12/10.9\text{k} = 1.1 \text{ mA}$ ✓	1									
b		<table border="1" style="width: 100%;"> <tr> <td>position</td> <td>pd/V</td> </tr> <tr> <td>AC</td> <td>6.0 ✓</td> </tr> <tr> <td>DF</td> <td>4.0 ✓</td> </tr> <tr> <td>CD</td> <td>2.0 ✓</td> </tr> </table>	position	pd/V	AC	6.0 ✓	DF	4.0 ✓	CD	2.0 ✓	3	C.E. for CD
position	pd/V											
AC	6.0 ✓											
DF	4.0 ✓											
CD	2.0 ✓											
c	(i)	AC: no change ✓ constant pd across resistors/parallel branches(AE) ✓	2	no CE from first mark								
c	(ii)	DF: decreases ✓ as greater proportion of voltage across fixed/ $10 \text{ k}\Omega$ resistor ✓	2	no CE from first mark								

11)

a	(i)	(use of $I = V/R$) $I = 12/8 \checkmark = 1.5\text{ A } \checkmark$	5
	(ii)	$I = (12 - 0.65 \checkmark)/4 = 2.8\text{ A } \checkmark$ sig figs \checkmark	
(b)	(i)	pd = $6.0 - 1.6 = 4.4\text{ (V) } \checkmark$	1
(b)	(ii)	current = $4.4/1200 = 3.7 \times 10^{-3}\text{ (A) } \checkmark$ (not 3.6)	1
(b)	(iii)	resistance = $1.6/3.7 \times 10^{-3} = 440$ or $430\text{ (}\Omega\text{) } \checkmark$ 2 sfs \checkmark	2
(c)		less current now flows or terminal pd/voltage lower \checkmark (or voltage across cell/external circuit is lower) (hence) pd/voltage across resistor will decrease \checkmark	2
Total			11

12)

(a)	(i)	voltage = $0.01 \times 540 = 5.4 \text{ V}$ ✓	1
(a)	(ii)	voltage = $15 - 5.4 = 9.6 \text{ V}$ ✓	1
(a)	(iii)	(use of resistance = voltage/current) resistance = $9.6/0.01$ ✓ = 960Ω ✓ or $R_T = 15/0.01 = 1500 \Omega$ ✓ $R = 150 - 590 = 960 \Omega$ ✓ or potential divider ratio ✓✓	2
(a)	(iv)	(use of $1/R = 1/R_1 + 1/R_2$) $1/960 = 1/200 + 1/R_2$ ✓ $1/R_2 = 1/960 - 1/1200$ $R_2 = 4800 \Omega$ ✓	2
(b)		(voltage of supply constant) (circuit resistance decreases) (supply) current increases or potential divider argument ✓ hence pd across 540Ω resistor increases ✓ hence pd across 1200Ω decreases ✓ or resistance in parallel combination decreases ✓ pd across parallel resistors decreases ✓ pd across 1200Ω decreases ✓	3
Total			9