

- 1) C
- 2) C
- 3) B
- 4)

(a) (i)	e.m.f. = energy / charge	C1	
	= $(1.6 \times 10^5) / (1.8 \times 10^4)$		
	= 8.9 V	A1	
(ii)	current = $\Delta Q / \Delta t$	C1	
	= $(1.80 \times 10^4) / (1.3 \times 10^5)$		
	= 0.14 A	A1	[4]
(b) (i)	energy $\propto R$ (or formula)	C1	
	energy = $(15 / 45) \times 1.14 \times 10^5$	C1	
	= 3.7×10^4 J	A1	
(ii)	energy dissipated in internal resistance (of battery)	B1	[4]
	OR in <u>extra</u> resistance in circuit		

5)

(a)	potential difference/current	B1	[1]
(b) (i)	1) 1.13 W 2) 1.50 V	B1	[1]
(ii)	power = V^2 / R or power = VI and $V = IR$ $R = 1.50^2 / 1.13$ = 1.99 Ω	C1 A1	[2]
(iii)	<u>either</u> $E = IR + Ir$ or voltage divided between R and r $I = 1.5 / 2.0$ (=0.75 A) p.d. across $R =$ p.d. Across $r = 1.5$ $3.0 = 1.5 + 0.75r$ $r = 2.0 \Omega$ so $R = r = 1.99 \Omega$	C1 C1 A1	[3]
(c)	larger p.d. across R means smaller p.d. across r smaller power dissipation at larger value of V since power is VI and I is same for R and r	M1 A1 A1	[3]

6)

(a)	both measure (energy / work) / charge for e.m.f., transfer of chemical energy to electrical energy for p.d., transfer of electrical energy to thermal energy / other forms	B1 B1 B1	[3]
(b) (i)	$I_1 + I_2 = I_3$	B1	[1]
(ii)	1. $E_2 = I_2 R_2 + I_3 R_3$ 2. $E_1 - E_2 = I_1 R_1 - I_2 R_2$	B1 B1	[1] [1]

7)

- (a) (i) 1 total resistance = 0.16Ω A1
 2 e.m.f. = *either* $(14 - E)$ or $(E - 14)$ A1 [2]
- (ii) *either* $14 - E = 42 \times 0.16$ or $(E - 14) = -42 \times 0.16$ C1
 $E = 7.3 \text{ V}$ A1 [2]
- (b) (i) charge = It C1
 $= 12.5 \times 4 \times 60 \times 60$
 $= 1.8 \times 10^5 \text{ C}$ A1 [2]
- (ii) *either* energy = EQ or energy = Eit C1
either energy = $14 \times 1.8 \times 10^5$ or energy = $14 \times 12.5 \times 4 \times 3600$
 $= 2.52 \times 10^6 \text{ J}$ A1 [2]
- (iii) energy = I^2Rt or Vit and $V = IR$ C1
 $= 12.5^2 \times 0.16 \times 4 \times 3600$
 $= 3.6 \times 10^5 \text{ J}$ A1 [2]
- (c) efficiency = $(2.52 \times 10^6 - 3.6 \times 10^5)/(2.52 \times 10^6)$ C1
 $= 86\%$ A1 [2]