

(b) (i)	(as temperature rises), resistance of (thermistor) decreases <i>either</i> resistance of parallel combination decreases <i>or</i> p.d. across 5 kΩ resistor / thermistor decreases p.d. across 2000 Ω resistor / voltmeter reading increases	M1 M1 A1	[3]
(ii)	if R is the resistance of the parallel combination, <i>either</i> $3.6 = (2 \times 6) / (2 + R)$ <i>or</i> current in 2 kΩ resistor = 1.8 mA $R = 1.33 \text{ k}\Omega$ current in 5 kΩ resistor = 0.48 mA $\frac{1}{1.33} = \frac{1}{5} + \frac{1}{T}$ current in thermistor = 1.32 mA $T = 1.82 \text{ k}\Omega$ $T = 2.4 / 1.32 = 1.82 \text{ k}\Omega$	C1 C1 C1 A1	[4]
	Total		[6]

1)

(a)	<i>either</i> $V = E R_1 / (R_1 + R_2)$ <i>or</i> $I = E / (R_1 + R_2)$ $= \frac{1800}{3000} \times 4.50$ $V = \frac{1800}{3000} \times 4.50$ $= 2.70 \text{ V}$ $= 2.70 \text{ V}$	C1 M1 A0	[2]
(b) (i)	for a wire, $V = I \times (\rho L/A)$ I, ρ and A are constant so $V \propto L$	M1 A1 A0	[2]

2)

(ii)	1 2.70 V	A1	[1]
	2 $\frac{L}{100} = \frac{2.70}{4.50}$	C1	
	$L = 60.0 \text{ cm}$	A1	[2]
(iii)	thermistor resistance decreases as temperature rises so QM is shorter	M1 A1	[2]

3)

(a)	<i>either</i> $V = IP$ current in circuit = $E / (P + Q)$ hence $V = EP / (P + Q)$	B1 B1 A0	[2]
<i>or</i>	current is the same throughout the circuit (M1) $V/P = E / (P + Q)$ (A1) hence $V = EP / (P + Q)$ (A0)		

- (b) (i) (as temperature rises), resistance of (thermistor) decreases M1
either resistance of parallel combination decreases M1
or p.d. across 5 k Ω resistor / thermistor decreases M1
p.d. across 2000 Ω resistor / voltmeter reading increases A1 [3]
- (ii) if R is the resistance of the parallel combination,
either $3.6 = (2 \times 6) / (2 + R)$ *or* current in 2 k Ω resistor = 1.8 mA C1
 $R = 1.33 \text{ k}\Omega$ current in 5 k Ω resistor = 0.48 mA C1
 $\frac{1}{1.33} = \frac{1}{5} + \frac{1}{T}$ current in thermistor = 1.32 mA C1
 $T = 1.82 \text{ k}\Omega$ $T = 2.4 / 1.32 = 1.82 \text{ k}\Omega$ A1 [4]

For more question on Potential dividers go to theonlinephysicstutor.com a search for question by topic.