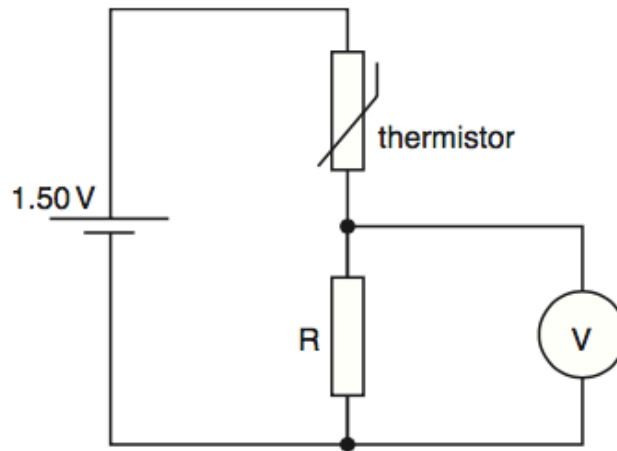


1)

A thermistor has resistance  $3900\ \Omega$  at  $0\ ^\circ\text{C}$  and resistance  $1250\ \Omega$  at  $30\ ^\circ\text{C}$ . The thermistor is connected into the circuit of Fig. 8.1 in order to monitor temperature changes.



**Fig. 8.1**

The battery of e.m.f.  $1.50\ \text{V}$  has negligible internal resistance and the voltmeter has infinite resistance.

**(a)** The voltmeter is to read  $1.00\ \text{V}$  at  $0\ ^\circ\text{C}$ . Show that the resistance of resistor  $R$  is  $7800\ \Omega$ .

[2]

**(b)** The temperature of the thermistor is increased to  $30\ ^\circ\text{C}$ . Determine the reading on the voltmeter.

reading = ..... V [2]

- (c) The voltmeter in Fig. 8.1 is replaced with one having a resistance of  $7800\ \Omega$ . Calculate the reading on this voltmeter for the thermistor at a temperature of  $0\ ^\circ\text{C}$ .

reading = ..... V [2]

2)

A battery of e.m.f. 4.50 V and negligible internal resistance is connected in series with a fixed resistor of resistance  $1200\ \Omega$  and a thermistor, as shown in Fig. 7.1.

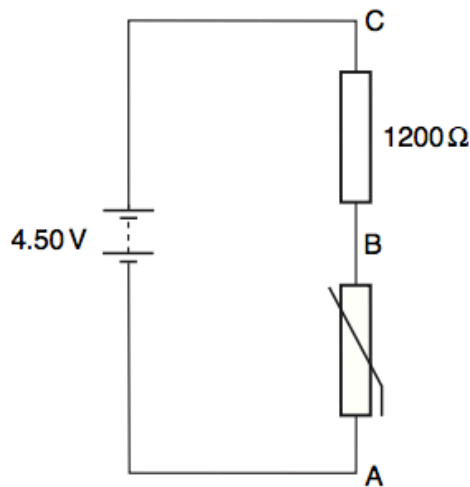


Fig. 7.1

- (a) At room temperature, the thermistor has a resistance of  $1800\ \Omega$ . Deduce that the potential difference across the thermistor (across AB) is 2.70 V.

[2]

- (b) A uniform resistance wire PQ of length 1.00 m is now connected in parallel with the resistor and the thermistor, as shown in Fig. 7.2.

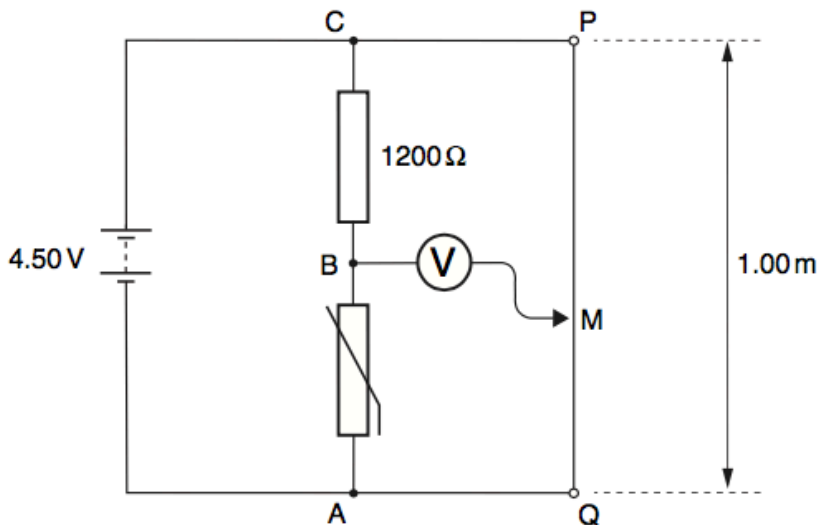


Fig. 7.2

A sensitive voltmeter is connected between point B and a moveable contact M on the wire.

- (i) Explain why, for constant current in the wire, the potential difference between any two points on the wire is proportional to the distance between the points.

.....  
.....  
.....[2]

- (ii) The contact M is moved along PQ until the voltmeter shows zero reading.

1. State the potential difference between the contact at M and the point Q.

potential difference = ..... V [1]

2. Calculate the length of wire between M and Q.

length = ..... cm [2]

- (iii) The thermistor is warmed slightly. State and explain the effect on the length of wire between M and Q for the voltmeter to remain at zero deflection.

.....  
.....  
.....[2]

3)

A potential divider circuit consists of two resistors of resistances  $P$  and  $Q$ , as shown in Fig. 7.1.

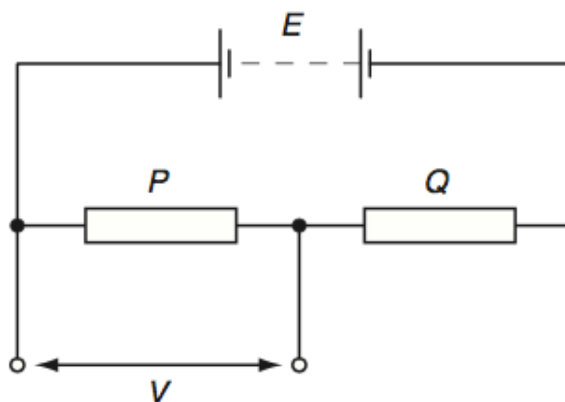


Fig. 7.1

The battery has e.m.f.  $E$  and negligible internal resistance.

- (a) Deduce that the potential difference  $V$  across the resistor of resistance  $P$  is given by the expression

$$V = \frac{P}{P + Q} E.$$

[2]

- (b) The resistances  $P$  and  $Q$  are  $2000\ \Omega$  and  $5000\ \Omega$  respectively. A voltmeter is connected in parallel with the  $2000\ \Omega$  resistor and a thermistor is connected in parallel with the  $5000\ \Omega$  resistor, as shown in Fig. 7.2.

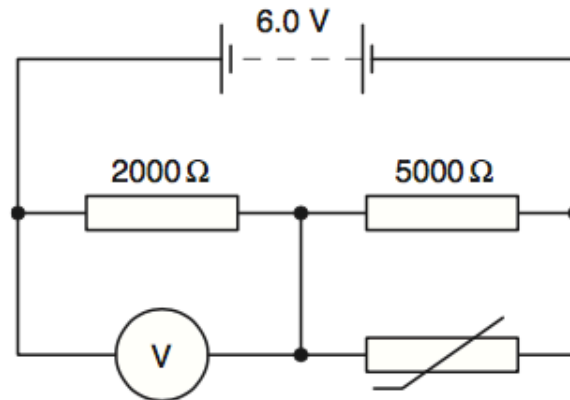


Fig. 7.2

The battery has e.m.f. 6.0V. The voltmeter has infinite resistance.

- (i) State and explain qualitatively the change in the reading of the voltmeter as the temperature of the thermistor is raised.

.....

.....

.....

..... [3]

- (ii) The voltmeter reads 3.6V when the temperature of the thermistor is  $19^\circ\text{C}$ . Calculate the resistance of the thermistor at  $19^\circ\text{C}$ .

resistance = .....  $\Omega$  [4]

For more question on Potential dividers go to [theonlinephysicstutor.com](http://theonlinephysicstutor.com) a search for question by topic.