

Name: _____

Circuits

Mark Scheme

Date:

Time:

Total marks available:

Total marks achieved: _____

Mark Scheme

Q1.

Question Number	Acceptable answers	Additional guidance	Mark
	A The p.d. across the resistor added to the p.d. across the thermistor must equal 6 V. This occurs when the current is 0.5 A.	0.5	1
	B assumes all the p.d. is across the thermistor C assumes that resistor and thermistor connected in parallel D assumes that the p.d. across the resistor and thermistor is more than 6 V		

Q2.

Question Number	Acceptable Answer	Additional Guidance	Mark
	<ul style="list-style-type: none"> • Ammeter in series with LED and voltmeter in parallel with LED (1)		1

Q3.

Question Number	Answer	Mark
	D Step 4	1
	Incorrect Answers: A – this step uses the conservation of energy B – this step is just a statement of Ohm's law C – this step uses the conservation of energy	

Q4.

Question Number	Answer	Mark
	C	1

Q5.

Question Number	Answer	Mark
	D 1080 C	1
	Incorrect Answers: A – current divided by time, with the time in seconds B – current divided by time, with the time in minutes C – correct formula of current \times time but the time is in minutes and not seconds	

Q6.

Question Number	Acceptable answers	Additional guidance	Mark
	A uses the parallel resistors equation $\frac{1}{R_T} = \frac{1}{R} + \frac{1}{R} = \frac{2}{R}$	$\frac{R}{2}$	1
	B assumes resistors in parallel have the same total R as each individual R C is the addition of both resistances as if they were in series D is the product of both resistances		

Q7.

Question Number	Answer	Mark
	B	1

Q8.

Question Number	Answer	Mark
	B	1

Q9.

Question Number	Answer	Mark
	B	1

Q10.

Question Number	Answer	Mark
	$I_3 = I_2 + I_1$ (possible reference to $(Q/t)_1$ etc accepted) (1)	
	Charge is conserved Or Conservation of charge Or charge into point = charge out of point Or no charge lost (1)	
	Correct reference to same time (e.g. same charge etc in same time Or $(Q/t)_3 = (Q/t)_1 + (Q/t)_2$ etc) (1)	3
	Total for question	3

Q11.

Question Number	Answer	Mark
	current same in series Or current is different if not in series (1)	
	to ensure the total resistance in the circuit isn't increased Or to ensure no pd lost (1)	
	because that would reduce the current being measured (1)	3
	[Just saying current changes or resistance changes is not sufficient for MP2 and 3. Candidates who only refer to what would happen if ammeter in parallel can only score MP1]	
	Total for question	3

Q12.

Question Number	Acceptable Answer	Additional Guidance	Mark
	<ul style="list-style-type: none"> The replacement charger will still have to supply the same charge (6510 C) (1) 	MP1: may be awarded for use of 6510 C in a calculation for MP2	
	<ul style="list-style-type: none"> The replacement charging plug takes more time to charge Or the old charging plug takes less time to charge (1) 	MP2 calculation to support this using $t = Q/I$ Or if the phone uses 1A the time to charge will be the same	
	<ul style="list-style-type: none"> Replacement charging plug uses a lower current therefore reduces heating effect (1) 		
	<ul style="list-style-type: none"> The phone may try and draw a current of 1 A which may damage the charging plug (1) 		
			4

Q13.

Question Number	Acceptable Answer	Additional Guidance	Mark
(i)	Use of $3600 \times W \text{ h}$ to give energy stored = 24900 (J) (1)	<u>Example of calculation</u> $6.91 \text{ W h} = 6.91 \times 3600 \text{ s} = 24876 \text{ J}$	1

Question Number	Acceptable Answer	Additional Guidance	Mark
(ii)	<ul style="list-style-type: none"> Use of $V = W/Q$ (1) $Q = 6510 \text{ C}$ (1) 	<u>Example of calculation</u> $Q = \frac{24876 \text{ J}}{3.82 \text{ V}} = 6512 \text{ C}$ (ecf for calculated energy from (a)(i)) (show that value gives $Q = 6545 \text{ C}$)	2

Question Number	Acceptable Answer	Additional Guidance	Mark
(iii)	<ul style="list-style-type: none"> Use of $Q = It$ Or $W = VIt$ (1) Use of $\frac{\text{time in seconds}}{3600}$ (1) $t = 2.0 \text{ (h)}$ (1) 	<u>Example of calculation</u> $t = \frac{6512 \text{ C}}{0.9 \text{ A}} = 7235.6 \text{ s}$ $t = \frac{7235.6 \text{ s}}{3600} = 2.01 \text{ h}$ (ecf for calculated charge from (a)(i)) (show that value gives $t = 2.02 \text{ h}$)	3

Q14.

(d)	Lower resistance	(1)	4
	(smaller current, so) lower temperature (so less vibration of lattice ions) Or (smaller current, so) smaller drift velocity	(1)	
	fewer collisions of electrons with lattice ions Or less frequent collisions of electrons with lattice ions	(1)	
	Less energy dissipation (as heat) Or less ke lost in collisions	(1)	
Total for question			15