



Resistors

Mark Scheme

Name: _____

Class: _____

Date: _____

Time: **87 minutes**

Marks: **86 marks**

Comments:

Mark schemes

- 1** level drops as petrol used;
causes circuit resistance to increase;
causes current to decrease

for 1 mark each

or if change not specified;
(one correct and two vague statements gains 2 marks,
three vague statements gains 1 mark)
e.g. level changes;)
so resistance changes;) = 1 mark
so current changes)

[3]

- 2** (a) electric current
(rate of) flow of (electric) charge / electrons

$$\text{accept } I = \frac{Q}{t}$$

with Q and t correctly named

1

potential difference

work done / energy transferred per coulomb of charge
(that passes between two points in a circuit)

$$\text{accept } V = \frac{W}{Q}$$

with W and Q correctly named

1

- (b) metals contain free electrons (and ions)
accept mobile for free

1

as temperature of filament increases ions vibrate faster /
with a bigger amplitude

accept atoms for ions

accept ions/atoms gain energy

accept vibrate more for vibrate faster

do not accept start to vibrate

1

electrons collide more (frequently) with the ions

or

(drift) velocity of electrons decreases

do not accept start to collide

accept increasing the p.d. increases the temperature (1 mark)

and

(and) resistance increases with temperature (1 mark) if no other marks scored

1

(c) 7.8

allow 1 mark for obtaining value 1.3 from graph

or allow 1 mark for a correct calculation using an incorrect current in the range 1.2-1.6 inclusive

2

[7]

3

(a) (i) 2

allow 1 mark for correct substitution i.e. 0.8×2.5 provided no further step shown

2

(ii) straight line drawn from origin to 2, 0.8

or

their (a)(i), 0.8

1

curve from 2, 0.8 to 12,2

or

their (a)(i) 0.8 to 12,2

accept curve from 2, 0.9 to 12,2

or

their (a)(i) 0.9 to 12,2

'convex' curve required

accept a curve that flattens between 10 and 12V

1

(iii) filament / lamp gets hot

accept temperature increases

1

(b) 108

allow 1 mark for correct substitution i.e. 1.5×72 provided no further step shown

2

[7]

4

(a) diode

accept LED

1

- (b) all symbols correct
must include at least voltmeter and diode

1



allow ecf from part (a) if the component is not identified as a diode
allow symbol without the line through triangle
ignore polarity of diode

voltmeter in parallel with component added in series
any additional components must not affect the ability to measure V and I for the diode / their (a)

1

- (c) (i) 0.05
accept 50 mA
accept between 0.048 and 0.050 inclusive

1

- (ii) 16

$$\frac{0.8}{0.05}$$
their (c)(i) correctly calculated gains both marks
allow 1 mark for correct transformation and substitution


$$\frac{0.8}{0.05} \text{ or } \frac{0.8}{\text{their (c)(i)}}$$
allow 17 if using 0.048

2

[6]

5

- (a) (i)

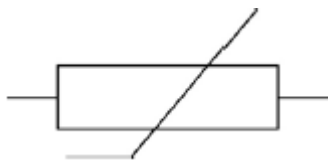


1

- (ii) 360
allow 1 mark for correct substitution, ie $9 = 0.025 \times R$

2

(iii) sketch graph of correct shape, ie

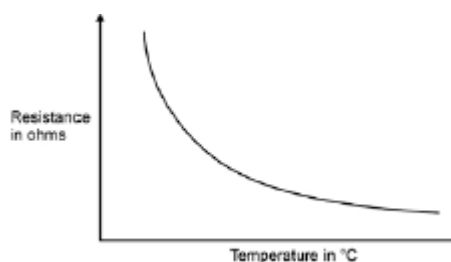

1

(iv) An automatic circuit to switch a heating system on and off.

1

(b) so ammeter reduces / affects current as little as possible

accept so does not reduce / change the current (it is measuring)

accurate reading is insufficient

not change the resistance is insufficient

1

(c) gives a common understanding

accept is easier to share results

accept can compare results

do not need to be converted is insufficient

prevent errors is insufficient

1

(d) replace Bunsen (and water) with a lamp

accept any way of changing light level

1

replace thermometer with light sensor

accept any way of measuring a change in light level

datalogger alone is insufficient

1

[9]

6

(a) (i) light dependent resistor / LDR

accept ldr

1

(ii) 25 (kilohms)

accept 24 - 26 inclusive

accept 25 000 Ω

1

(iii) 5 (V) or their (a)(ii) correctly converted to ohms $\times 0.0002$ correctly calculated

allow 1 mark for converting 25 k Ω /

their (a)(ii) to ohms

or

allow 1 mark for correct substitution

ie 0.0002 \times 25(000)

or 0.0002 \times their (a)(ii)

allow an incorrect conversion from kilohms providing this is clearly shown

2

(b) (i) linear scale

using all of the available axis

must cover the range 4 - 6 v

or their (a)(iii) - 6 v and lie within the range 0 - 15 inc.

1

(ii) negative gradient line

*do **not** allow lines with both positive and negative gradients*

1

passing through 20 lux and their (a)(iii)

only scores if the first mark is awarded

only scores if line does not go above 6 volts

1

(c) (i) 37.5 (k Ω) or their (a)(ii) + 50 % (a)(ii) correctly calculated

1

(ii) light intensity value would be unreliable / not accurate

1

due to variation in resistance value

accept because resistance varies by ± 50 %

accept tolerance of resistor is too great

*do **not** accept results are not accurate*

1

[10]

7

- (a) ordinary cell has higher voltage (normally / at start)

or

ordinary cell 1.3V nicad 1.2V (normally / at start)

for 1 mark

voltage of ordinary cell falls more slowly

gains 1 mark

(*accept* ordinary cell lasts longer)

but

as above with relevant quantification e.g. falls to zero in 60 seconds compared to 6 seconds

or

nicad falls to zero 10 times as fast

gains 2 marks

3

- (b) (i) answer in range 32-34 (seconds) (inclusive)

gains 1 mark

but

answer in range 22-24 (seconds) (inclusive)

gains 2 marks

- (ii) 12 (seconds)

gains 1 mark

but

2 (seconds)

gains 2 marks

4

- (c) resistance of the lamp / filament changes / increases

gains 1 mark

but

resistance of the lamp / filament decreases

gains 2 marks

because the temperature of the filament falls / filament cools


for 1 mark

3

[10]

8

(a)

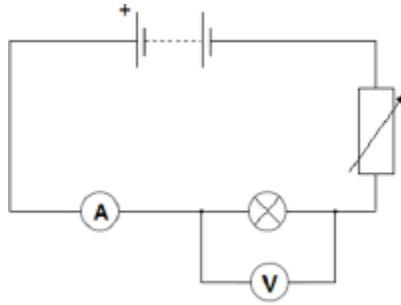

battery in series with bulb and ammeter

1

voltmeter in parallel with bulb

1

variable resistor

or

variable power pack

or

potentiometer

1

(b) A is brighter because it has a higher current (than lamp B at any p.d.)

1

(therefore A has a) higher power output (than bulb B)

accept higher energy output per second

1

(c) lower current (than lamp A) for the same potential difference

accept answer in terms of $R = V / I$

1

lower gradient (than lamp A)

1

(d) 0 – 2 Volts

allow a range from 0 V up to any value between 1 and 2 V.

1

(for an ohmic conductor) current is directly proportional to potential difference

allow lines (of best fit) are straight and pass through the origin

1

(so) resistance is constant

1

[10]

9

(a) Current = 0.4A (1)

$R = V/I$ or $240/0.4$ (1)




$R = 600$ ohm (1)

3

- (b) Doubles
gets 2 marks
 OR gets bigger
gets 1 mark 2
- (c) $P = V.I$ or 240×0.4
 $P = 96W$
for 1 mark each 2
- (d) $I = 0.2A$
 $P = 48W$
for 1 mark each
BUT may get equation mark here if not in (c) 2
- (e) $P = V.I.t$ (1)
 $P = 240 \times 0.2 \times 6 \times 3600$
OR $P = 48 \times 6 \times 3600$
gets 1 mark
 $P = 1036800 W$
gets 1 mark 3

[12]

10

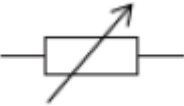- (a) (i) symbol for a diode  1
- accept*  1
- symbol for a variable resistor  1
- (ii) voltmeter is in series **or** voltmeter is not in parallel 1
- ammeter is in parallel **or** ammeter is not in series
accept an answer in terms of how the circuit should be corrected
voltmeter and ammeter are wrong way around is insufficient 1
- (b) (i) 0.2 (V)
accept any value between 0.20 and 0.21 inclusive 1

(ii) 37.5

allow 1 mark for $I = 0.008$ **or***allow 2 marks for correct substitution, ie $0.3 = 0.008 \times R$* **or***allow 1 mark for a correct substitution using $I = 0.8$ **or** $I = 0.08$* **or** $I = 0.009$ **or***allow 2 marks for answers of 0.375 **or** 3.75 **or** 33(.3)*

3

(c) (i) 25

allow 1 mark for obtaining period = 0.04(s)

2

(ii) diode has large resistance in reverse / one direction

1

so stops current flow in that / one direction

*allow diodes only let current flow one way / direction**allow 1 mark for the diode has half-rectified the (a.c. power) supply*

1

[12]