


Mark schemes

- 1** (a) 25( $\Omega$ ) 1
- (b) (i) 2(V) 2  
*allow 1 mark for showing a correct method, ie 6 / 3*
- (ii) equal to 1
- [4]**

- 2** (a) switch 1  
*allow answer circled in box*
- (b) 24 1
- (c) equal to 0.25 A 1
- (d) 4 1
- [4]**

**3**

(a)

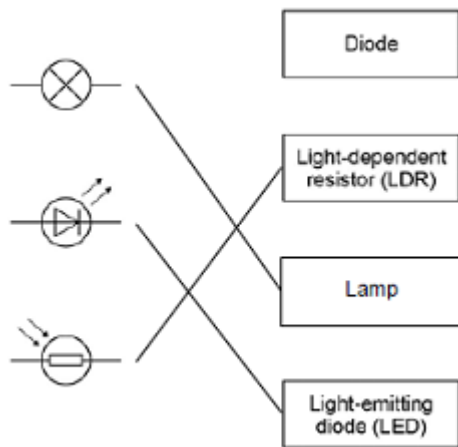

allow 1 mark for each correct line if more than one line is drawn from any symbol then all of those lines are wrong

3

(b) (i) half

1

(ii) 3(V)

1

(iii)  $V_1$

1

(c) (i) potential difference / voltage of the power supply

*accept the power supply*

*accept the voltage / volts*

*accept number of cells / batteries*

*accept (same) cells / batteries*

*do not accept same ammeter / switch / wires*

1

(ii) bar drawn – height 1.(00)A

*ignore width of bar*

*allow 1 mark for bar shorter than 3<sup>rd</sup> bar*

2

(iii) as the number of resistors increases the current decreases

1

[10]

**4**

(a) (i) 15

1

(ii) 4.5 or their (a)(i) x 0.3 correctly calculated

*allow 1 mark for correct substitution, ie 0.3 x 15/their (a)(i), provided no subsequent step*

2

(ii) decrease

(b) **Y**

*accept any correct indication*  
*reason only scores if Y is chosen*  
*accept voltage for p.d.*

1

(only one that) shows a direct current / p.d.

**or**

a battery / cell gives a direct current

*accept both X and Z are a.c.*

**or**

a battery/cell gives a constant current/p.d.

*accept it's a constant current/p.d.*  
*it is not changing is insufficient*

1

[6]

**5**

(a) current that is always in the same direction

1

(b) total resistance = 30 ( $\Omega$ )

1

$$V = 0.4 \times 30$$

1

12 (V)

1

*allow 12 (V) with no working shown for 3 marks*  
*an answer of 8 (V) or 4 (V) gains 2 marks only*

(c)  $P = 0.4 \times 12 = 4.8$

1

5 (W)

1

*allow 5 (W) with no working shown for 2 marks*  
*allow 4.8 (W) with no working shown for 1 mark*

[6]

**6**

(a)  $V = 0.10 \times 45$

1

4.5 (V)

1

(b)  $R = 12 / 0.10$

1

total resistance = 120 ( $\Omega$ )

1

$$R = 120 - 105 = 15 (\Omega)$$

(c) (total) resistance decreases

1

(so) current increases

1

[7]

7

(a)  $97\,500 = 65.0 \times t$

1

$$t = \frac{97500}{65.0}$$

1

$t = 1500$  (s)

*an answer of 1500 (s) scores 3 marks*

*an answer of 1.5 scores 2 marks*

1

(b)  $19.6 = I^2 \times 1.60$

1

$$I^2 = \frac{19.6}{1.60}$$

1

$I = 3.5$  (A)

*allow 1 mark for a correct value for I correctly multiplied by 4*

1

current through battery = 14 (A)

*an answer of 14 (A) scores 4 marks*

1

[7]

8

(a) 35

*an answer with more than 2 sig figs that rounds to 35 gains 2 marks*

*allow 2 marks for correct method, ie  $\frac{230}{6.5}$*

*allow 1 mark for  $I = 6.5$  (A) or  $R = \frac{230}{26}$*

*an answer 8.8 gains 2 marks*

*an answer with more than 2 sig figs that rounds to 8.8 gains 1 mark*

3

(b) (maximum) current exceeds maximum safe current for a  $2.5 \text{ mm}^2$  wire

*accept power exceeds maximum safe power for a  $2.5 \text{ mm}^2$  wire*

**or**

(maximum) current exceeds 20 (A)

*(maximum) current = 26 (A) is insufficient*

1

a 2.5 mm<sup>2</sup> wire would overheat / melt

*accept socket for wire*

*do not accept plug for wire*

1

(c) a.c. is constantly changing direction

*accept a.c. flows in two directions*

*accept a.c. changes direction*

*a.c. travels in different directions is insufficient*

1

d.c. flows in one direction only

1

[7]

9

(a) filament bulb

1

(b) (i) 6 V

1

(ii) 3 Ω or their  $\frac{(i)}{2}$  correctly calculated  
*allow 1 mark for correct substitution ie*  
 $6 = 2 \times R$   
*or their (i) = 2 × R*

2

(iii) 1 A

1

(iv) 6 Ω or their (i) / their (iii) correctly calculated

1

(v)

Decrease	Stay the same	Increase
	✓	
✓		
✓		

1


1

1

[9]

10

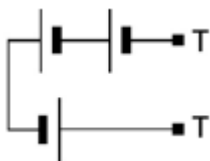- (a) 3
- <sup>rd</sup>
- box from the left ticked



1

- (b) correct symbol drawn in series with other components
- 
- symbol must have upper case A*

1

- (c) (i)
- $9 + 3 = 12V$
- 
- reason only scores if this mark scored*

1

pd of battery is shared between the variable resistor and fixed resistor

*accept  $V_1 + V_2 = \text{pd of the battery}$* *accept p.d. is shared in a series circuit**accept voltage for p.d.*

1

- (ii) 600
- 
- reason only scores if this mark scored*

1

p.d. of supply shared equally when resistors have the same value

**or**

ratio of the p.d. is the same as the ratio of the resistance

1

- (iii) 0.015
- 
- or**
- 
- their (c)(i)
- $\div$
- (their (c)(ii) + 200) correctly calculated
- 
- allow 2 marks for correct substitution ie  $12 = I \times 800$*

**or***their (c)(i) =  $I \times (\text{their (c)(ii) + 200}$* *allow 1 mark for total resistance =  $800 (\Omega)$  or their (c)(ii) + 200***or***allow 1 mark for a substitution of  $12 = I \times 200$* **or***their (c)(i) =  $I \times 200$* **or***alternative method using the graph*

$$V = 3 \text{ V (1)}$$

$$3 = I \times 200 \text{ (1)}$$

3

[9]

**11**

- (a) current at 0.5 V = 0.91 (A)

1

$$P = 0.91 \times 0.5$$

1

$$P = 0.455 \text{ (W)}$$

*an answer of 0.455 (W) scores 3 marks*

1

- (b) straight line with positive gradient

*allow for 1 mark a straight line that passes through (0.1, 0)*

1

positive y-axis intercept

*ignore any values on y-axis*

1

(c) 
$$0.15 = \frac{0.52}{\text{total } P}$$

1

total P = 3.47 (W)

1

area =  $\frac{3.47}{450}$

1

area =  $7.7 \times 10^{-3} \text{ (m}^2\text{)}$

*an answer of  $7.7 \times 10^{-3} \text{ (m}^2\text{)}$  scores 4 marks**allow use of student's calculated incorrect total power for last 2 marking points*

1

- (d) connect the solar cells in parallel

1

(so that) the current has multiple paths it can take

**or**

the total resistance is less than the resistance of one solar cell

1

**[11]**