

1)

Question	Expected Answer	Mark	Additional Guidance
(a)	coulomb <u>per</u> volt	B1	Allow: 1 F = 1 $\frac{CV}{V}$
(b) (i)	<u>Electrons</u> flow 'clockwise' / negative to positive These are deposited on (plate) A (and hence becomes negatively charged) or These are removed from (plate) B (and hence become positively charged)	B1 B1	Not: A becomes negative / B becomes positive
(ii)1	$Q = C \times V = 5.4 \times 10^{-9} \times 12$ charge = 6.48×10^{-8} (C)	B1	
(ii)2	energy = $\frac{1}{2}V^2C = \frac{1}{2} \times 12^2 \times 5.4 \times 10^{-9}$ energy = 3.89×10^{-7} (J)	B1	Possible ecf if Q used from (ii)1
(c) (i)	$R = \frac{12}{3.24 \times 10^{-6}}$ resistance = 3.7×10^6 (Ω)	M1 A0	Allow: 'R = 12/3.24 μ ' (= 3.7 M Ω)
(ii)	time constant = CR = $5.4 \times 10^{-9} \times 3.7 \times 10^6$ or 0.02 (s) $I = I_0 e^{-t/CR} = 3.24 \times e^{-(0.080/0.020)}$ current = 0.059 (μ A)	C1 A1	Allow: ecf for time constant Allow: 1 mark for 5.9×10^{-1}
(d)	(Total) resistance of circuit <u>halved</u> / time constant is <u>halved</u> Rate of discharge is <u>doubled</u> / (initial) current is <u>doubled</u>	B1 B1	
	Total	10	

2)

Question	Answers	Marks	Guidance
(a)	capacitance = charge/p.d. or capacitance = charge per (unit) p.d.	B1	Allow: voltage instead of p.d. Note: Do not allow mixture of quantity and unit, e.g. 'charge per (unit) volt'
(b) (i)	$C_{\text{parallel}} = 240$ (μ F) $C_T = (240 \times 120)/(240 + 120)$ or $C_T = (240^{-1} + 120^{-1})^{-1}$ total capacitance = 80 (μ F)	C1 C1 A0	Allow : 1 mark if C_T is not the subject, e.g: $\frac{1}{C_T} = \frac{1}{240} + \frac{1}{120}$
(ii)	$E = \frac{1}{2}V^2C$ $E = \frac{1}{2} \times 6.0^2 \times 80 \times 10^{-6}$ energy = 1.4×10^{-3} (J) or 1.44×10^{-3} (J)	C1 A1	Possible ecf Allow: 1 mark for an answer 1.44×10^n ($n \neq -3$)
(iii)1	$6.0/e = 2.2$ (V) (as on graph) Or $6.0 \times 0.37 = 2.2$ (V) (as on graph) Or At 20 (s), $V = 2.2$ (V), $2.2/6.0 = 0.37$ (or e^{-1})	B1	Allow: Graph reading within ± 0.2 V
(iii)2	$CR = 20$ $R = \frac{20}{80 \times 10^{-6}}$ $R = 2.5 \times 10^5$ (Ω)	C1 A1	Allow: Follow through with CR value from (iii)1
	Total	8	

3)

Question	Answer	Marks	Guidance
(a)	(farad = 1) coulomb per (unit) volt	B1	Allow: C V ⁻¹
(b)	(i) 1/C	B1	Allow: 'inverse of C'
	(ii) work (done) / energy	B1	
(c)	Diagram: All 3 capacitors connected in series $\frac{1}{C} = \frac{1}{100} + \frac{1}{200} + \frac{1}{500} \quad / \quad \frac{1}{C} = 1.7 \times 10^{-2}$ capacitance = 59 (μF)	B1 C1 A1	Note: Correct symbol must be used for capacitor and at least one of the capacitance values (without the unit) must be shown Allow: Answer to 1 sf Note: Answer to 3sf is 58.8 (μF) Allow: 1.7 × 10 ⁻² (μF) scores 1 mark from the C1A1
(d)	(i) Q = 0.040 × 60 charge = 2.4 (C)	C1 A1	Allow: 1 mark for 2.4 × 10 ⁿ , n ≠ 0 (POT error)
	(ii) energy = $\frac{1}{2} \times \frac{2.4^2}{0.10}$ energy = 29 (J)	C1 A1	Possible ecf from (d)(i) Note: Answer to 3 sf is 28.8 (J) Allow full credit for correct use of ½ VQ or ½ V ² C; the final p.d is 24 (V)
Total		10	

4)

Question	Expected Answers	Marks	Additional guidance
(a)	capacitance = charge / potential difference	B1	Allow: p.d. and voltage Not: charge per volt or coulombs per p.d
(b)	(i) V = Q/C and Q = constant in series circuit $V = \frac{450}{450 + 150} \times 6.0$ potential difference = 4.5 (V)	C1 A1	Allow: 1 mark for an answer of 1.5 (V) Note: Using (b)(ii), alternative marking scheme V = 6.75 × 10 ⁻⁴ / 150 × 10 ⁻⁶ C1 V = 4.5 V A1
	(ii) charge = 150 × 10 ⁻⁶ × 4.5 charge = 6.75 × 10 ⁻⁴ (C)	B1	Possible e.c.f. Note: Using (b)(iii) ... Q = 6.0 × 1.125 × 10 ⁻⁴ = 6.75 × 10 ⁻⁴ (C)
	(iii) $\frac{1}{C} = \frac{1}{150} + \frac{1}{450}$ (working in μF) capacitance C _T = 1.125 × 10 ⁻⁴ (F) or 113 μ(F)	B1	Possible alternative: capacitance = 6.75 × 10 ⁻⁴ / 6.0 capacitance = 1.125 × 10 ⁻⁴ (F) or 113 μ(F) Possible e.c.f. from (ii)
(c)	(i) time constant = CR time constant = 1.125 × 10 ⁻⁴ × 45 × 10 ³ time constant = 5.06 (s)	M1 A0	Note: The mark is for multiplying correct C and R values Possible e.c.f. from (b)(iii)
	(ii) Graph starting from 6.0 (V) Correct shaped curve Approximately correct value of V at CR	B1 B1 B1	Note: The (exponential decay) curve must not touch or cut the time axis Note: V is 2 to 2.5 (V) at t ≈ 5 s

Question	Expected Answers	Marks	Additional guidance
(iii)	$\frac{1}{2} \times 4.5^2 \times 150 \times 10^{-6}$ and $\frac{1}{2} \times 1.5^2 \times 450 \times 10^{-6}$ ratio = $\frac{0.5 \times 4.5^2 \times 150 \times 10^{-6}}{0.5 \times 1.5^2 \times 450 \times 10^{-6}}$ ratio = 3 Or $\frac{1}{2} Q^2/C_{150}$ and $\frac{1}{2} Q^2/C_{450}$ ratio = C_{450} / C_{150} ratio = 3	C1 A1 C1 A1	Allow: with or without the 10^{-8} Possible e.c.f. from (b)(i) and (b)(ii) Allow: full credit for correct use of either $\frac{1}{2}QV$ or $\frac{1}{2}Q^2/C$
(iv)	The ratio remains constant The charge / Q is the same for both capacitors	B1 B1	
Total		13	

5)

Question	Answers	Marks	Guidance
(a)	The time taken for the p.d / current / charge to decrease to $1/e$ of its (initial) value.	B1	Allow 37% instead of $1/e$. Not time constant = CR on its own.
(b)	Any suitable values with units, eg: 5 M Ω and 1 μ F.	B1	
(c) (i)	$R = \frac{4.9 \times 10^{-7} \times 5.0}{\pi \times (0.06 \times 10^{-3})^2}$ or $R = 217 (\Omega)$ time constant = 0.010×217 time constant = 2.2 (s)	C1 C1 A1	Note: An incorrect equation here for A prevents this and any subsequent marks. Allow 2 marks for 0.54 (s) – diameter of 0.12 mm used instead of radius 0.06 mm.
(ii)	Electrons are removed from X or electrons are deposited on Y. X becomes positive or Y becomes negative (The size of charge is the same because) an equal number of electrons are removed and deposited (on the plates).	B1 B1 B1	Allow electrons move anticlockwise (in the circuit). There is no ecf from the previous B1 mark.
(iii)	$E = \frac{1}{2} \times 0.010 \times 12^2$ or $E = 0.72$ (J) $m = 8900 \times [\pi \times (0.06 \times 10^{-3})^2 \times 5.0]$ or $5.0(3) \times 10^{-4}$ (kg) $5.03 \times 10^{-4} \times 420 \times \Delta\theta = 0.72$ increase in temperature = 3.4 ($^{\circ}$ C)	C1 C1 C1 A1	Note: An incorrect equation here for m or V prevents this and any subsequent marks. Correct substitution into $mc\Delta\theta = 0.72$; allow any subject. Note: Do not penalise using diameter here again if already penalised in (c)(i).
(iv)	Energy or V^2 increases by a factor of 4. The (change in temperature) increases by a factor of 4 (because $\Delta\theta \propto E$).	B1 B1	Allow the label E or W for energy. Allow $\Delta\theta = 13.6$ ($^{\circ}$ C) for this B1 mark - possible ecf from (iii).
Total		14	

6)

Question	Answer	Marks	Guidance
(a) (i)	Correct shape of (exponential) decay curve (labelled L)	B1	Note: The curve must show a gradient of decreasing magnitude as time increases and appear to have a finite value of V at $t = 0$ Ignore any levelling of the curve or $V = 0$ towards the end
(ii)	Correct shape of curve (labelled H)	B1	Note: As (i) and this curve must show a smaller time constant than (i); the initial V can be different Note: One of the curves must be labelled
(iii)	Correct explanation in terms of constant-ratio for V values for <u>fixed</u> intervals of t	B1	Allow V is halved every half-life; V decreases to 0.37 (of its initial value) after every time constant Note: This can be scored on a suitably labelled sketch graph in either (iii) or Fig. 4.1
(b) (i)	(time constant = $6.9 \times 10^{-6} \times 240$) time constant = 1.7×10^{-3} (s)	B1	Note: Answer to 3 sf 1.66×10^{-3} (s)
(ii)	charge = $6.9 \times 10^{-6} \times 1.4$ (= 9.66×10^{-6} C) $(\Delta t = 1/120 = 0.0083 \text{ s})$ current = $\frac{6.9 \times 10^{-6} \times 1.4}{0.0083}$ current = 1.2×10^{-3} (A)	C1 C1 A1	Possible ecf from (b)(i) for value of total capacitance Note: Answer to 3 sf 1.16×10^{-3} (A) Allow: 2 marks for $9.66 \times 10^{-6} \times 60 = 5.8 \times 10^{-4}$ (A); $\Delta t = 1/60$ s used Allow: 2 marks for $9.66 \times 10^{-6} \times 240 = 2.3 \times 10^{-3}$ (A); $\Delta t = 1/240$ s used
(iii)	The capacitors do not fully discharge (AW) Any <u>one</u> from: <ul style="list-style-type: none"> Period (of switching) is (halved to) 4.2×10^{-3} (s) (and this time is comparable to the time constant) The time constant (of the circuit) and period of mechanical switch are comparable / similar 	B1 B1	
Total		9	

7)

Question	Answer	Marks	Guidance
(a)	Series branch: Using $(100^{-1} + 300^{-1})^{-1}$ and $C = 75$ (μF) capacitance = $500 + 75$ capacitance = 575 (μF)	C1 A1	Possible ecf, if capacitance of series branch is incorrect
(b) (i)	Time constant method: 37% of 6.0 V is 2.2 V. The time taken to reach 2.2 V is equal to the time constant time constant = 60 (s) / CR = 60 (s) $500 \times 10^{-6} \times R = 60$ $R = \frac{60}{500 \times 10^{-6}}$ resistance = 1.2×10^5 (Ω) Substitution method: Correct values for p.ds and t substituted into $V = V_0 e^{-\frac{t}{CR}}$ Correct values substituted into $\ln(V/V_0) = -\frac{t}{CR}$ resistance = 1.2×10^5 (Ω)	C1 C1 A1 C1 C1 A1	Note: Allow full credit for other correct methods Allow: time constant in the range 58 s to 62 s Deduct 1 mark for misreading graph followed by ecf Note: If C value from (a) is used, then deduct 1 mark followed by ecf Eg: $2.2 = 6.0 e^{-\frac{60}{CR}}$ - values read to ± 1 small square Eg: $\ln(2.2/6.0) = -\frac{60}{500 \times 10^{-6} \times R}$ Note: If C value from (a) is used, then deduct 1 mark followed by ecf. Using 575 (μF) gives 1.04×10^5 (Ω)
(ii)	Correct p.ds from graph: 6 (V) and 3.6 (V) $\frac{1}{2} \times 500 \times 10^{-6} \times 6.0^2$ or $\frac{1}{2} \times 500 \times 10^{-6} \times 3.6^2$ energy is 9.00×10^{-3} (J) and 3.24×10^{-3} (J) energy lost = 5.76×10^{-3} (J) or 5.8×10^{-3} (J)	C1 C1 A1	Allow V value to be in the range 3.5 V to 3.7 at 30s Note: Do not penalise 10^n error from (b)(ii) again here Allow 1 mark for: $\frac{1}{2} \times 500 \times 10^{-6} \times (6.0 - 3.6)^2 = 1.44 \times 10^{-3}$ (J) Note: Do not penalise use of 575 μF again. This gives a value of 6.62×10^{-3} (J)
Total		8	

8)

Question	Expected Answers	Marks	Additional Guidance
a	Capacitance = charge per (unit) potential difference	B1	Allow: capacitance = charge / potential difference, charge/pd, charge/voltage but not charge / volt, coulomb /pd (no mixture of quantities and units. Allow 'over' instead of per
b (i)	$Q = CV = 4.5 \mu \times 6.3 = 28.(35) (\mu C)$	B1	Allow: 28 (≥ 2 sf)
(ii)	$E = \frac{1}{2} CV^2 = 0.5 \times 4.5 \mu \times (6.3)^2$ $= 8.9(3) \times 10^{-5} (J) / 89.3 \mu(J)$	C1 A1	Allow use of $E = \frac{1}{2} QV$ and the Q value from (b)(i) $Q=28 E= 8.82$ and $Q=28.4 E=8.946$ Allow ecf from (b)(i) penalise power of ten error (-1)
c (i)	Electrons / they move in an anticlockwise direction Charge on plates decreases / electrons neutralise positive charge p.d. decreases <u>exponentially</u>	B1 B1 B1	Alternatives for anticlockwise: from / lower plate around the circuit, from / lower plate through the resistor to top plate implied Capacitor discharges / loses charge
(ii)	(dissipated as heat) in the resistor / wires	B1	
d (i)	Total capacitance = $1.5 + 4.5 = 6.(0) (\mu F)$	A1	Allow one SF
(ii)	Original charge on $4.5 \mu F$ capacitor is conserved ($28.35 \mu C$) $V = (28.35 \mu) / (1.5 + 4.5) \mu = 4.7 (V)$	C1 A1	ecf from (b)(i) and (d)(i)
Total		[11]	

9)

Question	Answer	Marks	Guidance
(a) (i)	Any <u>two</u> from: Correct direction of movement of electrons Electrons deposited on Y / removed from X An equal number of electrons removed and deposited on plates (AW)	B1 x 2	
(ii)1	$Q = 40 \times 10^{-6} \times 100 (= 4.0 \times 10^{-3} C)$ $4.0 \times 10^{-3} = 1.6 \times C$ $C = 2.5 \times 10^{-3} (F)$	C1 C1 A1	Allow: 2 marks for $2.5 \times 10^n (F)$, where $n \neq -3$ (POT error)
(ii)2	Graph starts at <u>origin</u> and has positive gradient A straight line graph that passes between 1-2 V at 100 s	M1 A1	
(b) (i)	$CR = 4.7 \times 10^{-6} \times 220 (= 1.03 \times 10^{-3} s)$ $4.00 = 6.00e^{-\frac{t}{1.03 \times 10^{-3}}}$ $t = -\ln(4.00/6.00) \times 1.03 \times 10^{-3}$ time = $4.2 \times 10^{-4} (s)$	C1 C1 A1	Note: Answer to 3 sf is $4.19 \times 10^{-4} (s)$ Allow: 2 marks for $t = -\ln(4.00/6.00) \times 1.03 \times 10^{-3} = 1.8 \times 10^{-4} s$
(ii)	speed = $\frac{0.100}{4.2 \times 10^{-4}}$ speed = $240 (m s^{-1})$	B1	Possible ecf from (b)(i)
Total		11	

10)

Question	Expected Answers	Marks	Additional Guidance
a	Capacitance = charge per (unit) potential difference	B1	Allow: capacitance = charge / potential difference, charge/pd, charge/voltage but not charge / volt, coulomb /pd (no mixture of quantities and units. Allow 'over' instead of per
b (i)	$Q = CV = 4.5 \mu \times 6.3 = 28.(35) (\mu\text{C})$	B1	Allow: 28 (≥ 2 sf)
(ii)	$E = \frac{1}{2} CV^2 = 0.5 \times 4.5 \times \mu \times (6.3)^2$ $= 8.9(3) \times 10^{-5} (\text{J}) / 89.3 \mu(\text{J})$	C1 A1	Allow use of $E = \frac{1}{2} QV$ and the Q value from (b)(i) $Q=28 E= 8.82$ and $Q=28.4 E=8.946$ Allow ecf from (b)(i) penalise power of ten error (-1)
c (i)	Electrons / they move in an anticlockwise direction Charge on plates decreases / electrons neutralise positive charge p.d. decreases <u>exponentially</u>	B1 B1 B1	Alternatives for anticlockwise: from / lower plate around the circuit, from / lower plate through the resistor to top plate implied Capacitor discharges / loses charge
(ii)	(dissipated as heat) in the resistor / wires	B1	
d (i)	Total capacitance = $1.5 + 4.5 = 6(.0) (\mu\text{F})$	A1	Allow one SF
(ii)	Original charge on $4.5 \mu\text{F}$ capacitor is conserved ($28.35 \mu\text{C}$) $V = (28.35 \mu) / (1.5 + 4.5) \mu = 4.7 (\text{V})$	C1 A1	ecf from (b)(i) and (d)(i)
Total		[11]	