

1)

Question	Expected Answers	Marks	Additional Guidance
<b>a</b>	resistors in series add to 20 $\Omega$ and current is 0.60 A so p.d. across XY is $0.60 \times 12 (= 7.2 \text{ V})$	B1 B1	<b>accept</b> potential divider stated <b>or</b> formula gives $(12/20) \times 12 \text{ V} (= 7.2 \text{ V})$
<b>b</b>	<b>i</b> the resistance of the LDR decreases (so total resistance in circuit decreases) and current increases	M1 A1	
	<b>ii</b> resistance of LDR and 12 $\Omega$ (in parallel)/across XY decreases so has smaller share of supply p.d. (and p.d. across XY falls)	B1 B1	<b>alternative</b> I increases so p.d. across 8.0 $\Omega$ increases; so p.d. across XY falls
<b>Total question 3</b>		<b>6</b>	

2)

<b>(a)</b>	<b>(i)</b>	$I = V/R = 8.0/200$ $I = 0.040 \text{ (A)}$	C1 A1	
	<b>(ii)</b>	$V = 24 - 8 = 16 \text{ (V)}$	B1	
	<b>(iii)</b>	$R = 16/0.04$ giving $R = 400 \text{ (}\Omega\text{)}$	C1 A1	<b>accept</b> ratio of p.d.s to ratio of Rs <b>ecf</b> from (i) & (ii) ie (a)(ii)/(a)(i)
	<b>(iv)</b>	$P = VI = I^2R = V^2/R$ $P = 0.640 \text{ (W)}$	C1 A1	<b>ecf</b> from (i) & (ii) <b>accept</b> 640 mW
<b>(b)</b>	<b>(i)</b>	the thermistor has heated up/ its temperature has increased so its resistance has dropped so the ratio of the voltages across the potential divider changes/AW	B1 M1 A1	<b>accept</b> so the current increases <b>accept</b> so IR of fixed resistor increases
	<b>(ii)</b>	voltages are equal so resistances are equal	B1	
<b>(c)</b>	<b>(i)</b>	straight line through origin labelled R passing through 0.06,12	B1 B1	<b>allow</b> correct lines with no labels
	<b>(ii)</b>	upward curve below straight line through origin labelled T passing through 0.06,12	B1 B1	
<b>Total question 3</b>		<b>15</b>		

3)

<b>a</b>		resistance decreases with increase in light intensity	B1	<b>ora</b>
<b>b</b>	<b>i</b>	3.0 (V)	B1	<b>accept</b> 3 V, no SF error
	<b>ii</b>	$3.0 = I.1.2 \times 10^3$ giving $I = 2.5 \times 10^{-3} \text{ A}$ $6.0/2.5 \times 10^{-3} = R = 2400 \Omega \quad 2.4 \text{ k}\Omega$	C1 C1 A1	<b>accept</b> $6 = (R/ R + 1.2 \text{ k}).9$ $2R + 2.4 \text{ k} = 3R$ or similar $R = 2.4 \text{ k}$ ; <b>give</b> 2 with POT error <b>accept</b> ratio of resistors $6/3 \times 1.2$ good candidates can do this by inspection with no working – full marks <b>allow</b> 2400 written on answer line rather than 2.4 if 2400 $\Omega$ within body of text
	<b>iii</b>	49 or 50 ( $\text{W m}^{-2}$ )	B1	<b>ecf</b> (b)(ii) if on R within graph range
<b>c</b>	<b>i</b>	2.2 (k $\Omega$ )	B1	<b>allow</b> any value from 2.1 to 2.2
	<b>ii</b>	large(r) <u>changes in</u> R at low light intensities  relating change in R to change in V	B1  B1	<b>allow</b> greater sensitivity of LDR at low light <b>or</b> steeper gradient/AW <b>e.g.</b> bigger change in I so in V <b>or</b> use of $V = R/(R + 1200) V_s$ <b>or</b> bigger change in V ratio across Rs
<b>d</b>		V across 1.2 k $\Omega$ falls so V across LDR rises because ratio of Rs changes in favour of LDR/ potential divider argument <b>or</b> total V is constant	B1 B1 B1	<b>alternative</b> I increases because <u>total</u> R is less so V across LDR rises do <b>not</b> award B marks where there is CON e.g. V across 1.2 k rises so V across LDR rises
<b>e</b>		continuous record for very long time scale of observation can record very short time scale signals (at intervals) automatic recording/remote sensing data can be fed directly to computer (for analysis)	B1 B1	<b>allow</b> any two sensible suggestions which fall within the 4 categories listed for 2 marks
<b>Total question 4</b>		<b>14</b>		

4)

(a)		R of <u>thermistor</u> decreases as temperature increases supply V is constant/ <u>total</u> R is smaller current increases <u>as</u> $V = IR/AW$	B1 B1 B1	<b>accept</b> more free e's as temperature rises using $I = nAev$ current increases as v decrease very small/AW
(b)		$R_{th} = 40 \Omega$ at $240^\circ C$ (stated or used in calculation) total R in circuit = $240 \Omega$ $I = 6/240 = 0.025 A$ $V = 200 \times 0.025 = 5.0 V$	B1 C1 C1 A1	<b>apply ecf</b> if wrong value of R read from graph <b>allow</b> $V = (200/240)6$ so $V = 5.0 V$ <b>accept</b> 5 V (no SF error)
(c)	(i)	correct symbol for LDR	B1	no circle required
	(ii)	R of <u>LDR</u> decreases/current in circuit increases so V increases <u>across fixed/200 <math>\Omega</math> resistor/AW</u>	M1 A1	<b>accept</b> simple potential divider argument <b>accept</b> voltmeter reading increases
<b>Total</b>			<b>10</b>	

5)

a	i	V is not proportional to I	B1	<b>accept</b> not a straight line; R is not constant
	ii	R (approximately) constant up to $V = 0.5 V$ and $I = 50 mA$ so $R = 0.5/0.05 = 10 (\Omega)$	B1 B1	<b>allow</b> graph is (almost) linear/straight (to $V = 0.5 V$ ) or constant gradient <b>allow</b> any correct calculation, e.g. $0.2/0.02$
	iii	the resistivity/resistance of the (metal) filament increases with temperature the larger the current in the filament the hotter it becomes/AW	B1 B1	<u>larger current</u> heats filament <u>so</u> resistance increases <b>or</b> electron-ion collisions increase/AW; <b>allow</b> atom for ion
b		Any potential divider argument or calculation <i>In the light</i> parallel combination less than or about $1 \Omega/AW$ so V across lamp less than $0.5 V$ (so lamp out)/ small compared to V across $25 \Omega$	B1 B1 B1	<b>QWC</b> the arguments must be clear for full marks <b>allow</b> $R_{lamp} = 10$ to $25 \Omega$ for any calculation <b>or</b> comparison of voltage across $25 \Omega$ to $1 \Omega$ <b>N.B.</b> answers given in terms of current are likely to score zero
		<i>In the dark</i> parallel combination about $25 \Omega/AW$ so V across lamp approximately $6.0 V$ so lamp on	B1 B1	
<b>Total</b>			<b>10</b>	