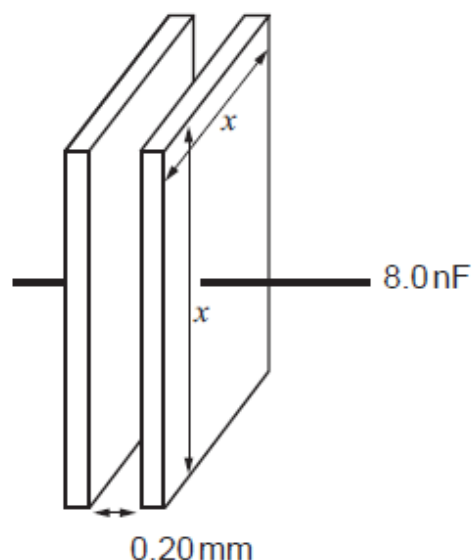


- (a) (i) An 8.0 nF capacitor has square plates separated by 0.20 mm of air. Calculate the length (x) of the sides of the plates. [3]



.....

.....

.....


.....

.....

.....

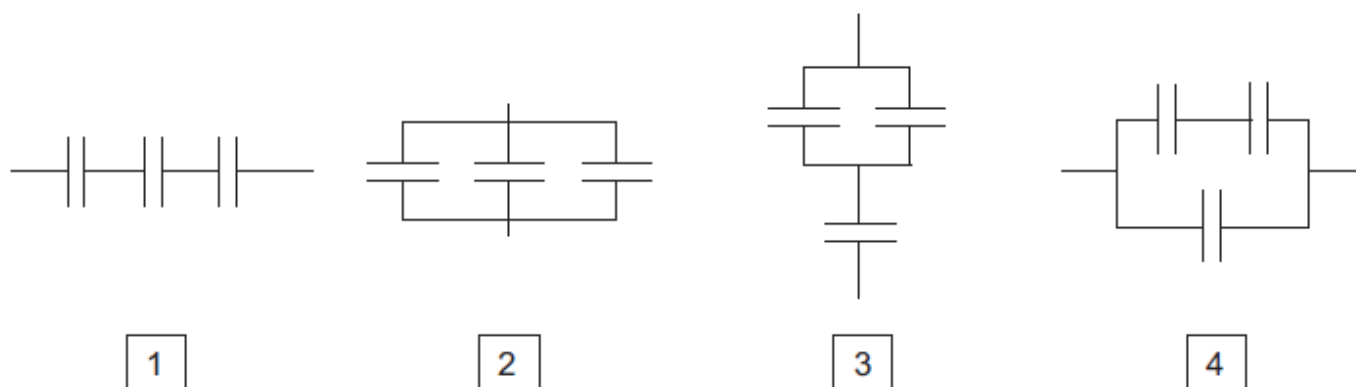- (ii) Which of the following combinations of 8.0 nF capacitors has a capacitance of 12.0 nF ? Justify your answer. [4]

All individual capacitors shown are 8.0 nF .



.....

.....

.....


.....

.....

- (iii) State how the capacitance of the capacitor can be increased without changing its dimensions. [1]


- (iv) Calculate the charge on the plates of the 8.0 nF capacitor when it stores an energy of $0.62\text{ }\mu\text{J}$. [3]

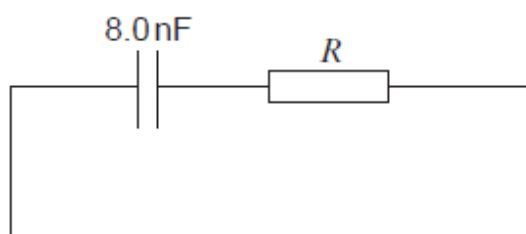- (b) (i) A charged 8.0 nF capacitor is discharged through a large resistor. Calculate the resistance of the resistor if the time constant is 15.5 ms . [2]



- (ii) Calculate the fraction of the initial charge remaining on the capacitor after 31.0 ms . [3]

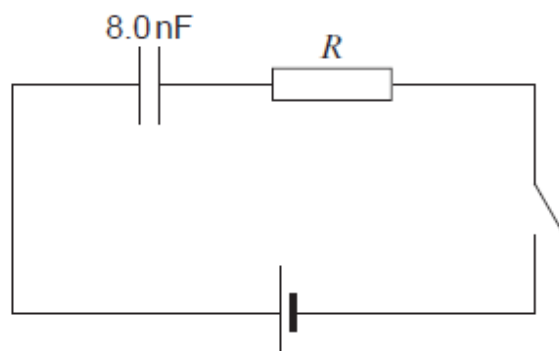
- (c) An identical, uncharged 8.0 nF capacitor is **charged** in the following circuit, **using the same large resistor, R** . The switch is closed and the capacitor is uncharged at time $t = 0$.



Without further calculations, sketch graphs of:


- (i) the charge on the plates of the capacitor against time;

[2]

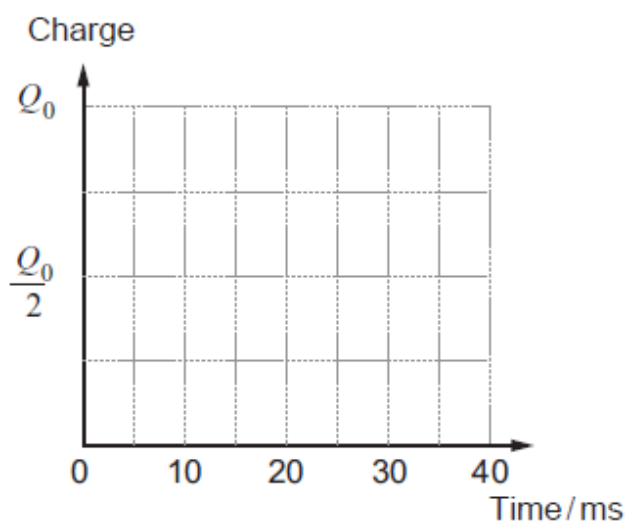


- (ii) the current in the circuit against time.

[2]

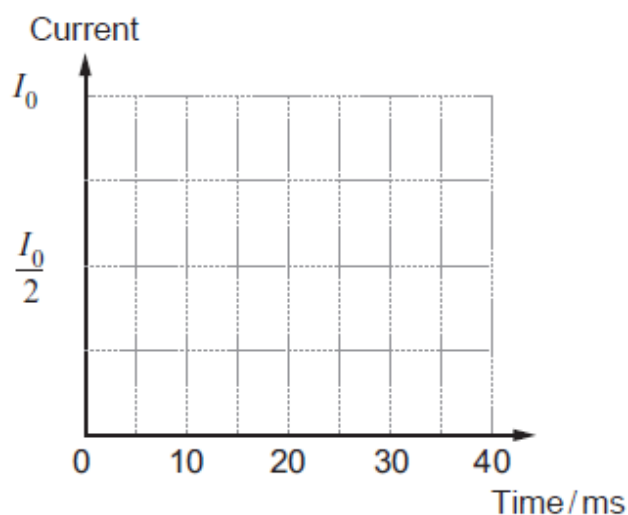

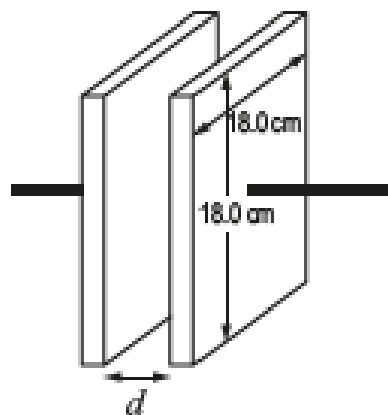1. (a) (i) A laboratory technician has two square aluminium plates with sides of length 18.0 cm. Calculate the separation, d , of the plates that produces a capacitance of 2.0 nF. [3]



.....


.....

.....

.....

.....

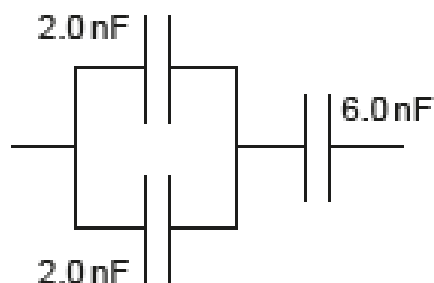- (ii) Calculate the capacitance of the capacitor combination shown. [3]



.....


.....

.....

.....

.....

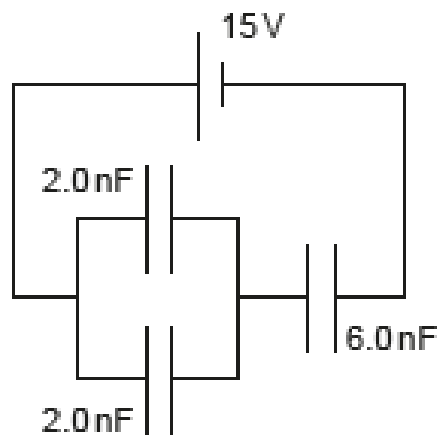- (iii) Show that the charge stored on a 2.0 nF capacitor in the following circuit is 18 nC . [3]



.....

.....

.....

.....

.....

.....

- (iv) Calculate the total energy stored by the capacitor combination. [2]

.....


.....

.....


.....

(b) A group of students investigated the charging of a capacitor through a resistor and obtained the following data.

pd across capacitor / V

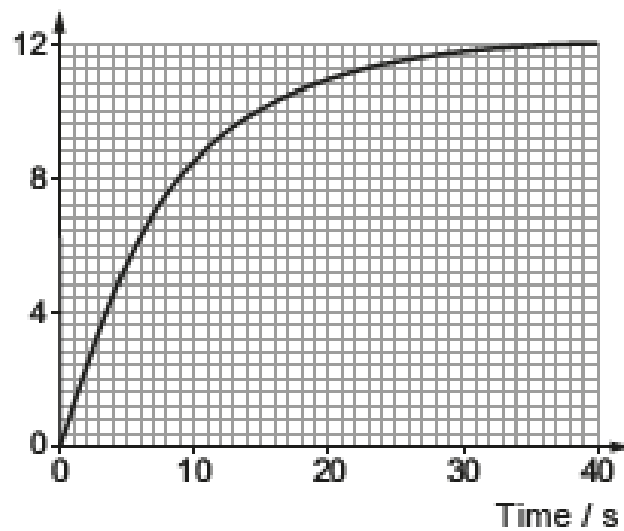

Current / mA

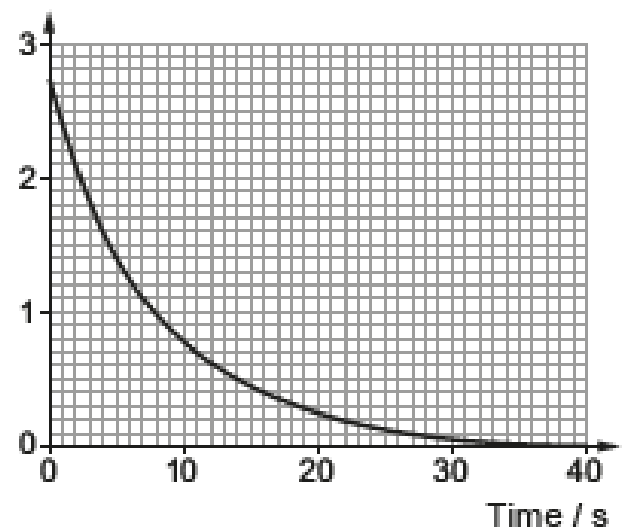

- (i) Draw a circuit diagram of the apparatus that might have been used to obtain the data. [2]

- (ii) Use the graphs to determine:
- the emf of the power supply;
 - the resistance of the resistor;
 - the capacitance of the capacitor.

[5]

.....

.....

.....

.....

.....


.....

.....

.....

.....

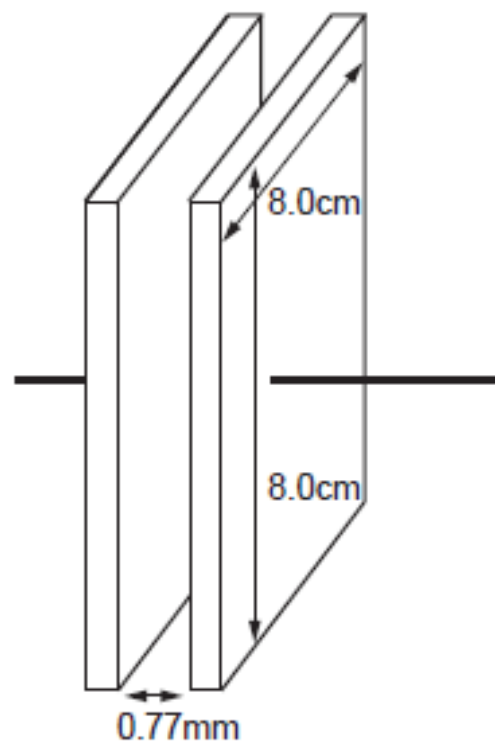1. (a) (i) For the air-spaced parallel plate capacitor shown, calculate the pd applied when it stores $25.5\mu\text{J}$ of energy. [4]



.....

.....

.....

.....

.....

.....

.....

.....

(ii) Explain why the capacitor stores energy when a pd is applied to the plates. [2]

.....

.....

.....

.....

(iii) A group of scientists claim that they have developed a new dielectric that enables the above capacitor to store a million times more charge and energy for a given pd. Explain what further steps must be taken by the scientific community and industry before this new dielectric can be used in devices and sold to the public. [3]

.....

.....


.....

.....

.....

.....

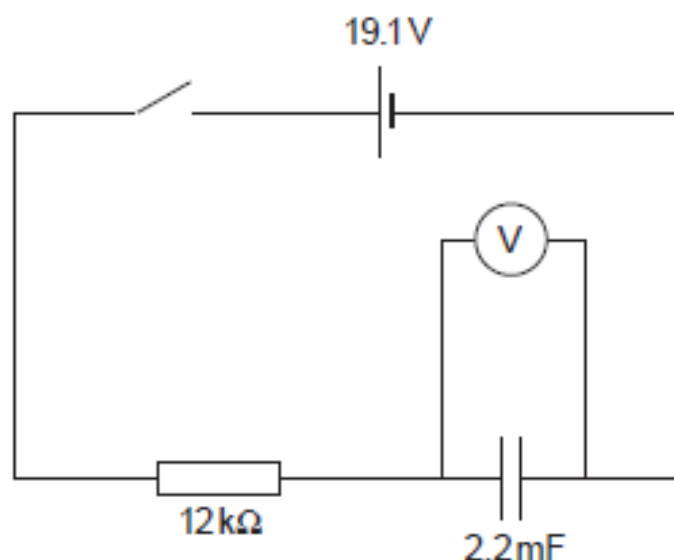(b) Bethan investigates the charging of a capacitor using the following circuit.



The results she obtains are then tabulated.

Time / s	pd across capacitor / V $\pm 0.5\text{ V}$	Charge on capacitor / mC $\pm 1.1\text{ mC}$
10.0	6.1	13.4
20.0	10.0	22.0
30.0	12.8	
40.0	15.1	33.2
50.0	16.2	35.6
60.0	17.1	
70.0	17.7	38.9
80.0	18.3	40.3

- (i) Confirm that the uncertainty in the charge is 1.1 mC (you may assume that the uncertainty in the 2.2 mF capacitor is negligible).

[1]

.....


.....

- (ii) Complete the table.

[2]

- (iii) Complete the graph by labelling the y -axis scale, plotting the remaining two points, adding error bars for charge and drawing a curve of best fit. [5]

Charge / mC

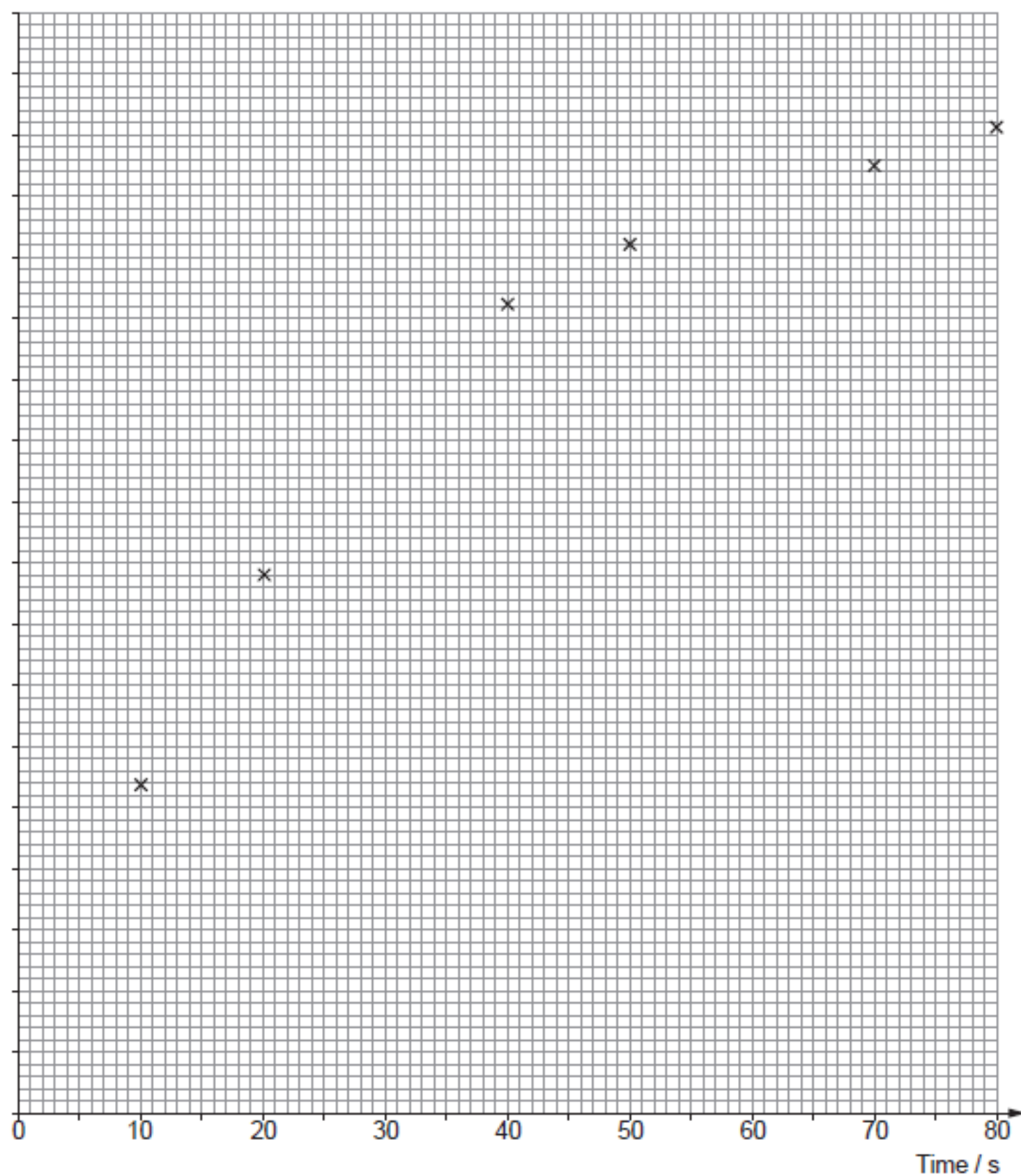

- (c) Use the graph on page 5 and your answers to (b)(iv) and (b)(v) to evaluate whether or not the data obtained in this experiment are in good agreement with the equations: [5]

$$Q = Q_0 \left(1 - e^{-\frac{t}{RC}} \right) \text{ and } I = I_0 e^{-\frac{t}{RC}}$$

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

