

Marking Scheme


1.	Question		Marking details	Marks available				Maths	Prac
				AO1	AO2	AO3	Total		
1	(a)	(i)	Resistance of LDR / circuit increases [as light intensity decreases] (1) [Hence] current decreases (1)	2			2		2
		(ii)	Either: $\text{Current in LDR} = \frac{4.0}{2.4 \times 10^3} = [1.67 \times 10^{-3} \text{ A}] \text{ (1)}$ $R = \frac{5.0(1)}{1.67 \times 10^{-3}}$ $R = 3.0 \text{ k}\Omega \text{ (1)}$ Alternative: $4.0 = \frac{2.4 \times 10^3 \times 9.0}{(2.4 \times 10^3 + R)} \text{ (1) [substitution into potential divider equation]}$ Correct algebra (1) $R = 3.0 \text{ k}\Omega \text{ (1)}$ Alternative: $\frac{4}{5} = \frac{2.4}{R} \text{ (1)}$ $R = 3.0 \text{ k}\Omega \text{ (1)}$	1	1 1		3	2	3
	(b)		Light from lamp will decrease [LDR resistance and hence] V across lamp low so lamp not activated (1) Hence reason for on/off, e.g. lamp off $\rightarrow$ LDR in dark $\rightarrow V_{\text{out}}$ high $\rightarrow$ lamp on		2		2		2
			Question 1 total	3	4	0	7	2	7

Question			Marking details	Marks available				Maths	Prac
				A01	A02	A03	Total		
2	(a)	(i)	Rate of charge flow Accept $I = \frac{\Delta Q}{\Delta t}$ only if ΔQ and Δt defined [accept Q and t]	1			1		
		(ii)	J C ⁻¹ and C s ⁻¹ as units of V and I respectively clearly shown (1) Correct division seen i.e. $\frac{JC^{-1}}{Cs^{-1}}$ seen (1) Or from alternative correct expression, e.g. $R = \frac{V^2}{P}$ or $R = \frac{V}{I}$ Or equivalent in terms of quantities.	1	1		2	1	
	(b)	(i)	I through $R_P = 1.2$ A and I through $R_T = 0.8$ A (1) $\frac{V_P}{V_T} = \frac{1.2R_P}{0.8R_T}$ (=1.5) seen (1) Or Parallel combination calculated as $\frac{2}{3}R$ (1) Potential divider: $\frac{R}{R + \frac{2}{3}R} \times 9 = 1.5$ (1)		2		2	1	
		(ii)	$2.5V_T = 9.0$ or $\frac{5V_P}{3} = 9.0$ (1) $V_T = 3.6$ V or $V_P = 5.4$ V (1) Award 2 marks for either V_P or V_T calculated correctly. $R_T = \frac{3.6}{0.8} = 4.5 \Omega$ or $R_P = \frac{5.4}{1.2} = 4.5 \Omega$ or $\frac{1.8}{0.4} = 4.5 \Omega$ (1) Alternative: Total circuit $R = \frac{9.0}{1.2} = 7.5 \Omega$ (1) Parallel and series combination shown to be $= \frac{5R}{3}$ (1) $\frac{5R}{3} = 7.5$ and $R = 4.5 \Omega$ (1) Alternative: Understanding that $V_P + V_T = 9$ (1) $1.2R_P + 0.8R_T = 9$ (1) (award 2 marks for this only) $R_P = R_T = R$ and $R = \frac{9}{2} = 4.5 \Omega$ clearly shown (1) Accept reverse argument.		3		3	3	
	(c)		P (circuit) = 10.8 W (1) (either $\frac{81}{7.5}$ or $(1.2)^2 \times 7.5$ or 1.2×9) P in $R_Q = (0.4)^2 \times 4.5 = 0.72$ W (1) $\frac{10.8}{0.72} = 15$ seen (1) Alternative: $P_s = P_Q$ since $I_s = I_Q$ $P_T = 4 \times P_Q$ since $I_T = 2 \times I_Q$ $P_P = 9 \times P_Q$ since $I_P = 3 \times I_Q$ Hence total circuit power = $P_Q + P_Q + 4P_Q + 9P_Q$ $= 15P_Q$ Award (1) for correct individual power analysis Award (1) for correct reason linked to currents Award (1) for showing correct total P		3		3	2	
	(d)		Circuit resistance increases, leading to total current decreasing. Power dissipated in circuit decreases (1) V across R_Q has increased (from 1.8 V to 3.0 V), so P_Q increases / I through R_Q has increased (from 0.4 A to 0.67 A) so P_Q increases (1) Hence ratio decreases (1) [only award from correct explanation] Accept numerical explanation: e.g. Circuit resistance is now 13.5 Ω and circuit current = 0.67 A (1) circuit power shown to be 6 W and P_Q shown to be 2 W (1) Hence ratio decreases or is now 3 (1) Alternative: With T removed, I through all remaining resistors is the same or V across each is the same (1) Use of VI or I^2R or V^2/R or power / energy dissipated in all three resistors equal (1) So total $P = 3 \times P_Q$ or which is less than $15P_Q$ (1)		3		3		
			Question 2 total	2	12	0	14	7	0

Question	Marking details		Marks available				Maths	Prac
			AO1	AO2	AO3	Total		
2	(a)	There are 6 J of energy/work done (converted from electrical to other forms) (1) Per coulomb of charge between X and Y (1)	2			2		
	(b)	(i) Attempt to use equation to determine resistors in parallel (1) Resistance of parallel combination = $3.7[2] \Omega$ (1) Total circuit resistance = 9.3Ω ecf on parallel (1) Current = $\frac{V}{R} = 0.64 \text{ A}$ [accept 0.65 A] answer to 2 d.p. (1)	1	1 1 1		4	3	
		(ii) Apply ecf from part (b) (i) PD across parallel = 0.65×3.7 ecf OR pd across $5.6 \Omega = 0.65 \times 5.6 = 3.6 \text{ V}$ (1) Answer = 2.4 V (1)		2		2	1	
		(iii) Substitute values into $P = I^2 R$ [$P = 0.65^2 \times 3.7$] (1) $P = 1.54 \text{ W}$ – ecf (1)	1	1		2	2	
		Question 2 total	4	6	0	10	6	0

4.	(a)	(i)	$R = \frac{1.6}{15 \times 10^{-3}(1)}$ (reading from graph, accept 14×10^{-3}) $R = 107 \Omega$ [answers in range 107 – 114 Ω]	2
		(ii)	[Very] high [accept infinite]	1
	(b)	(i)	V not proportion to I / not a straight line [through the origin] [“Not through origin” insufficient on its own]	1
		(ii)	Bulb / thermistor [Not wire or superconductor, but accept superconducting device, e.g. superconducting electromagnet coil]	1
	(c)		$R = \frac{V}{I} (1); R = \frac{10.4(1)}{15 \times 10^{-3}} = 693 \Omega (1)$ Alt 1: $10.4 = \frac{R}{R + 107} \times 12$ [or equiv.] (1) manipulation e.g. $10.4R + 112.8 = 12(1); R = 696 \Omega (1)$ Alt 2: $R_T = \frac{V}{I}$ or $\frac{12}{1.5 \times 10^{-3}} (1) = 800 \Omega (1); R = 800 - 107 = 693 \Omega (1)$	3
				[8]

Question				Marking details	Marks available					
					A01	A02	A03	Total	Maths	Prac
3.	(a)			In a <u>water</u> bath or in a beaker of <u>water</u> must imply heading (1) Using ice cubes / taking water from fridge / in an ice bath or equivalent (1)	1		1	2		2
	(b)	(i)		Straight line of best fit drawn (from 18 – 100 °C) with points either side or reference to very little scatter in the readings (1) Reference to or comparison with $y = mx + c$ (1) Positive intercept or positive gradient (1)		1	1 1	3		3
		(ii)	I	5.5 Ω , 5.6 Ω or 5.7 Ω unit mark [Accept attempts at 3 sf]		1		1	1	1
			II	Either Readings from graph line inserted in $\frac{\Delta R}{\Delta \theta}$. Tolerate slips (1) Gradient = 0.023 [± 0.002] [$\Omega ^\circ\text{C}^{-1}$] or by implication (1) $\alpha = 3.9 [\pm 0.4] \times 10^{-3} ^\circ\text{C}^{-1}$ unit mark ecf on R_0 and gradient (1) Or Value of R_0 and (R , θ) values from another point on graph line inserted in equation. Tolerate slips (1) Correct algebra (1) $\alpha = 3.9 [\pm 0.4] \times 10^{-3} ^\circ\text{C}^{-1}$ unit mark ecf on R_0			1 1 1	3	3	3
				Question 3 total	1	2	6	9	4	9

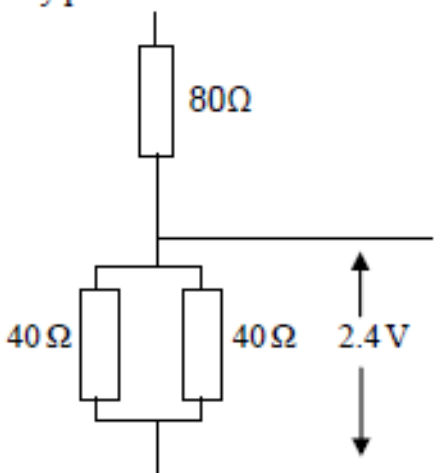
6.	(a)	(i)	$Resistance = \frac{pd}{current}$ (accept: voltage / if V and I written must be qualified)	[1]
		(ii)	$V = JC^{-1}$ (1); $I = C s^{-1}$ (1); Convincing working (1) Don't accept use of t -award ecf for 3 rd mark. Alternative route using power formulae is acceptable.	[3]
	(b)	(i)	$I = \frac{V_{in}}{R_1 + R_2}$	[1]
		(ii)	$V_{out} = IR_2$ (1); I (from (i)) used correctly (1)	[2]
	(c)	(i)	Any parallel combination shown (1); 40 [Ω] used correctly (1)	[2]
		(ii)	 Resistor combination shown (1) ecf from (c)(i) 2.4 [V] or V_{out} labelled correctly (1)	[2]

7. (a)	(i)	$I \propto V(1)$ Providing the temperature / physical conditions remain constant (1)	2																				
	(ii)	$V A^{-1}$ circled	1																				
(b)	(i)	<table border="1"> <thead> <tr> <th>Switch combination</th><th>P</th><th>Q</th><th>S</th></tr> </thead> <tbody> <tr> <td>X open, Y open</td><td>On</td><td>On</td><td>Off</td></tr> <tr> <td>X closed, Y open</td><td>Off</td><td>On</td><td>Off</td></tr> <tr> <td>X open, Y closed</td><td>On</td><td>On</td><td>On</td></tr> <tr> <td>X closed, Y closed</td><td>Off</td><td>On</td><td>On</td></tr> </tbody> </table> (1) (1) (1)	Switch combination	P	Q	S	X open, Y open	On	On	Off	X closed, Y open	Off	On	Off	X open, Y closed	On	On	On	X closed, Y closed	Off	On	On	3
Switch combination	P	Q	S																				
X open, Y open	On	On	Off																				
X closed, Y open	Off	On	Off																				
X open, Y closed	On	On	On																				
X closed, Y closed	Off	On	On																				
	(ii)	Either $R = \frac{9}{0.18} (1) (= 50 \Omega) \rightarrow R_P + R_Q = 50 (1)$ $R_{\text{each buzzer}} = 25[\Omega] (1)$ ecf between 2nd and 3rd marks Or $R = \frac{4.5 (1)}{0.18} (1) = 25[\Omega] (1)$	3																				
	(iii)	$R_{\text{Total}} = 16\frac{2}{3} [\Omega] (1) \quad I = \frac{9}{16\frac{2}{3}} = 0.54 [A] (1)$ ecf from (b)(ii) / no ecf for R_{Total}	2																				
	(iv)	<u>Either</u> ecf from (b)(ii) or (b)(iii) or both $P_S = \left(\frac{2}{3} \times 0.54\right)^2 \times 25 (1) \quad P_S = 3.24 [W]$ $P_Q = \left(\frac{1}{3} \times 0.54\right)^2 \times 25 (1) \quad P_Q = 0.81 [W]$ <u>Or</u> $P_S = \frac{9^2}{25} (1) = 3.24 [W] \quad P_Q = \frac{4.5^2}{25} (1) = 0.81 [W]$ <u>Or</u> $P_S = \frac{2}{3} \times 0.54 \times 9 (1) = 3.24 [W] \quad P_Q = \frac{1}{3} \times 0.54 \times 4.5 (1) = 0.81 [W]$ $\rightarrow \frac{3.24}{0.81} = 4 (1) \quad \text{or any correct algebraic solution} = 3 \text{ marks}$	3																				

8.

(a)

(i)

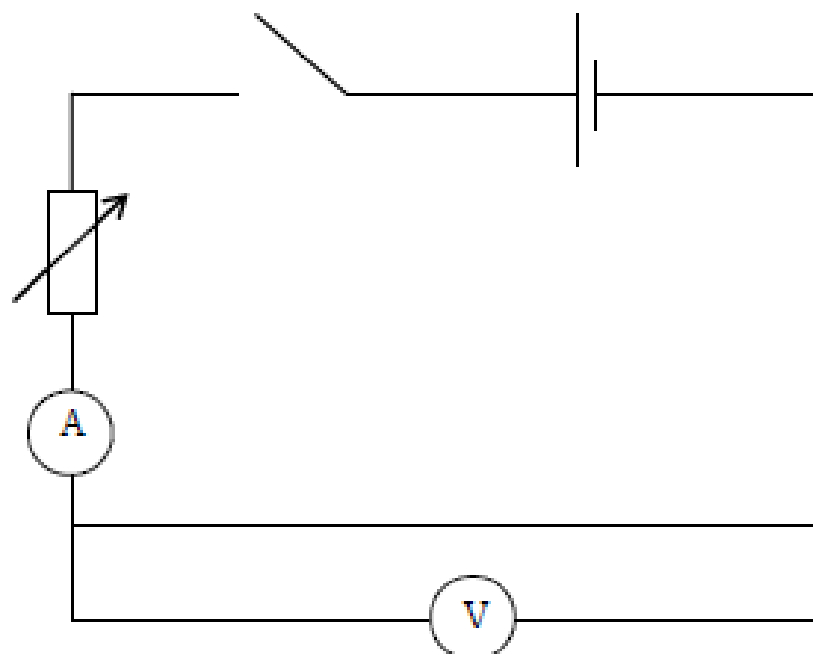

Circuit (without voltmeter and ammeter) (1)

Voltmeter and Ammeter correctly positioned (1)

2

$$(ii) \quad R = \frac{10}{0.9} = 11.11 \, [\Omega] \quad (1)$$

$$A = 3.14 \times 10^{-8} \, [\text{m}^2] \quad (1)$$

$$\rho = \frac{11.11 \times 3.14 \times 10^{-8}}{3.2} \quad (1) \text{ substitution} \quad \rho = 1.09 \times 10^{-7} \, [\Omega \text{ m}] \quad (1)$$

ecf for R and A

4

(iii) Platinum and Tin

1

(b)

$$\rho = \frac{0.74 \times 10^{-3}}{(3.14 \times 10^{-8} \times 3.2)(1)} = 7365 \, [\text{kg m}^{-3}] \quad (1) \text{ ecf for A}$$

Tin (1) ecf from density value

3

9.	(a)	(i)	[For a metallic conductor] the potential difference and current are [directly] proportional/ $I \propto V$ (1), provided the temperature remains constant / all physical factors remain constant (1) $V = IR$ only no marks	2
		(ii)	It is constant / stays the same / increases as the temperature increases	1
	(b)	(i)	$A = 1.5(3) \times 10^{-8} \text{ [m}^2\text{]}(1)$ $R = \frac{\rho l}{A} = \frac{95 \times 10^{-8} \times 3.2}{1.5(3) \times 10^{-8}} (1) = 199 \text{ } [\Omega] (1)$	3
		(ii)	$\frac{230^2}{200} = 265 \text{ [W]}$ allow e.c.f. from (b)(i)	1
		(iii)	$\frac{1}{66.7(1)} = \frac{1}{200} + \frac{1}{R_2} (1)$ $R_2 = 100 \text{ } [\Omega] (1)$	3
		(iv)	R_2 (1) either reference to $\frac{V^2}{R}$ so lower R / same V across lower R or reference to $I^2 R$ so greater I or reference to IV so I increased [for constant V] or correct calculation of R_2 (1)	2
		(v)	$\frac{230}{66.7} = 3.5 \text{ [A]}$ allow e.c.f. from (b)(iii)	1

(a)	(i)	[For a metallic conductor] the potential difference and current are [directly] proportional/ $I \propto V$ (1), provided the temperature remains constant / all physical factors remain constant (1) $V = IR$ only no marks	2
	(ii)	It is constant / stays the same / increases as the temperature increases	1
(b)	(i)	$A = 1.5(3) \times 10^{-8} \text{ [m}^2\text{]}(1)$ $R = \frac{\rho l}{A} = \frac{95 \times 10^{-8} \times 3.2}{1.5(3) \times 10^{-8}} (1) = 199 \text{ } [\Omega] (1)$	3
	(ii)	$\frac{230^2}{200} = 265 \text{ [W]}$ allow e.c.f. from (b)(i)	1
	(iii)	$\frac{1}{66.7(1)} = \frac{1}{200} + \frac{1}{R_2} (1)$ $R_2 = 100 \text{ } [\Omega] (1)$	3
	(iv)	R_2 (1) either reference to $\frac{V^2}{R}$ so lower R / same V across lower R or reference to $I^2 R$ so greater I or reference to IV so I increased [for constant V] or correct calculation of R_2 (1)	2
	(v)	$\frac{230}{66.7} = 3.5 \text{ [A]}$ allow e.c.f. from (b)(iii)	1

10.	Question		Marking details	Marks available				Maths	Prac
				AO1	AO2	AO3	Total		
2	(a)		$I = 0.0012 \text{ A}$ and $R_{\text{int}} = 5000 \Omega$ or $V_{\text{therm}} = 4.80 \text{ V}$ or $\frac{R_{\text{th}}}{1000 \Omega} = \frac{4.8 \text{ V}}{1.2 \text{ V}}$ or any other correct and relevant potential divider equation or by implication (1) $R_{\text{therm}} = 4000 \Omega$ (1) $\theta = 15^\circ$ ecf on R_{therm} (1)		3		3	3	
	(b)		Graph gradient changes [with θ] or graph not straight [or voltmeter reading doesn't vary linearly with R_{therm}] or ΔV not proportional to ΔR (1) n not constant [with varying θ] / he is wrong [only award if backed up by reasonable argument] (1)			2	2	1	
	(c)		So thermistor [accept: 'it'] doesn't heat up (1) Reference to electrical heating [even of circuit or resistor] or masking response to surroundings (or equiv) (1)		2		2		
			Question 2 total	0	5	2	7	4	0

11.	(a)	(i)	[Rate of] flow of charge / $I = \frac{Q}{t}$ or $\frac{dQ}{dt}$ <u>with Q defined</u>	1
		(ii)	C s^{-1}	1
	(b)	(i)	$x = y + z$	1
		(ii)	charge	1
	(c)	(i)	$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$ or $R = \frac{R_1 R_2}{R_1 + R_2}$ of by impl. (1) $R_{\parallel} = 30 \Omega$ (1); $R_{\text{Total}} = 40 \Omega$ (1) [no e.c.f.]	3
		(ii)	[Current $x =$] 0.15 A e.c.f. [Accept equiv., e.g. $\frac{6}{40}$, but not 0.2 A without working]	1
		(iii)	$V_1 = 0.15 \times 10 [= 1.5 \text{ V}]$ (1) [e.c.f.] $V_2 = 6 - 1.5 [= 4.5 \text{ V}]$ [or $30 \times 0.15 = 4.5 \text{ V}]$ (1) [e.c.f.]	2
		(iv)	$y = \frac{4.5}{120} [= 0.038 \text{ A}]$ (1) $z = 0.15 - 0.038 \text{ e.c.f.} [= 0.11 \text{ A}]$ $\left[\text{or } \frac{4.5}{40} [= 0.11 \text{ A}] \right]$ (1)	2
			[Accept solutions based upon ratios, e.g. $y = \frac{0.15}{4} \dots$]	[12]

13.

Question			Marking details	Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
1.	(a)	(i)	The current [through a metal conductor at constant temperature] is proportional to the pd [across it] Accept $I \propto V$ with well-defined symbols.	1			1		
		(ii)	Constant [or independent of current [or pd]] (1)	1			1		
	(b)	(i)	pd across X = 0.70 [V] (1) or by impl so $R_X = 58 \text{ } \Omega$ (1) or total resistance = 183 Ω (1) or by impl so $R_X = 58 \text{ } \Omega$ (1)		2		2	2	
		(ii)	$R_X = 16 \text{ } \Omega$ or equivalent (1) So Ohm's law not obeyed (1) [not freestanding] no ecf or If R_X stayed at 58 Ω (or 58.3 Ω), then $I = 27$ (or 26) mA (1) Not so, therefore Ohm's law not obeyed (1) no ecf			2	2	1	
		(iii)	No. Filament resistance increases with increasing pd [or current] or equivalent ecf on calculated value of R_X in (b)(ii)			1	1		
	(c)	(i)	Temperature at which a material [that is classed as a superconductor] loses all its resistivity [accept resistance] [when cooled]. Accept "... below which a material [...] has no resistivity [accept resistance]"	1			1		
		(ii)	Coil for MRI machine, power cables, magnets / electromagnets or anything reasonable (1) Can be kept below transition temp [cheaply] by liquid nitrogen [accept: superconducts in liquid nitrogen] (1)	2			2		
			Question 1 total	5	2	3	10	3	0

Question		Marking details	Marks available					
			A01	A02	A03	Total	Maths	Prac
4	(a)	Indicative content: Description: D1: At very low temperatures resistance of superconductor is zero ohms D2: Reference to transition temperature or critical temperature..... D3:where resistance suddenly drops to zero as temperature drops (or jumps up from zero as temperature rises) D4: Above transition temperature resistance increases with temperature D5: This increase in resistance with temperature is [approximately] linear [Sketch graph can show some of these points] Explanation: No explanation required for superconducting state. Above transition temperature: E1: As temperature increases, the ions in the metal lattice vibrate more quickly E2: Which makes it more likely that an electron will interact (accept collide) with the ion.... E3: So electrons lose kinetic energy and the drift velocity decreases E4:and collisions will cause ions to gain kinetic energy making further collisions more likely 5-6 marks Comprehensive description and explanation provided. <i>There is a sustained line of reasoning which is coherent, relevant, substantiated and logically structured.</i> 3-4 marks Comprehensive description or explanation provided or limited attempt at both description and explanation. <i>There is a line of reasoning which is partially coherent, largely relevant, supported by some evidence and with some structure.</i> 1-2 marks Limited attempt at description or explanation. <i>There is a basic line of reasoning which is not coherent, largely irrelevant, supported by limited evidence and with very little structure.</i> 0 marks No attempt made or no response worthy of credit.	6			6		
	(b)	One benefit to society given for each application: Particle accelerator 1 × (1) from: • Improve understanding of the nature of particles, • Skilled workforce opportunities • Have led to more powerful computing • Particle discoveries used in everyday applications e.g. TV sets • Well-reasoned economic benefits MRI scanner 1 × (1) from: • Improved diagnoses and treatment of many ailments • Skilled workforce opportunities • Benefits more people Reasoned choice of application [1]			3	3		
		Question 4 total	6	0	3	9	0	0

Question			Marking details	Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
1	(a)		I^2 - Energy (per coulomb or unit charge) used in external resistor/circuit [1] E - Energy (per coulomb/unit charge) transferred by source [or from chemical energy or from other forms] or used in whole circuit [1] Ir - energy (per coulomb/unit charge) wasted/lost in source or due to internal resistance [1] Use of 'per coulomb' or 'unit charge' at least once [1]	4			4		
	(b)	(i)	Circuit current = $\frac{1050 \times 10^{-3}}{2.5} = 0.42$ [A] [1] Total internal resistance = $\frac{0.5}{0.42} = 1.2$ [Ω] ecf on I [1] $r_{\text{cell}} = 0.6$ [Ω] [1]		3		3	2	
		(ii)	Substitution into $I^2 r t$ i.e. $(0.42)^2 \times 0.6 \times 60$ (ecf on I, r) [1] Alternative: Substitution into $\frac{I^2 t}{r}$ i.e. $\frac{(0.25)^2 \times 60}{0.6}$ (ecf on I, r) Alternative: Substitution into It^2 i.e. $0.42 \times 0.25 \times 60$ (ecf on I, I) Energy dissipated = 6.3 [J] [N.B. Alternative $\rightarrow$ 6.4 J] [1]	1			2	1	
	(c)		Either: Total resistance of coils in parallel = 2.975 [Ω] [1] and total circuit resistance = 4.175 [Ω] ecf [1] New current in circuit = $\frac{3}{4.175} = 0.72$ [A] [1] For the 4th mark: Rate of energy dissipation in each cell = $(0.72)^2 \times 0.6 = 0.31$ [W] so Kiera correct (or ratio calculated to be approx. 3) Or Energy dissipated in each cell in one minute = $(0.72)^2 \times 0.6 \times 60 = 18.6$ [J] so Kiera correct (or ratio calculated to be approx. 3) [1] Alternative: Total resistance of coils in parallel = 2.975 [Ω] [1] and total circuit resistance = 4.175 [Ω] ecf [1] New current = 0.72 [A] and pd drop across internal resistance = $0.72 \times 1.2 = 0.86$ [V] [1] Rate of energy dissipation in each cell For the 4th mark: = $\frac{(0.43)^2}{0.6} = 0.31$ [W] so Kiera correct (or ratio calculated to be approx. 3) Or Energy dissipated in each cell in one minute = $\frac{(0.43)^2 \times 60}{0.6} = 18.6$ [J] so Kiera correct (or ratio calculated to be approx. 3) [1]			4	4		
			Question 1 total	5	4	4	13	3	0

Question				Marking details	Marks available				Maths	Prac
					AO1	AO2	AO3	Total		
1	(a)	(i)		Energy (or work) /charge or energy (or work) per coulomb [accept joules per coulomb] (1) The above put correctly into context, e.g. Energy given by battery / energy transfer from chemical [or to electrical]. [Free standing mark] (1)	1 1			2		
		(ii)		Method 1 $I = \frac{4.33 \text{ V}}{6.60 \Omega} [= 0.656 \text{ A}]$ or by implication (1) $r = \frac{4.80 \text{ V} - 4.33 \text{ V}}{0.656 \text{ A}} = 0.71 / 0.72 / 0.7 \Omega$ (1) Method 2 Any correct and relevant pot div equation e.g. $\frac{r}{6.6 \Omega} = \frac{4.80 \text{ V} - 4.33 \text{ V}}{4.33 \text{ V}}$ or $4.33 = \frac{4.80 \times 6.60}{r + 6.60}$ (1) $r = 0.71 / 0.72 / 0.7 \Omega$ (1) See additional guidance for methods assuming 0.7 Ω	1	1		2	2	
		(iii)	i	More current (1) Therefore greater Ir [accept: greater lost volts] (1) NB $V = E - Ir$ on its own doesn't score. or Ratio (ext res)/ r lower (1) So ratio (ext pd)/(pd across r) less (1) or equivalents	1	1		2		
			ii	Current in either resistor = $\frac{3.35}{3.30} [= 1.02 / 1.015 \text{ A}]$ (1) Division by e at any stage (1) [e.g. $\rightarrow 61 \text{ C}$] Electrons in 1 minute = $3.8 \times 10^{20} \text{ C}$, ecf on I [NB electrons through parallel combination = $7.6 \times 10^{20} \rightarrow (2)$]		3		3	2	
	(b)	(i)		$R = \frac{V^2}{P}$ or $\left[I = \frac{1000 \text{ W}}{230 \text{ V}} \text{ and } R = \frac{V}{I} \right]$ (1) $R = 53 \Omega$ [accept early rounding] (1)	1	1		2	2	
		(ii)		3.6 [MJ]		1		1	1	
	(c)			If electric heating is used rather than gas, for a given heating effect more CO_2 produced [or more gas, a non-renewable resource [accept: fossil fuel] is used]. (1) Greater contribution to climate change/global warming [so use of electric heaters <i>should</i> be discouraged] (1) Any one of... • [But] higher cost of electricity [per kW] is discouragement enough • [But] not all power stations are gas-fired. [Some eg nuclear, wind, don't produce CO_2] • [But] not all homes have gas available • CO_2 absorbs long-wavelength infrared (or infrared emitted from Earth's surface) in context of climate change • Any other relevant and non-trivial point e.g. safety issue with naked flames / CO emission / gas leaks Example of point not worth credit: "it's none of anyone else's business how I heat my home" – the word in the question was "discouraged" / electric heaters more expensive to run			3	3		
				Question 1 total	5	7	3	15	7	0

Additional guidance for 1(a)(ii)

Method 3

[Assuming that] $r = 0.7 \Omega$:Total resistance = 7.30Ω

$$\therefore \text{Current} = \frac{4.80 \text{ V}}{7.30 \Omega} = 0.658 \text{ A} \quad (1)$$

$$\text{Terminal pd, } V = E - Ir = 4.80 - 0.685 \times 0.7 = 4.34 \text{ V, which is approximately as expected} \quad (1)$$

So the initial assumption is correct

Method 4

[Assuming that] $r = 0.7 \Omega$:[Total resistance = 7.30Ω]

Using the potential divider equation:

$$V = E \times \frac{R}{R+r} = 4.80 \text{ V} \times \frac{6.60 \Omega}{7.30 \Omega} \text{ equation used correctly} \quad (1)$$

$$= 4.34 \text{ V, which is approximately as expected} \quad (1)$$


17.

Question			Marking details	Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
4	(a)	(i)	Using $R = \frac{\rho l}{A}$ (1) Area = $\frac{\pi d^2}{4} = 6.16 \times 10^{-8} \text{ m}^2$ (1) Resistivity = $1.62 \times 10^{-8} \Omega \text{ m}$ unit mark (1)	1	1 1		3	2	
		(ii)	$p_i = \frac{0.1}{32.4} \times 100\% = 0.3\%$ or statement – negligible (1) $p_A = 2 \times p_d = 7.1\%$ (1) Total percentage uncertainty = 12% (ecf) (1) Abs unc (resistivity) = $\pm 0.2 \times 10^{-8} [\Omega \text{ m}]$ to 1 sf maximum (ecf) (1)		4		4	4	4
		(iii)	Silver and copper lie within range of values (ecf) (1) Material cannot be determined exactly from table (1)			2	2		
	(b)	(i)	Current is flow of (free) electrons (1) Flow is obstructed by collisions with ions (1) Collisions increase as temperature increases (1) Because of increased vibrations of ions/lattice or random speed of electrons increases (1)	4			4		
		(ii)	Using $R = \frac{V}{I}$ or proportional to $\frac{1}{I}$ OR temperature is inversely proportional to current (V constant) (1) Determining constant for at least 3 values dependent on method $k = \frac{R}{\text{Temperature}}$ or Temperature $\propto I$ (1) Conclusion – not constant (accept directly proportional if temperature in kelvin) (1)			3	3	2	3
			Question 4 total	5	6	5	16	8	7

18.

Question			Marking details	Marks available					
				AO1	AO2	AO3	Total	Maths	Prac
5	(a)	(i)	All resistors connected in parallel (1) Using $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ [or equiv] (1) $R_{\text{total}} = 1.44 [\Omega]$ (1)	1	1 1		3	2	3
	(b)	(i)	(A4/emf) is the energy generated in the cell (1) per coulomb (1) Loss of energy in circuit in the load resistor (E4) (1) $E - V$ is the energy is lost in internal resistance (1) Energy is conserved (1) Re-arrange gives $r = \frac{E - V}{I}$ (1)	1 1	1 1 1		6	1	
		(ii)	Substituting values in $\frac{A7 - E7}{D7}$ (1) $r = 0.15 [\Omega]$ (1)	1	1		2	2	
		(iii)	Using $P = I^2 R$ (1) $P = 0.45 [\text{W}]$ (1) 0.50 W – has to be greater than the power dissipated (need reason) (1)	1	1 1		3	1	
			Question 5 total	5	9	0	14	6	3

19.

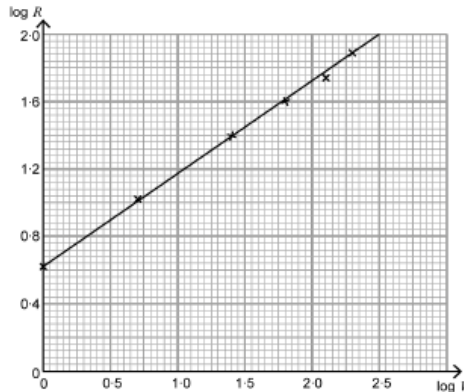
Question		Marking details	Marks available																																																						
			A01	A02	A03	Total	Maths	Prac																																																	
2	(a)	Varies value of variable resistor			1	1		1																																																	
	(b)	Correct attempt e.g. $\ln R = \ln(kV^n)$ or $\ln R = \ln k + \ln V^n$ [or using $\log_e$ or using $\log_{10}$] [1] Correct expression $\ln R = n \ln V + \ln k$ [or using $\log_e$ or using $\log_{10}$] [1]		2		2	2	2																																																	
	(c)	<table border="1"><thead><tr><th>V/V</th><th>I/A</th><th>R/Ω</th><th>$\ln(I/V)$</th><th>$\ln(R/\Omega)$</th></tr></thead><tbody><tr><td>1.00</td><td>0.52</td><td>1.9(2)</td><td>0.00</td><td>0.65</td></tr><tr><td>2.00</td><td>0.72</td><td>2.78 or 2.8</td><td>0.69</td><td>1.02</td></tr><tr><td>4.00</td><td>0.98</td><td>4.08 or 4.1</td><td>1.39</td><td>1.41</td></tr><tr><td>6.00</td><td>1.20</td><td>5.00</td><td>1.79</td><td>1.61</td></tr><tr><td>8.00</td><td>1.40</td><td>5.7(1)</td><td>2.08</td><td>1.74</td></tr><tr><td>10.00</td><td>1.54</td><td>6.49 or 6.5</td><td>2.30</td><td>1.87</td></tr></tbody></table> $\ln V$ values correct or accept $\log_{10} V$ values [1] Use of $R = \frac{V}{I}$ and all R and $\ln R$ values correct or accept $\log_{10} R$ values [1] <table border="1"><thead><tr><th>$\log_{10}(I/V)$</th><th>$\log_{10}(R/\Omega)$</th></tr></thead><tbody><tr><td>0.00</td><td>0.28</td></tr><tr><td>0.30</td><td>0.45</td></tr><tr><td>0.60</td><td>0.61</td></tr><tr><td>0.78</td><td>0.70</td></tr><tr><td>0.90</td><td>0.76</td></tr><tr><td>1.00</td><td>0.81</td></tr></tbody></table> Accept 2 or 3 sig figs in all cases. Accept 4 sig. Figs for $\ln V$ at 10.00 V (= 2.302) [1]	V/V	I/A	R/Ω	$\ln(I/V)$	$\ln(R/\Omega)$	1.00	0.52	1.9(2)	0.00	0.65	2.00	0.72	2.78 or 2.8	0.69	1.02	4.00	0.98	4.08 or 4.1	1.39	1.41	6.00	1.20	5.00	1.79	1.61	8.00	1.40	5.7(1)	2.08	1.74	10.00	1.54	6.49 or 6.5	2.30	1.87	$\log_{10}(I/V)$	$\log_{10}(R/\Omega)$	0.00	0.28	0.30	0.45	0.60	0.61	0.78	0.70	0.90	0.76	1.00	0.81		3		3	3	3
V/V	I/A	R/Ω	$\ln(I/V)$	$\ln(R/\Omega)$																																																					
1.00	0.52	1.9(2)	0.00	0.65																																																					
2.00	0.72	2.78 or 2.8	0.69	1.02																																																					
4.00	0.98	4.08 or 4.1	1.39	1.41																																																					
6.00	1.20	5.00	1.79	1.61																																																					
8.00	1.40	5.7(1)	2.08	1.74																																																					
10.00	1.54	6.49 or 6.5	2.30	1.87																																																					
$\log_{10}(I/V)$	$\log_{10}(R/\Omega)$																																																								
0.00	0.28																																																								
0.30	0.45																																																								
0.60	0.61																																																								
0.78	0.70																																																								
0.90	0.76																																																								
1.00	0.81																																																								
	(d)	Axes labelled either with no units i.e. $\ln R$ (or $\log_{10} R$) on y-axis and $\ln V$ (or $\log_{10} V$) on x-axis, or with $\ln(R/\Omega)$ and $\ln(V/V)$ respectively (or equivalent using) [1] Suitable scale e.g. large block – 0.2 on y-axis and 0.4 on x-axis for $\ln$ values and 0.2 on x-axis and 0.1 on y-axis on both axes for $\log_{10}$ values. [Linear, scales, with points occupying $\geq$ half available space] [1] All points plotted correctly within $\pm$ small square division [2] 5 points plotted correctly within $\pm$ small square division [1] 4 or less points plotted correctly within $\pm$ small square division [0] Straight line of best fit drawn [1] e.g. for $\ln$ graph: 		5		5	4	5																																																	
	(e)	(i) Attempt at taking gradient [1] $n = \frac{(2.0 - 0.65)}{2.5} = 0.5(4)$ [1] [answer gains both marks] $\ln k = 0.65$ or $k = e^{0.65}$ [1] $k = 1.9(2)$ [1] [answer gains both marks] N.B. ecf from graph for both values. Mark scheme to be applied as above for candidates using $\log_{10}$ values.	1	1																																																					
		(ii) $R = 1.9 V^{0.5}$ (ecf on n and k)	1			1	1	1																																																	
	(f)	Required statement: Results lie close to line of best fit suggests good quality Accept: results fit with the expected theory Don't accept it's a straight line or reference to measuring instruments			1	1		1																																																	
		Question 2 total	3	12	2	17	13	17																																																	

20.	Question			Marking details	Marks available					
					AO1	AO2	AO3	Total	Maths	Prac
2.	(a)			Gives charge [electrical potential] energy Accept pumps charge around circuit / does work on charge. Accept electrons instead of charge	1			1		
	(b)	(i)		Total emf = 3×1.60 or 4.80 [V] (1) Total resistance = $(1.20 + (3 \times 0.10))$ or 1.50 [Ω] (1) Current $[= \frac{V}{R}] = 3.2$ [A] (1) N.B. If workings in reverse award a maximum of 2 marks		3		3	1	
		(ii)	I	12.3 [W] ecf (10.8 W if 3 A used) e.g. using $P = I^2 R = 3.2^2 \times 1.2 = 12.3$ [W]		1		1	1	
			II	15.4 [W] ecf (14.4 W if 3 A used) e.g. using $P = IE = 3.2 \times 4.8 = 15.4$ [W]		1		1	1	
		(iii)		Thermal or internal. Accept 'heat', 'dissipated' (1) in internal resistance (1)	2			2		
	(c)			3.15 A or 3.2 A [Accept: even on short-circuit, extra cell gives only 3.0 A] (1) No. Current less than [accept same as] before ecf on (b)(i) (1)			2	2	1	
				Question 2 total	3	5	2	10	4	0

21.	(a)		V - energy (per coulomb) used in [external] resistor / circuit. (1) E - energy (per coulomb) transferred / supplied by source / in the whole circuit (1) Ir - energy (per coulomb) wasted / lost in source / cell / internal resistance (1) Use of 'per coulomb / unit charge' once. (1)	[4]
	(b)	(i)	4 [Ω]	[1]
		(ii)	Gradient attempted e.g. 60/10 (1) (or use of equation ecf from (b) (i)) emf = 6 [V] (1)	[2]
		(iii)	$1/I = 4$ [A^{-1}] or by implication (1) $R = 20$ [Ω] (1) Use of $I^2 R$ i.e. $(0.25)^2 \times 20$ (ecf) (1) or correct substitution into both $V = IR$ and $P = IV$ or V^2/R $P = 1.25$ [W] (1)	[4]
	(c)	(i)	emf = 12.0 [V] (ecf) <u>and</u> $r = 8.0$ [Ω] (ecf)	[1]
		(ii)	$R = 52.0$ [Ω] (ecf)	[1]
		(iii)	y intercept ($r \rightarrow 8.0 \Omega$ (ecf)) (1) Precise gradient e.g. through (5,52) (ecf) (1)	[2]

22.	(a)	<u>Electrical energy (or work done) transferred [to other forms passing] between two points (1) per coulomb of charge (1)</u> Definition of 1 V award 1 mark only	[2]
(b)	(i)	$V_{\text{supply}} = V_1 + V_2 + V_3$	[1]
	(ii)	Energy	[1]
(c)	(i)	$R_1 + 12 = \frac{9}{0.5} \quad (1)$ Clear manipulation seen to show $R_1 = 6 \, [\Omega] \quad (1)$	[2]
	(ii) (I)	$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$ to show effective parallel combination = $6 \, \Omega \quad (1)$ this can be implied V across upper $6 \, \Omega$ resistor shown = $4.5 \, [\text{V}]$ (ecf on parallel combination) (1)	[2]
	(II)	Total resistance = $12 \, \Omega \quad (1)$ $I = \frac{9.0}{12} = 0.75 \, [\text{A}] \quad (1)$ (accept $\frac{4.5}{6} = 0.75 \, [\text{A}]$)	[2]
	(III)	$1.2 = \frac{9}{(6 + R_{\text{parallel}})} \quad (1)$ $R_{\text{parallel}} = 1.5 \, [\Omega] \quad (1)$ $n \times \left(\frac{1}{12}\right) = \frac{1}{1.5} \quad (1)$ ecf on $1.5 \, [\Omega]$ $n = 8 \quad (1)$ Full marks for correct answer based on trial and error Alternative solution: $\frac{9}{1.2} = 7.5 \, [\Omega] \quad (1)$ $7.5 - 6 = 1.5 \, [\Omega] \quad (1)$ $\frac{12}{n} = 1.5 \, [\Omega] \quad (1)$ $n = 8 \quad (1)$	[4]

(a)	(i) Correct and convincing use of $\rho = \frac{RA}{l}$ (including unit conversion)	[1]
	(ii) $\left(\frac{2000}{11.2}\right) = 179 \text{ A unit mark}$	[1]
	(iii) $v = \frac{I}{nAe}$ rearranged (or shown numerically) (1) $n = 6.0 \times 10^{28} \times 3$ (1) $v = 1.55 \times 10^{-5} [\text{m s}^{-1}]$ (ecf on I and n) (1)	[3]
(b)	(i) Same (or equivalent)	[1]
	(ii) v increased (1) because...; A decreased, I, n, e unchanged by implication (1)	[2]
	(iii) Increased frequency / more collisions <u>between electrons and lattice / atoms / ions</u> or electrons carry greater kinetic energy (1) leading to <u>increased vibrational / kinetic energy of lattice atoms</u> (1)	[2]

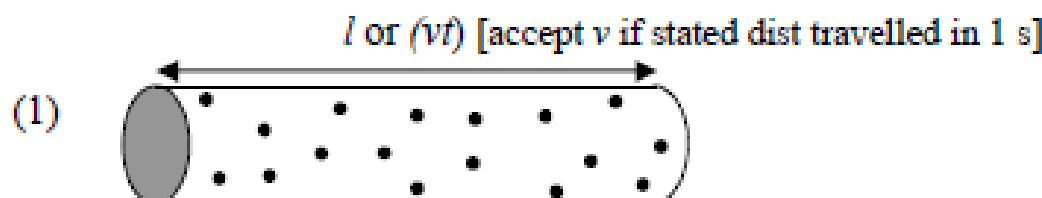

[NB free electrons not required to be labelled]

Number of free electrons = $nAvt$ [or nAl] (1)

Total charge = $nAvte$ [or $nAle$] (1)

$$I = \frac{nAvte}{t} \text{ with cancelling shown [or } \frac{nAle}{t}, \text{ where } \frac{l}{t} = v \text{ shown]} (1)$$

4

$$2.0 = 1.0 \times 10^{29} \times 1.7 \times 10^{-6} v \times 1.6 \times 10^{-19} (1) \text{ [substitution]}$$

$$v = 7.4 \times 10^{-5} \text{ m s}^{-1} ((\text{unit}))(1)$$

2

collisions [accept obstructions](1)

between free electrons and copper atoms / ions / lattice (1) [accept: delocalised / moving / conducting electrons]

2

$$R = \frac{P}{I^2} \text{ [or } P = I^2 R] (1); R = \frac{0.1}{4} [=0.025 \Omega] (1)$$

$$\rho = \frac{0.025[\text{e.c.f.}] \times 1.7 \times 10^{-6}}{2.5} (1) \text{ [manipulation i.e. } \rho = \frac{RA}{l} \text{ or with}$$

figures]

$$\rho = 1.7 \times 10^{-8} \Omega \text{ m. (1)}$$

4

cross-sectional area

smaller (1)

n

the same (1)

resistivity

the same (1)


3

[15]

25.	2	(a)		Ammeter shown in series with bulb [or in series with bulb/voltmeter parallel combination] (1) Voltmeter shown in parallel with bulb [or across bulb/ammeter series combination] (1)	2
		(b)	(i)	2.0 A	1
			(ii)	6.0 Ω	1
		(c)		Either: $\frac{1}{18} + \frac{1}{6(\text{ecf})} = \frac{1}{R_{\text{p}}}$ (1); $R_{\text{p}} = 4.5 \Omega$ (1) Subst into pot div equations: $12 = \frac{4.5}{4.5 + R} \times 16$ (1) $R = 1.5 \Omega$ (1) Or: $I_{18\Omega} = \frac{12}{18}$ [=0.67 A] (1); So $I_{\text{total}} = 2.67 \text{ A}$ [ecf from (a)](1) $R = \frac{4(1)}{2.67(\text{ecf})} = 1.5 \Omega$ (1)	4
		(d)		Graph shown with positive gradient and linear through the origin for low values (1) and smoothly reducing gradient for higher values [NB – not negative gradients at end](1)	2
					[10]

26.	(a)	(i)		Metal wire at constant temperature - straight diagonal line. Filament of lamp - curved line.	[1]
		(ii)		Straight line: R constant throughout [or V/I constant] as... (1) T constant throughout (1) Curve: Initially R constant [or V/I constant] as....(1) Then T increases (1) so R increases - accept explanation in terms of particles (1)	[5]
	(b)	(i)		$I = 2 \text{ [A]}$	[1]
		(ii)	(I)	Voltage across X = 12 [V]	[1]
			(II)	12 V - 6 V = 6 [V] ecf from (I)	[1]
			(III)	$R_2 = \frac{6}{4} = 1.5 [\Omega]$ ecf from (II)	[1]
			(IV)	V across $R_1 = 3 \text{ [V]}$ (1) I through $R_1 = 6 \text{ [A]}$ (1) $R_1 = \frac{3}{6}$ (ecf on I and/or V) = 0.5 [Ω] (1)	[3]

(a)	(i) Diagram to include • Correct electric circuit with ohmmeter or power supply with ammeter + voltmeter with correct symbols and positioning (1) • Method of heating shown (1) • Method of recording temperature shown (1) (ii) Linear [or approximately linear] graph with positive gradient (1) and positive intercept on R axis (1).	3 2
(b)	(i) Conducting / delocalised / free electrons (1) collide (1) with metal lattice / atoms / ions (1) [not with other free electrons] (ii) The greater the temperature the greater the vibrational energy of the lattice / metal ions (1) producing a greater chance [or rate] of collisions/ collisions more often / greater frequency of collisions (1) [not harder] .	3 2

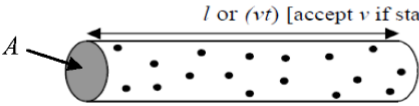Question			Marking details	Marks Available
3	(a)	(i)	[Free] electrons forced to move by applied pd (Need a reference to drift velocity or electron flow but does not need to be explicitly stated) (1) They collide with atoms/nuclei/ions/lattice of the wire (1) don't accept particles or molecules	2
		(ii)	$\text{Power} = \frac{1.8}{60} = 0.03 \text{ [W]} (1)$ $R = \frac{0.03(\text{ecf})}{1.6^2} = 0.0117 \text{ [\Omega]} (1)$ Alternative solution possible for the first 2 marks using $V = \frac{W}{Q}$ and $R = \frac{V}{I}$ $\rho = \frac{0.0117 \times 2 \times 10^{-6}}{0.4} (1) \text{ [ecf on } R]$ $= 5.9 \times 10^{-8} \text{ [\Omega m]} (1)$	4
	(b)	(i)	 [NB free electrons not required to be labelled] Number of free electrons = $nAvt$ [or nAl] (1) Total charge = $nAvte$ [or $nAle$] (1) $I = \frac{nAvte}{t}$ with cancelling shown [or $\frac{nAle}{t}$, where $\frac{l}{t} = v$ shown] (1) Volume defined either from diagram [e.g. A and l labelled as shown] or in body of derivation [e.g. $\text{vol} = Al$] and n identified correctly– for the first mark	4
		(ii)	$1.6 = 6.4 \times 10^{28} \times 2 \times 10^{-6} \times v \times 1.6 \times 10^{-19} (1: \text{substitution})$ $v = 7.8 \times 10^{-5} \text{ [m s}^{-1}] (1)$	2
		(iii)	(I) less than 1.6 A identified/circled (1) (II) the same as identified/circled (1) (III) half identified/circled (1)	3
			Question 3 Total	[15]

29.

(a)		n - number of free/conducting electrons (charge carriers) per unit volume (1) accept free electron density v - drift velocity (1)	[2]
(b)		LHS: $C s^{-1}$ (1) RHS: $m^3 \times m^2 \times m s^{-1} \times C$ (1) Clear manipulation to show/state LHS = RHS (1)	[3]
(c)	(i)	$v = \frac{I}{nAe}$ (1) (or correct substitution) $v = 1.30 \times 10^{-4} m s^{-1}$ (1) (-1 for slips in powers of 10) $t = \frac{5.0}{1.30 \times 10^{-4}} = 3.85 \times 10^4 [s]$ (1) ecf for incorrect value of v	[3]
(ii)		Reduced CSA (or diameter) <u>and</u> n, e constant..... (1)Increased v (1)Hence reduced t (1)	[3]

30.

(a)	(i)	Ruler and wire shown and labelled (1) Moving pointer or jockey or crocodile clip indicated (1) Either: Correctly positioned ohmmeter with no power supply; or correctly positioned voltmeter and ammeter with power supply (1) [No labelling required for either method].	[3]
(ii)		Diagonal line through origin	[1]
(iii)		CSA from <u>diameter of wire</u> (1) Gradient from graph = (R/l) or (ρ/A) Or stated take a pair of R and l values from the graph (1) $\rho = \text{gradient} \times \text{CSA}$ or use of $\rho = RA/l$ (1)	[3]
(b)	(i)	$R = \frac{144}{32} = 4.5 [\Omega]$ (1) Correct substitution into $R = \rho l/A$ (1) $l = 0.375 [m]$ (1) (ecf on R)	[3]
(ii)		$I = 2.7 [A]$ (from V/R or P/V etc) (1) (ecf on l) Correct substitution into $I = nAve$ (1) $v = 1.24 \times 10^{-2} [m s^{-1}]$ (1) accept $0.01 m s^{-1}$	[3]
Question 5 Total			[13]

31. (a)	(i) Ruler and wire shown and labelled (1) Moving pointer or jockey or crocodile clip indicated (1) Either: Correctly positioned ohmmeter with no power supply; or correctly positioned voltmeter and ammeter with power supply (1) [No labelling required for either method].	[3]
	(ii) Diagonal line through origin	[1]
	(iii) CSA from <u>diameter of wire</u> (1) Gradient from graph = (R/l) or (ρ/A) Or stated take a pair of R and l values from the graph (1) $\rho = \text{gradient} \times \text{CSA}$ or use of $\rho = RA/l$ (1)	[3]
(b)	(i) $R = \frac{144}{32} = 4.5 [\Omega]$ (1) Correct substitution into $R = \rho l/A$ (1) $l = 0.375 [\text{m}]$ (1) (ecf on R)	[3]
	(ii) $I = 2.7 [\text{A}]$ (from V/R or P/V etc) (1) (ecf on l) Correct substitution into $I = nAve$ (1) $v = 1.24 \times 10^{-2} [\text{m s}^{-1}]$ (1) accept 0.01 m s^{-1}	[3]