

Name: \_\_\_\_\_

EMF

Questions

**Date:**

**Time:**


**Total marks available:**

**Total marks achieved:** \_\_\_\_\_

## **Questions**

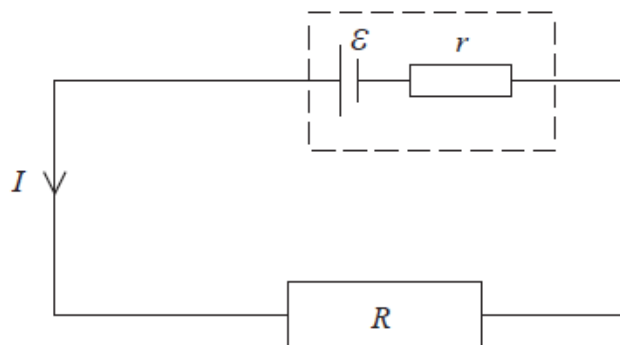Q1.

The diagram shows a resistor of resistance  $R$  across a cell of e.m.f.  $\varepsilon$  and internal resistance  $r$ .




Which of the following is a correct expression for the current  $I$ ?

- A**  $I = \varepsilon / r$
- B**  $I = \varepsilon / R$
- C**  $I = \varepsilon / (R + r)$
- D**  $I = \varepsilon / (R - r)$

**(Total for question = 1 mark)**

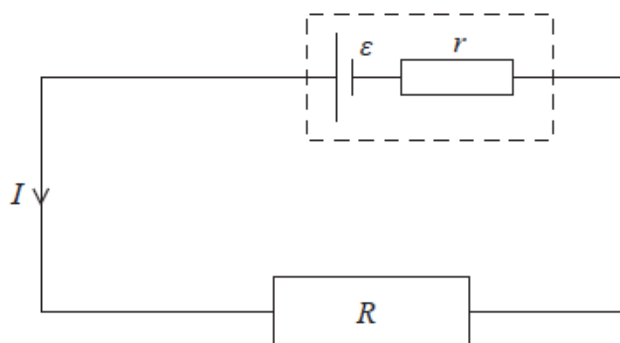Q2.

The diagram represents a resistor of resistance  $R$  in a series circuit with a cell of e.m.f.  $\varepsilon$  and internal resistance  $r$ .



Which of the following correctly gives the potential difference  $V$  across the internal resistance?

**A**  $V = \frac{\epsilon(R+r)}{r}$

**B**  $V = \frac{\epsilon R}{R+r}$

**C**  $V = \frac{\epsilon(R+r)}{R}$


**D**  $V = \frac{\epsilon r}{(R+r)}$

**(Total for question = 1 mark)**

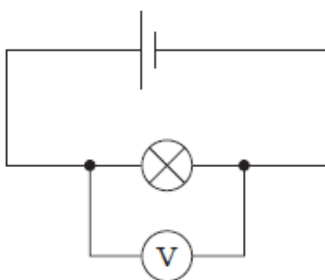Q3.

A torch uses a 1.5 V dry cell. Over time, the light intensity produced by the torch decreases as the cell 'goes flat'.

Student A sets up the following circuit in an attempt to measure the e.m.f. of a cell.



Explain why the voltmeter reading will **not** be the e.m.f. of the cell.

(2)

.....

.....

.....

.....

**(Total for question = 2 marks)**

Q4. When a cell of e.m.f. 1.5 V is connected across a resistance of  $6.6 \Omega$  the current is  $0.21$  A.

Calculate the internal resistance of the cell.

(3)

.....

.....

.....

.....

.....

.....

Internal resistance = .....

**(Total for Question = 3 marks)**

Q5.

A torch uses a 1.5 V dry cell. Over time, the light intensity produced by the torch decreases as the cell 'goes flat'.

Student B correctly determined the e.m.f. of an unused cell as 1.63 V and its internal resistance as  $1.15 \Omega$ .

He repeated this after the cell had been used for several weeks. When a voltmeter was connected directly across the used cell, the reading was 1.36 V.

A bulb of resistance  $5.92 \Omega$  was then connected across the used cell and the reading fell to 0.84 V.

Student A suggests that the cell goes flat as it is used because the e.m.f. decreases.

Student B suggests it is because the internal resistance increases.

Determine whether either student is correct about the changes in the cell as it goes flat.

(5)

.....

.....

.....

.....

.....

.....

.....

.....


.....

.....

**(Total for question = 5 marks)**

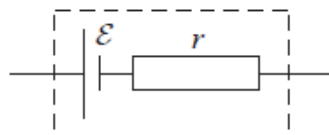Q6.


A cell may be represented as an e.m.f.  $\mathcal{E}$  in series with an internal resistance  $r$ .



A student used the relationship  $V = \mathcal{E} - Ir$  and a graphical method to determine  $\mathcal{E}$  and  $r$ . She connected a cell in a circuit and took a series of measurements of the current  $I$  in the cell and the potential difference  $V$  across the terminals of the cell.


(a) Complete a circuit diagram of a circuit she could have used.

(2)

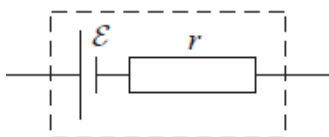

(b) The student's measurements are shown in the table and plotted on the graph.

$I / \text{mA}$	$V / \text{V}$
27.5	3.97
41.0	3.94
51.6	3.90
78.6	3.88
143.0	3.75

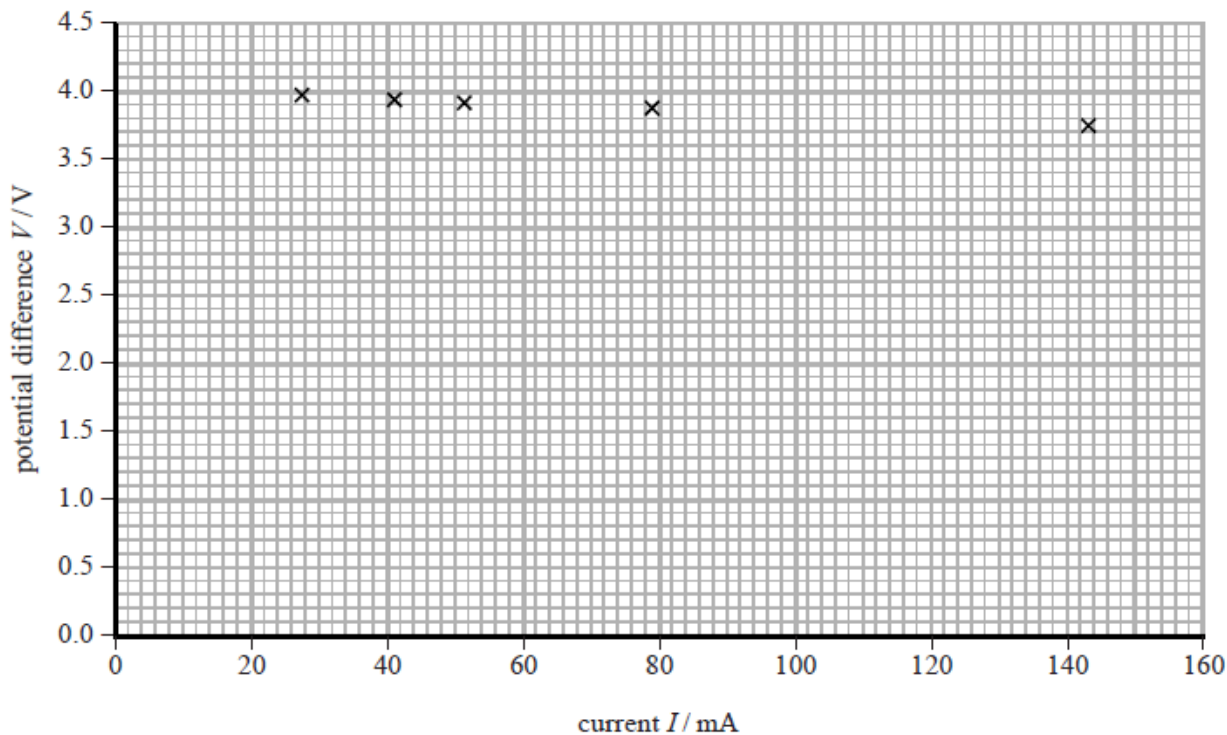

Determine values for  $\epsilon$  and  $r$  from the graph and show how you obtained your answers.

(4)

.....

.....

.....

.....

.....

.....


$\epsilon =$  .....

$r =$  .....

(c) Explain how the graph could be constructed to obtain better values for  $\epsilon$  and  $r$ .

(2)

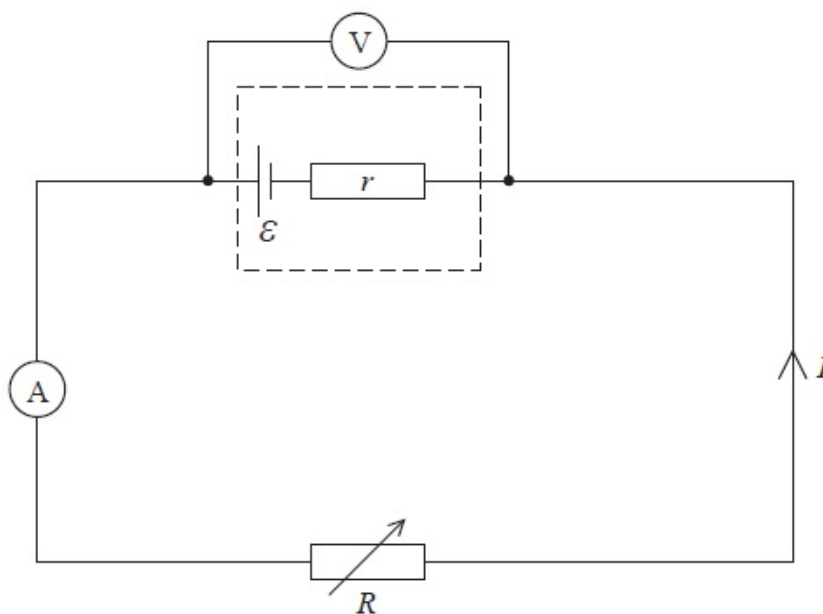
Q7. The diagram shows a circuit which may be used to find the emf  $\varepsilon$  and internal resistance  $r$  of a cell.



(a) As the resistance  $R$  of the variable resistor is varied, values of the current  $I$  in the circuit and the terminal potential difference  $V$  across the cell are recorded.

Sketch the graph of  $V$  against  $I$  and explain how it may be used to determine  $\varepsilon$  and  $r$ .

(5)

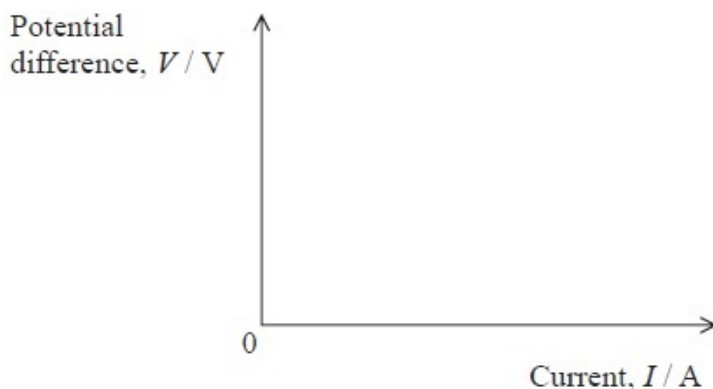

.....  
.....  
.....

\*(b) We usually assume that ammeters have negligible resistance and voltmeters have infinite resistance.

The determination of  $\epsilon$  and  $r$  is not affected by using an ammeter with non-negligible resistance but is affected by using a voltmeter with a low resistance.

Explain why.

(4)

.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....

**(Total for Question = 9 marks)**