

Name: \_\_\_\_\_

Edexcel\_Potential\_Divider

Mark Scheme

**Date:**

**Time:**

**Total marks available:**

**Total marks achieved:** \_\_\_\_\_

## **Mark Scheme**

Q1.

Question Number	Answer	Mark
	C	1


Q2.

Question Number	Answer	Mark
	B	1

Q3.

Question Number	Answer	Mark
	B	1

Q4.

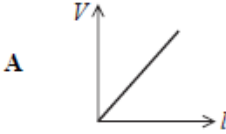Question Number	Acceptable Answer	Additional Guidance	Mark
	A 		1

Q5.

Question Number	Answer	Mark
	D $\frac{R_2}{R_1+R_2} V$	1
	Incorrect Answers: A – this looks similar to the correct formula but has an incorrect resistance as the numerator and does not have the total resistance as the denominator B – this looks similar to the correct formula with the correct resistance as the numerator but does not have the total resistance as the denominator C – This would give the PD across resistor $R_1$ and not $R_2$	

Q6.

Question Number	Answer	Mark
	D	1

Q7.

Question Number	Acceptable Answer	Additional Guidance	Mark
	<p>An explanation that makes reference to the following:</p> <ul style="list-style-type: none"> <li>• Combined resistance of (light) bulb and LDR is about <math>3\ \Omega</math> (in the dark) Or the combined resistance is less than the resistance of bulb/LDR (1)</li> <li>• The combined resistance is always much less than the (<math>75\ \Omega</math>) fixed resistance (1)</li> <li>• The p.d. across the bulb will be much less than <math>3\ \text{V}</math> and so the bulb will not come on (in the dark). (1)</li> </ul>	MP3: accept the idea that the p.d. across the bulb is never high enough to make the bulb come on in the dark	3

Q8.

Question Number	Acceptable Answer	Additional Guidance	Mark
	<ul style="list-style-type: none"> <li>• potential difference across the LDR = 3.6 V Or <math>\frac{R}{(R+75 \Omega)}</math> seen Or <math>\frac{75 \Omega}{(R+75 \Omega)}</math> seen (1)</li> <li>• Use of <math>V = IR</math> Or resistance ratio <math>\times 6.0 \text{ V} =</math> corresponding p.d. (1)</li> <li>• <math>R = 110 \Omega</math> (1)</li> </ul>	<p>MP2 use of <math>V = IR</math> with 2.4 V or 3.6 V only</p> <p><u>Example of calculation</u></p> <p><math>I = 2.4 \text{ V} / 75 \Omega = 0.032 \text{ A}</math> Voltage across LDR = 6.0 V – 2.4 V = 3.6 V <math>R = \frac{3.6 \text{ V}}{0.032 \text{ A}}</math> <math>R = 112.5 \Omega</math></p> <p>Or use of ratios <math>\frac{75 \Omega}{(R+75 \Omega)} \times 6.0 \text{ V} = 2.4 \text{ V}</math> <math>R = 112.5 \Omega</math></p>	<b>3</b>

Q9.

Question Number	Answer	Mark	
(a)(i)	Determines width of at least 9 coils Use of half of their diameter in $\pi r^2$ Area = $(1.96 \text{ to } 2.42) \times 10^{-7} (\text{m}^2)$  <u>Example of calculation</u> 18 coils = 1.00 cm Diameter = $0.0100 \text{ m} \div 18 = 5.56 \times 10^{-4} \text{ m}$ Area = $\pi \times (5.56 \times 10^{-4} \div 2)^2$ Area = $2.42 \times 10^{-7} \text{ m}^2$	(1) (1) (1)	3
(a)(ii)	Use of $R = \rho l / A$ Resistivity magnitude = $4.4 \times 10^{-7}$ (show that value gives $3.7 \times 10^{-7}$ ) Unit $\Omega \text{m}$  <u>Example of calculation</u> $\rho = RA / l$ $= 22 \Omega \times 2.4 \times 10^{-7} \text{ m}^2 / 12 \text{ m}$ $= 4.4 \times 10^{-7} \Omega \text{m}$	(1) (1) (1)	3
(a)(iii)	A sensible response with some detail, e.g. <ul style="list-style-type: none"> <li>• Avoid difficulty in reading a small scale while holding it and counting turns</li> <li>• it can be enlarged and done more accurately</li> <li>• compare with unravelling and using a micrometer</li> <li>• remains stationary, so easier to measure accurately</li> <li>• you can mark the coils as you go so you don't lose count</li> </ul> (treat parallax as neutral and )	(1)	1
(b)	Use of ratio of lengths $\times$ pd $V = 8.2 \text{ V}$  <u>Example of calculation</u> $V = (7.0 \text{ cm} / 10.2 \text{ cm}) \times 12 \text{ V}$ $= 8.2 \text{ V}$	(1) (1)	2
<b>Total for question</b>			<b>9</b>

Q10.

Question Number	Acceptable answers	Additional guidance	Mark
(a)	<ul style="list-style-type: none"> <li>• (UV radiation consists of) photons</li> <li>• One photon interacts with one electron</li> <li>Or energy of photon depends on frequency</li> <li>• Electrons released if energy (of photon) greater than work function</li> <li>Or frequency is greater than threshold frequency</li> <li>Or <u>energy</u> supplied is sufficient to remove electron</li> </ul>	(1) (1) (1)	3

Question Number	Acceptable answers	Additional guidance	Mark
(b)(i)	<ul style="list-style-type: none"> <li>when slider at the bottom - reading on voltmeter is zero Or minimum resistance - reading on voltmeter is zero (1)</li> <li>When slider at the top – reading on voltmeter is 1.5 V Or maximum resistance - reading on voltmeter is 1.5 V (1)</li> <li>Potential difference split between top and bottom part of resistor (either side of slider) Or reading on voltmeter depends on the ratio of resistances (either side of slider) Or moving the slider changes the resistance that the voltmeter is across (1)</li> </ul>		3

Question Number	Acceptable answers	Additional guidance	Mark
(b)(ii)	Maximum Kinetic Energy of electron = 0.6 (eV) (1)		1

Question Number	Acceptable answers	Additional guidance	Mark
(c)	<p><b>Max 4</b></p> <p>Valid because:</p> <ul style="list-style-type: none"> <li>Moon and photocell both have vacuum (1)</li> <li>Both demonstration and theory use photoelectric effect (1)</li> </ul> <p>Not valid because:</p> <ul style="list-style-type: none"> <li>Different wavelengths in each case (1)</li> <li>On the moon there is dust not metal (1)</li> <li>Dust is free to move but the metal plate is fixed (1)</li> <li>On the moon UV removes electrons from (individual) <u>atoms</u> and in the demo light removes electrons from metal <u>surface</u> (1)</li> <li>Demonstration is based on photoelectric effect but effect on moon could be ionisation (1)</li> </ul>	<p>Full marks can only be scored if a correct link is made between at least one physics point and the demonstration being valid or not valid</p> <p>Accept the same concept for photoelectric effect</p> <p>Accept one uses light the other UV</p> <p>Accept different materials for MP4</p>	4

Q11.

Question Number	Acceptable answers	Additional guidance	Mark
	<ul style="list-style-type: none"> <li>p.d. across capacitor increases Or p.d. across resistor decreases (1)</li> <li>p.d. across capacitor increases to 5V (1)</li> <li>p.d. across resistor starts at 5V and reduces to 0V (1)</li> <li>Exponentially (1)</li> </ul>		4

Q12.

Question Number	Acceptable answers	Additional guidance	Mark
(a)	<ul style="list-style-type: none"> <li><math>V</math> at top/start = 0V Or recognition "potential divider" Or <math>V</math> increases (by implication) Or <math>V</math> at bottom = 1.5V (1)</li> <li>Two sections of wire act as series resistors Or <math>R = \rho l/A</math> Or comment about <math>R</math> proportional to length (1)</li> <li>Or <math>\frac{V}{1.5} = \frac{R}{R_T}</math></li> <li>potential difference proportional to length of wire (1)</li> </ul>	<p><b>Alternative MS</b>                      Constant Current (<math>I</math>) in wire (1)                      p.d. across section of wire = <math>Ir</math> between A and loop (1)                      Increases from 0V to 1.5V linearly (1)</p>	3

Question Number	Acceptable answers	Additional guidance	Mark
(b)	<ul style="list-style-type: none"> <li>Tangent drawn at 1.5 s (1)</li> <li>Scales p.d. to give distance (1)</li> <li>Gradient determined using a base of triangle of at least 1.0 s Or use of <math>s = \frac{(u+v)}{2}t</math> and correct <math>V</math> read from graph (1)</li> <li>velocity = 1.0 m s<sup>-1</sup> – 1.3 m s<sup>-1</sup> (1)</li> </ul>	<p><u>Example of calculation</u>                      Gradient = <math>\frac{1.1V - 0.2V}{1.0s} = 0.9Vs^{-1}</math>                      As 1.5 V represents 2.00 m  <math>v = 0.9 Vs^{-1} \times \frac{2.00m}{1.5V} = 1.2 ms^{-1}</math></p>	4

Question Number	Acceptable answers	Additional guidance	Mark
(c)	<ul style="list-style-type: none"> <li>• Use of <math>v = u + at</math></li> <li>• Use of <math>a = g \sin \theta</math></li> <li>• Calculates a value for <math>a</math>, <math>\theta</math> or <math>v</math> (using a SUVAT AND <math>a = g \sin \theta</math>)</li> <li>• Valid comparison of their calculated quantity and the stated quoted uncertainty.</li> </ul>	<p>(1) <u>Example of calculation</u>  <math>1.5 \text{ m s}^{-1} = 1.2 \text{ m s}^{-1} + a \times 0.5 \text{ s}</math>  <math>a = \frac{0.3 \text{ m s}^{-1}}{0.5} = 0.6 \text{ m s}^{-2}</math></p> <p>(1)</p> <p>(1) <math>0.6 \text{ m s}^{-2} = 9.81 \text{ m s}^{-2} \sin \theta</math>  <math>\theta = 3.6^\circ</math></p>	<b>4</b>